
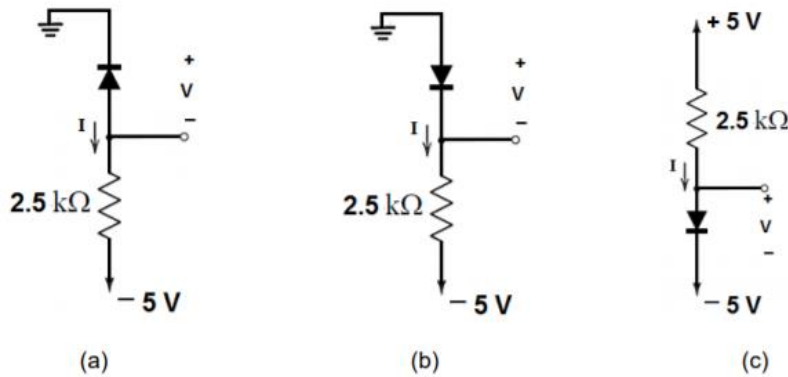


PN Junction Diode

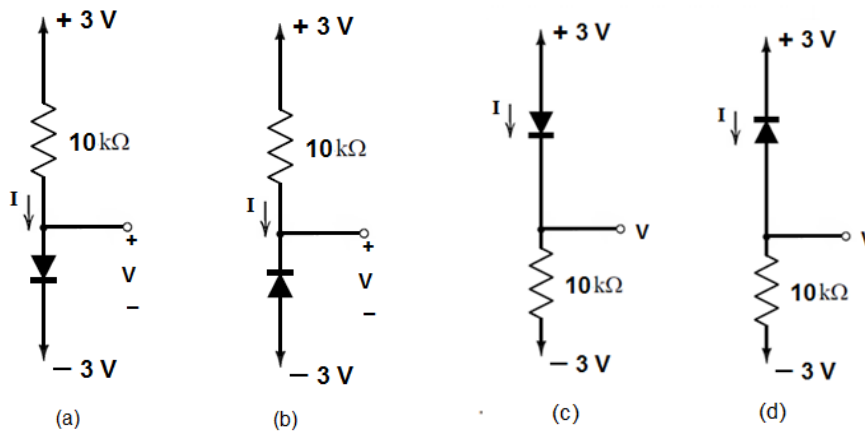
Q1. Find the values of I and V in the circuits shown below. Assume diodes to be ideal.



Q2. For the circuits shown using ideal diodes find the values of voltage and current.



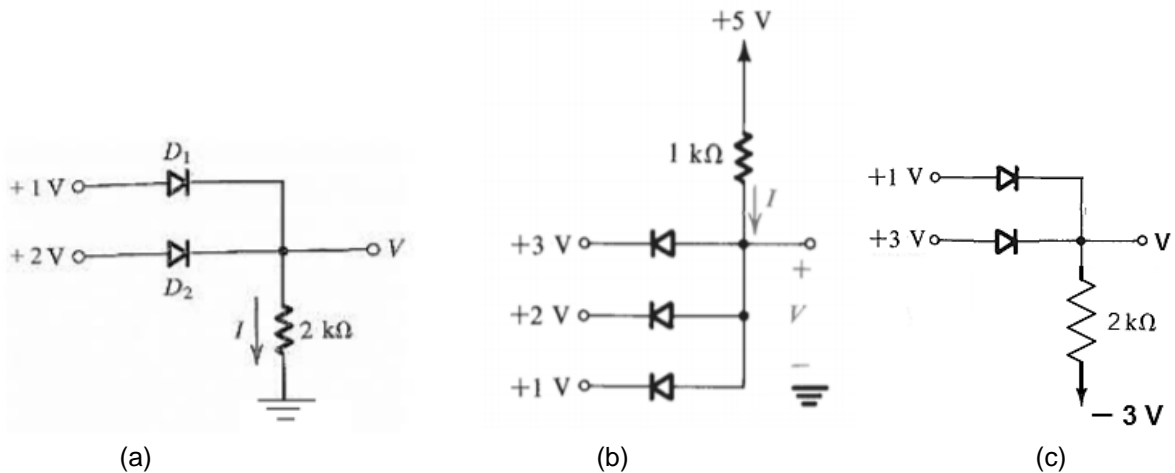Q3. Determine I and V . Assume diodes to be ideal.




Q4. Consider a silicon diode with $\eta = 1.5$. Find the change in voltage if the current changes from 0.1 mA to 10 mA.

Q5. A silicon junction diode with $\eta = 1$ has $v = 0.7$ V at $i = 1$ mA. Find the voltage drop at $i = 0.1$ mA.


Q6. Find the value of the diode small-signal resistance r_d at bias current of 10 mA. Assume $\eta = 1$.

PN Junction Diode

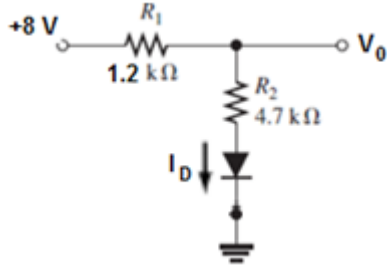
Q7. Determine I_D and V_0 for the following circuit.



(a)

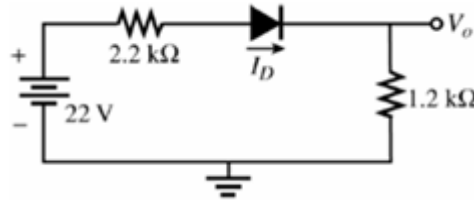


(b)

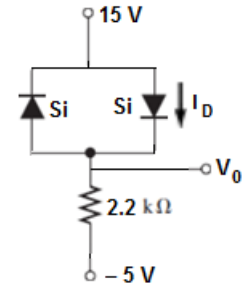

(c)

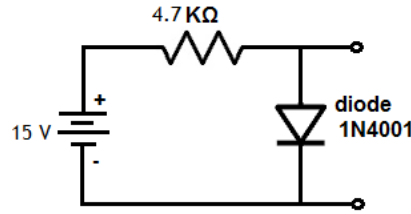Q8. A silicon diode is used in the circuit as shown. Calculate the diode current.



Q9. Determine the current I_D and the diode voltage V_D for the circuit shown with $V_{DD} = 5\text{ V}$ and $R = 1\text{ k}\Omega$. Assume that the diode has a current of 1 mA at a voltage of 0.7 V.

