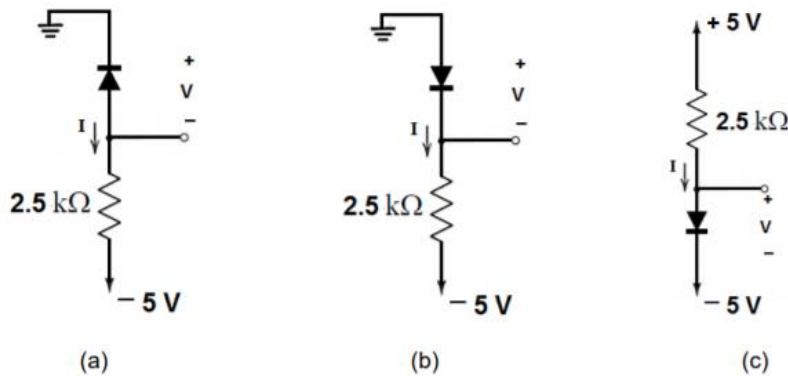


19EEE114 Electronic Circuits
SOLUTION


Assignment #1

Q1. Find the values of I and V in the circuits shown below. Assume diodes to be ideal.




[Ans: (a) 0 mA, 5 V; (b) 2 mA, 0 V; (c) 4 mA, - 5 V]

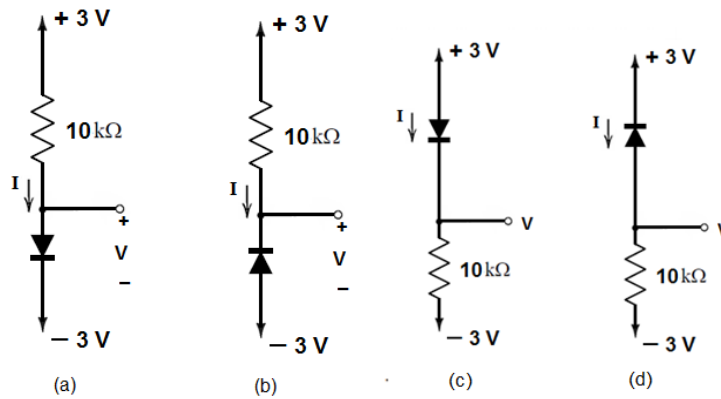Q2. For the circuits shown using ideal diodes find the values of voltage and current.



[Ans: (a) - 3V, 0.6mA; (b) 3V, 0 mA; (c) 3V, 0.6mA; (d) - 3V, 0 mA]

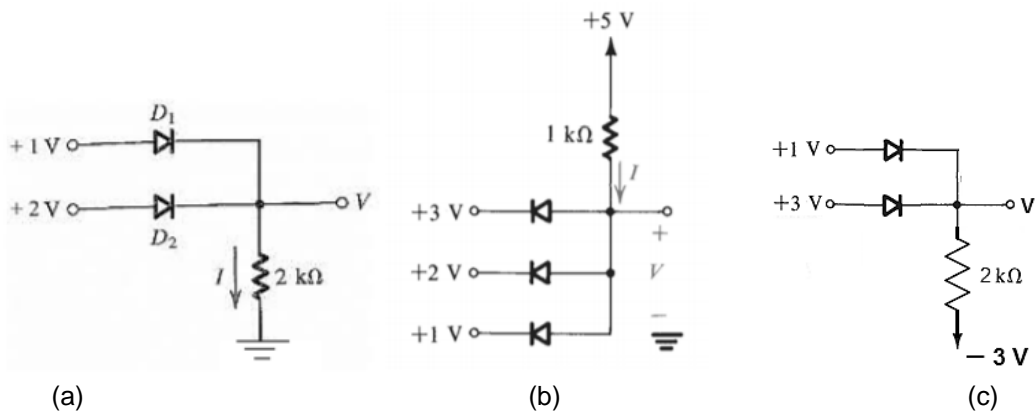Q3. Determine I and V . Assume diodes to be ideal.



[Ans: (a) 1 mA, 2 V; (b) 4 mA, 1 V; (c) 3 V, 3 mA]

Q4. Consider a silicon diode with $\eta = 1.5$. Find the change in voltage if the current changes from 0.1 mA to 10 mA.
[Ans: 172.5 mV]

Q5. A silicon junction diode with $\eta=1$ has $v = 0.7$ V at $i = 1$ mA. Find the voltage drop at $i = 0.1$ mA.
[Ans: 0.64]


Q6. Find the value of the diode small-signal resistance r_d at bias current of 10 mA. Assume $\eta=1$.
[Ans: 2.5 Ω]

19EEE114 Electronic Circuits
SOLUTION

Assignment #1

Q7. Determine I_D and V_o for the following circuit.

(a)

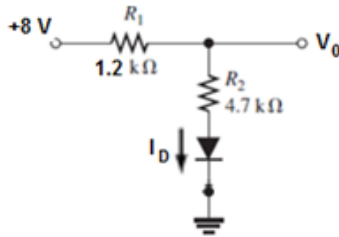


Sol:

Diode forward-biased,

$$I_D = \frac{8 \text{ V} - 0.7 \text{ V}}{1.2 \text{ k}\Omega + 4.7 \text{ k}\Omega} = \mathbf{1.24 \text{ mA}}$$

$$V_o = V_{4.7 \text{ k}\Omega} + V_D = (1.24 \text{ mA})(4.7 \text{ k}\Omega) + 0.7 \text{ V} = \mathbf{6.53 \text{ V}}$$

(b)

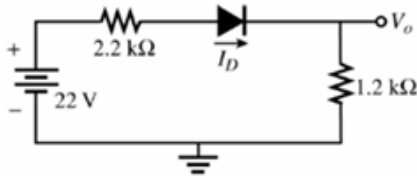


Sol:

Diode forward-biased

$$I_D = \frac{22 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega + 1.2 \text{ k}\Omega} = \mathbf{6.26 \text{ mA}}$$

$$V_o = I_D(1.2 \text{ k}\Omega) = (6.26 \text{ mA})(1.2 \text{ k}\Omega) = \mathbf{7.51 \text{ V}}$$

(c)

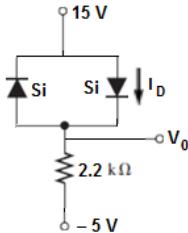


Sol:

Right diode forward-biased:

$$I_D = \frac{15 \text{ V} + 5 \text{ V} - 0.7 \text{ V}}{2.2 \text{ k}\Omega} = \mathbf{8.77 \text{ mA}}$$

$$V_o = 15 \text{ V} - 0.7 \text{ V} = \mathbf{14.3 \text{ V}}$$

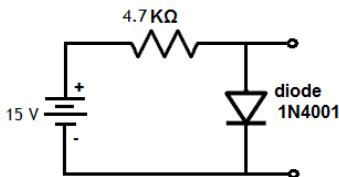
Q8. A silicon diode is used in the circuit as shown. Calculate the diode current.



Sol:

$$V = I_D R + V_D \Rightarrow I_D = (15 - 0.7) / 4.7 = \mathbf{3.04 \text{ mA}}$$

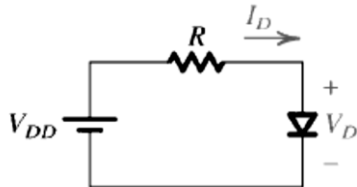Q9. Determine the current I_D and the diode voltage V_D for the circuit shown with $V_{DD} = 5 \text{ V}$ and $R = 1 \text{ k}\Omega$. Assume that the diode has a current of 1 mA at a voltage of 0.7 V.



Sol:

assume that $V_D = 0.7 \text{ V}$

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.7}{1} = \mathbf{4.3 \text{ mA}}$$

$$V_2 - V_1 = 2.3 V_T \log \frac{I_2}{I_1}$$

$$V_2 = V_1 + 0.06 \log \frac{I_2}{I_1}$$

Substituting $V_1 = 0.7 \text{ V}$, $I_1 = 1 \text{ mA}$, and $I_2 = 4.3 \text{ mA}$ results in $V_2 = \mathbf{0.738 \text{ V}}$.