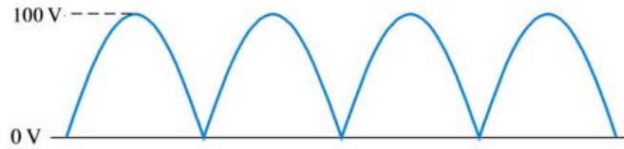








Applications of Diode

Q1. Find the average value of the full-wave rectified voltage shown below.



Q2. A diode with $V_F = 0.7 \text{ V}$ is connected as a half-wave rectifier. The load resistance is $470 \text{ } \Omega$ and the ac input is 2 V from the secondary of transformer. Determine the peak output voltage, peak load current and the diode peak reverse voltage.

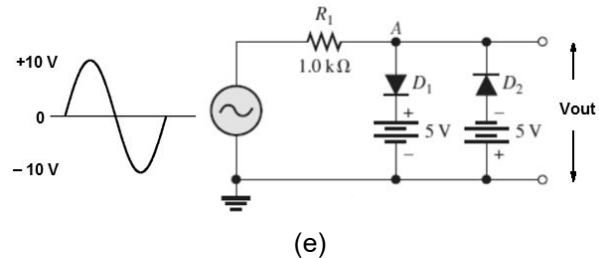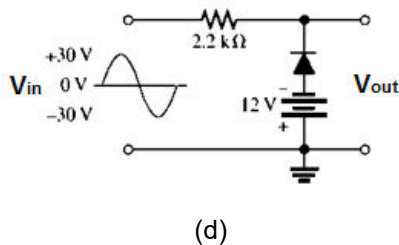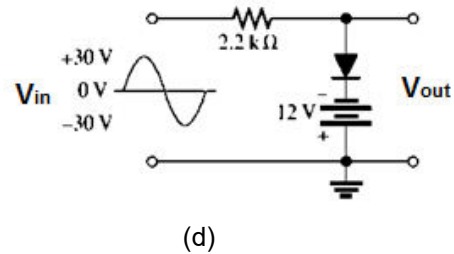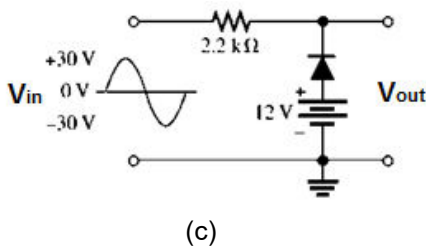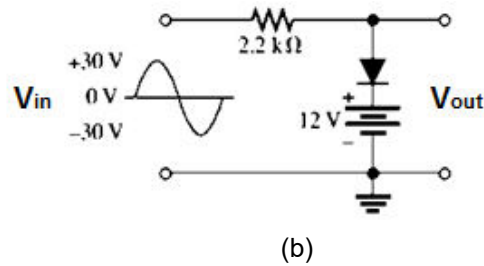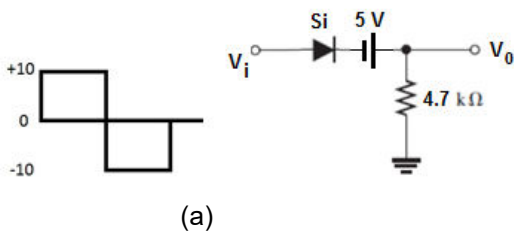Q3. Determine the output waveform of the following circuits for the given input signals.



Q4. For a certain Zener diode, $V_Z = 10 \text{ V}$ at $I_{ZT} = 30 \text{ mA}$. If $Z_Z = 8 \text{ } \Omega$, what is the terminal voltage at $I_Z = 50 \text{ mA}$?

Q5. A Zener regulator has an input voltage that may vary from 22 V to 30 V . If the regulated output voltage is 12 V and the load resistance varies from $140 \text{ } \Omega$ to $10 \text{ k} \Omega$, what is the maximum allowable series resistance?

Q6. A Zener regulator has an input voltage ranging from 15 V to 20 V and a load current ranging from 5 mA to 20 mA . If the Zener voltage is 6.8 V , what is the maximum allowable series resistance?

Q7. A Zener diode whose nominal voltage is 10 V at 10 mA has an incremental resistance of $50 \text{ } \Omega$.

- What is the value of V_{Z0} in the Zener model?
- What voltage do you expect if the diode current is doubled?