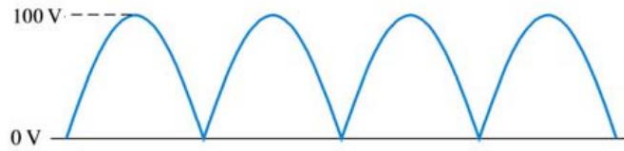


**19EEE114 Electronic Circuits**  
**SOLUTION**

Assignment #2

**Q1.** Find the average value of the full-wave rectified voltage shown below.



**Solution:**

$$V_{avg} = 2V_m/\pi = (2 \times 100)/\pi = 63.69 \text{ V}$$

**Q2.** A diode with  $V_F = 0.7 \text{ V}$  is connected as a half-wave rectifier. The load resistance is  $470 \Omega$  and the ac input is  $12 \text{ V}$  from the secondary of transformer. Determine the peak output voltage, peak load current and the diode peak reverse voltage.

**Solution:**

$$V_{in} = 1.414 \times 12 = 16.968 \text{ V}$$


$$V_{out} = V_{in} - V_F = 16.968 - 0.7 = 16.268 \text{ V}$$

$$I = 16.268/470 = 34.61 \text{ mA}$$

$$PIV = V_{peak} = 16.968 \text{ V}$$


**Q3.** Determine the output waveform of the following circuits for the given input signals.

(a)

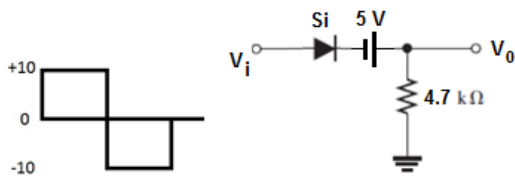


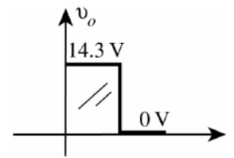**Sol:**


Positive pulse of  $v_i$ :  
 $V_o = 10 \text{ V} - 0.7 \text{ V} + 5 \text{ V} = 14.3 \text{ V}$   
 Negative pulse of  $v_i$ :  
 diode "open",  $v_o = 0 \text{ V}$




(b)

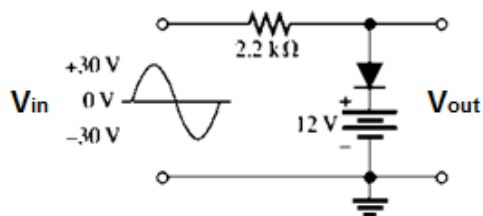

**Sol:**

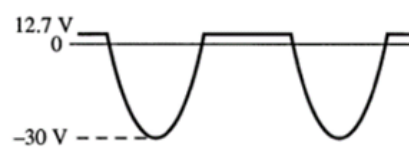


(c)

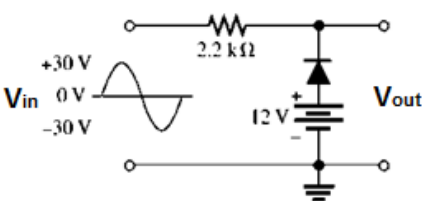


**Sol:**



(d)

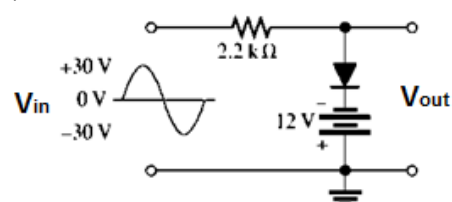


**Sol:**

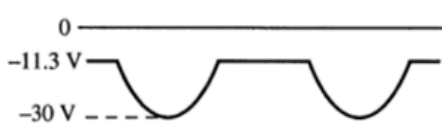


19EEE114 Electronic Circuits  
SOLUTION

Assignment #2


(e)

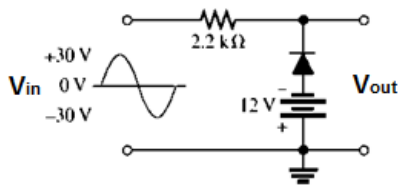


Sol:

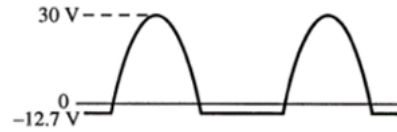

(f)

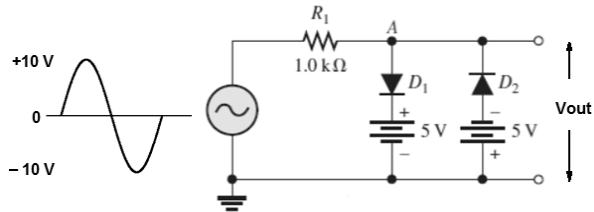

Sol:

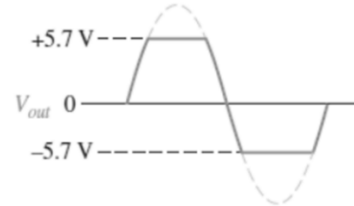

Q4. For a certain Zener diode,  $V_Z = 10\text{ V}$  at  $I_{ZT} = 30\text{ mA}$ . If  $Z_Z = 8\Omega$ , what is the terminal voltage at  $I_Z = 50\text{ mA}$ ?

Sol:

$$V_Z = 10\text{ V} + (20\text{ mA})(8) = 10.16\text{ V}$$

Q5. A Zener regulator has an input voltage that may vary from 22 to 30 V. If the regulated output voltage is 12V and the load resistance varies from 140  $\Omega$  to 10 k $\Omega$ , what is the maximum allowable series resistance?

Sol:

$$R_{S(\max)} = \left( \frac{V_{S(\min)}}{V_Z} - 1 \right) R_{L(\min)}$$

$$R_{S(\max)} = (22/12 - 1) \times 140 = 117\ \Omega$$

As long as the series resistance is less than 117  $\Omega$ , the zener regulator will work properly under all operating conditions.

Q6. A Zener regulator has an input voltage ranging from 15 to 20 V and a load current ranging from 5 to 20 mA. If the Zener voltage is 6.8 V, what is the maximum allowable series resistance?

Sol:

$$R_{S(\max)} = \frac{V_{S(\min)} - V_Z}{I_{L(\max)}}$$

$$R_{S(\max)} = (15 - 6.8)/20\text{ mA} = 410\ \Omega$$

If the series resistance is less than 410  $\Omega$ , the zener regulator will work properly under all conditions.

Q7. A Zener diode whose nominal voltage is 10 V at 10 mA has an incremental resistance of 50  $\Omega$ .

- What is the value of  $V_{Z0}$  in the Zener model?
- What voltage do you expect if the diode current is doubled?

Sol:

$$V_Z = V_{Z0} + I_Z r_Z$$

$$10 = V_{Z0} + 50\ \Omega \times 10\text{ mA}$$

$$\text{a) } V_{Z0} = 9.5\text{ V}$$

$$I_Z = 20\text{ mA} \Rightarrow V_Z = 9.5 + 20\text{ mA} \times 50 = 10.5\text{ V}$$

$$\text{b) } V_Z = 10.5\text{ V}$$