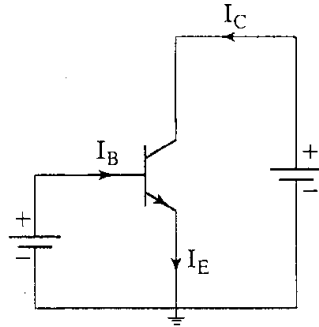
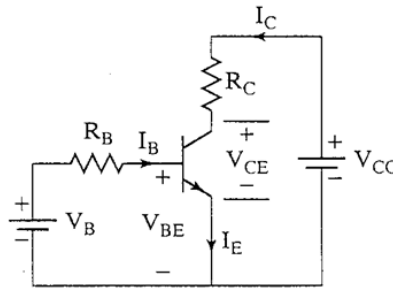


- Q1.** A transistor has a current gain of 175. If the base current is 0.1 mA, what is the collector current?
- Q2.** A transistor has a collector current of 10 mA and a base current of 40 μ A. What is the current gain of the transistor?
- Q3.** Consider an npn transistor with $v_{BE} = 0.7$ V at $i_C = 1$ mA. Find v_{BE} at $i_C = 0.1$ mA and 10 mA.
- Q4.** Transistors of a certain type are specified to have β values in the range 50 to 150. Find the range of their α values.
- Q5.** A transistor is connected as shown in figure and has a base current of 16 μ A and a beta of 80. What is the collector current and emitter current of the transistor?



- Q6.** Measurement of an npn BJT in a particular circuit shows the base current to be 14.46 μ A, emitter current to be 1.460 mA, and the base-emitter voltage to be 0.7 V. Calculate α , β , and I_S .
- Q7.** For the circuit shown below with $R_B = 100$ k Ω , $R_C = 2$ k Ω , $V_B = 3$ V, $V_{CC} = 9$ V and $\beta = 120$, determine the collector current and V_{CE} .



- Q8.** Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the circuit. Assume $\beta_{DC} = 150$.

