
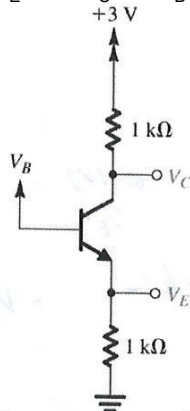


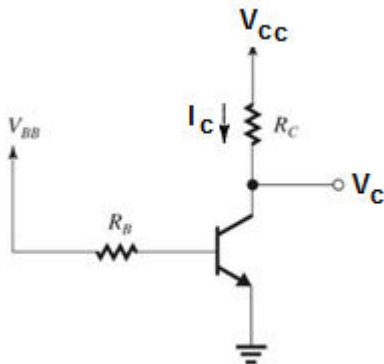
Q1. The Transistor in the circuit below has a very high β , Find V_E and V_C for $V_B = +2.0V$.




Q2. For the circuit below let $V_{CC} = 10V$, $R_C = 1k\Omega$, and $R_B = 10k\Omega$. The bipolar junction transistor has $\beta = 50$. Find the values of V_{BB} that results in the transistor operating
 (a) in the active mode with $V_C = 2V$;
 (b) at the edge of saturation;
 (c) deep in saturation with $\beta_{forced} = 10$.
 Assume $V_{BE} \approx 0.7V$.



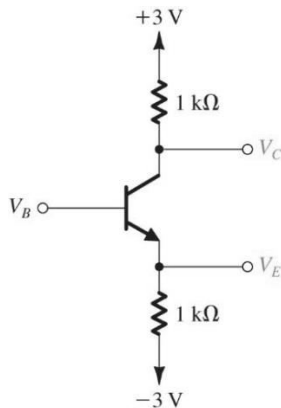
Q3. Consider the operation of the circuit shown below for V_B at $-1V$, $0V$, and $+1V$. Assume that β is very high. What values of V_E and V_C result? What is the mode of operation of transistor in each case.



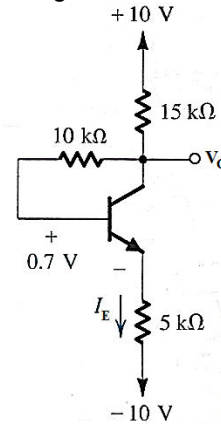
Q4. For the circuit shown below, assume that the transistor has very large β . Find the values of the labeled voltages and current.



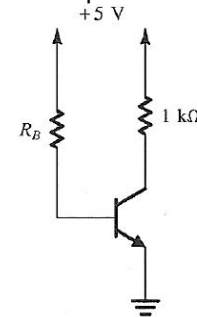Q5. For the circuit shown, design a value for R_B so that the transistor saturates with an overdrive factor of 10. The BJT is specified to have a minimum β of 20 and $V_{CEsat} = 0.2V$. What is the value of forced β achieved?




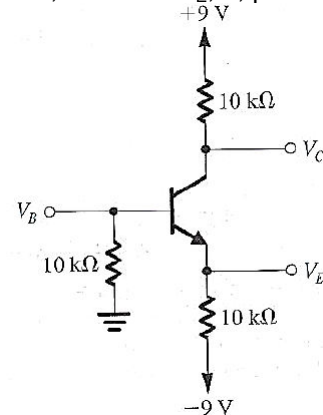Q6. For the circuit shown, $V_B = -1.5V$. Assuming $V_{BE} = 0.7V$, calculate V_E , α , β and V_C .




Q7. A transistor with $\beta = 120$ is biased to operate at a DC collector current of $1.2mA$. Find the values of g_m , r_π , and r_e .

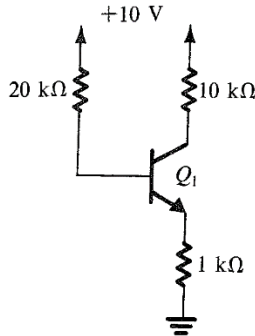
Q8. Find the collector voltage in the circuit shown below. Also, calculate forced β for the transistor. Assume the transistor is operating in saturation.




Q9. Consider the circuit shown below. Find the emitter, base and collector voltages and currents. Use $\beta=50$, but assume $|V_{BE}| = 0.8\text{ V}$ independent of current level.

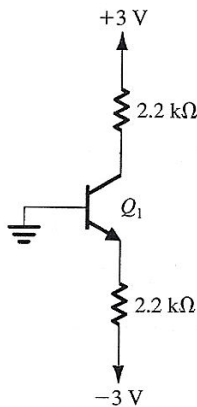

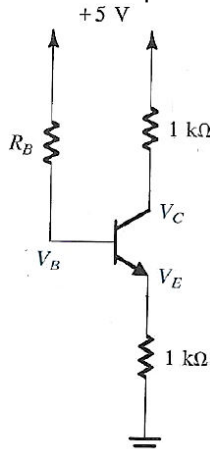
Q10. For the circuit shown below, find V_B , V_E and V_C for $R_B = 100\Omega k$. Let $\beta=100$.



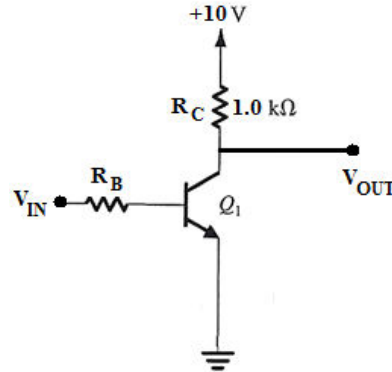Q11. (a) For the transistor circuit shown, what is V_{CE} when $V_{IN} = 0\text{ V}$?
 (b) What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Neglect $V_{CE(sat)}$.
 (c) Calculate the maximum value of R_B when $V_{IN} = 5\text{ V}$.



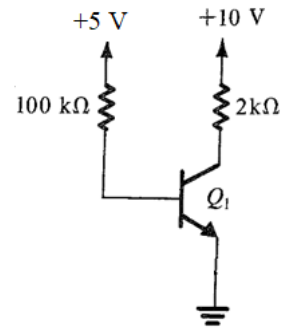Q12. Determine the voltage at all nodes and current through the branches. Assume $\beta=100$.



Q13. Determine the voltage at all nodes and current through the branches. Assume $\beta=100$.

