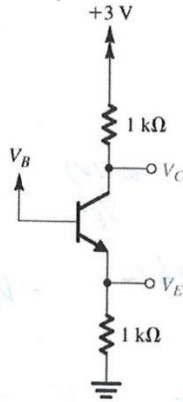


Q1. The Transistor in the circuit below has a very high β , Find V_E and V_C for $V_B = +2.0V$.



Solution:

$$V_{BE} = V_B - V_E$$

$$V_E = V_B - V_{BE} = 2 - 0.7 = 1.3 \text{ V}$$

$$I_E = V_E / R_E = 1.3 \text{ mA}$$


Transistor has high β , $\Rightarrow I_C \simeq I_E = 1.3 \text{ mA}$

$$V_C = V_{CC} - I_C R_C = 3 - 1.3 = 1.7 \text{ V}$$

Q2. For the circuit below let $V_{CC} = 10 \text{ V}$, $R_C = 1\text{k}\Omega$, and $R_B = 10 \text{ k}\Omega$. The bipolar junction transistor has $\beta = 50$. Find the values of V_{BB} that results in the transistor operating

- in the active mode with $V_C = 2 \text{ V}$;
- at the edge of saturation;
- deep in saturation with $\beta_{\text{forced}} = 10$.

Assume $V_{BE} \approx 0.7 \text{ V}$.

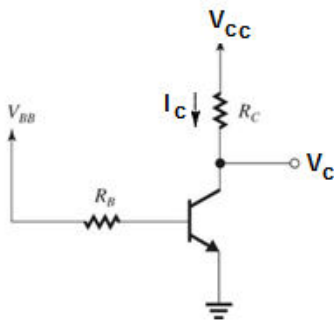

Solution:

$$(a) I_C = (V_{CC} - V_C) / R_C = (10 - 2) / 1 = 8 \text{ mA}$$

$$I_B = I_C / \beta = 0.16 \text{ mA}$$

$$V_{BB} = V_B + I_B R_B = 2.3 \text{ V}$$

$V_C > V_B$, therefore active mode

(b) at edge of saturation, $V_{CE} = 0.3 \text{ V}$

$$V_E = 0 \text{ V} \Rightarrow V_C = 0.3 \text{ V}$$

$$I_C = 9.7 \text{ mA}$$

$$I_B = 9.7 / 50 = 0.194 \text{ mA}$$

$$V_{BB} = 2.64 \text{ V}$$

(c) in deep saturation $V_{CE} = 0.2 \text{ V}$


$$V_E = 0 \text{ V} \Rightarrow V_C = 0.2 \text{ V}$$

$$I_C = 9.8 \text{ mA}$$

$$I_B = I_C / \beta_{\text{forced}} = 9.8 / 10 = 0.98 \text{ mA}$$

$$V_{BB} = 10.5 \text{ V}$$

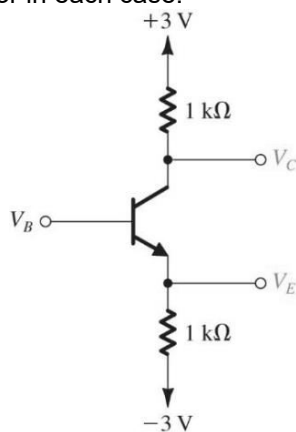Q3. Consider the operation of the circuit shown below for V_B at -1 V , 0 V , and $+1 \text{ V}$. Assume that β is very high. What values of V_E and V_C result? What is the mode of operation of transistor in each case.



Solution:

(a) $V_B = -1 \text{ V}$, $V_E = -1 - 0.7 = -1.7 \text{ V}$

$$I_C = I_E = (-1.7 - (-3)) / 1 = 1.3 \text{ mA}$$

$$V_C = 3 - 1.3 = 1.7 \text{ V}$$

$V_C > V_B$, therefore active region

(b) $V_B = 0 \text{ V}$, $V_E = -0.7 \text{ V}$

$$I_C = I_E = (-0.7 - (-3)) / 1 = 2.3 \text{ mA}$$

$$V_C = 3 - 2.3 = 0.7 \text{ V}$$

$V_C > V_B$, therefore active region

(c) $V_B = 1 \text{ V}$, $V_E = 1 - 0.7 = 0.3 \text{ V}$


$$I_C = I_E = (0.3 - (-3)) / 1 = 3.3 \text{ mA}$$

$$V_C = 3 - 3.3 = -0.7 \text{ V}$$

$V_C < V_B$, therefore saturation region

Not in active mode, so $I_C \neq I_E$, $V_C = V_E + V_{CE} = 0.5 \text{ V}$

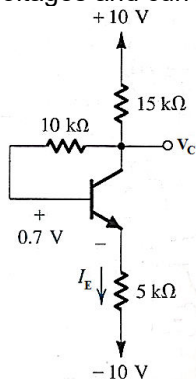Q4. For the circuit shown below, assume that the transistor has very large β . Find the values of the labeled voltages and current.



Solution:

Equating the collector and emitter currents:

$$I_C = I_E$$

$$\frac{10 - V_C}{15} = \frac{(V_C - 0.7) - (-10)}{5} \rightarrow 10 - V_C = 3V_C + 27.9$$

$$4V_C = -17.9$$


$$V_C = -4.475 \text{ V.}$$

$$I_C = \frac{10 - (-4.475)}{15} = 0.965 \text{ mA} = I_E$$

$$I_C = I_E = 0.965 \text{ mA}$$

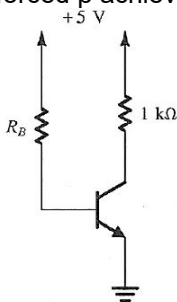Q5. For the circuit shown, design a value for R_B so

that the transistor saturates with an overdrive factor of 10. The BJT is specified to have a minimum β of 20 and $V_{CEsat} = 0.2 \text{ V}$. What is the value of forced β achieved?



Solution:

$$I_{C(sat)} = \frac{5 - 0.2}{1} = 4.8 \text{ mA}$$

$$I_{B(EOS)} = \frac{I_{C(sat)}}{\beta_{min}} = \frac{4.8}{20} = 0.24 \text{ mA}$$


$$I_B = I_{B(EOS)} \times ODF = 2.4 \text{ mA}$$

$$I_B = \frac{5 - 0.7}{R_B} \rightarrow R_B = \frac{4.3}{2.4} = 1.792 \text{ k}\Omega$$

$$\beta_{forced} = \frac{I_{C(sat)}}{I_B} = \frac{4.8 \text{ mA}}{2.4 \text{ mA}} = 2;$$

$$\beta_{forced} = 2$$

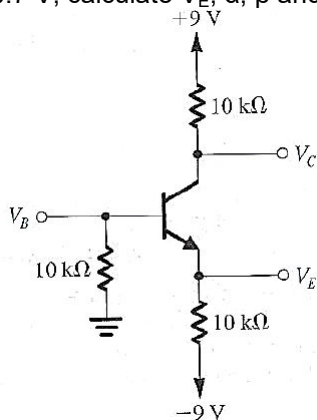Q6. For the circuit shown, $V_B = -1.5 \text{ V}$. Assuming $V_{BE} = 0.7 \text{ V}$, calculate V_E , α , β and V_C .



Solution:

$$I_B = \frac{0 - (-1.5)}{10} = 0.15 \text{ mA}$$

$$V_E = V_B - 0.7 = -1.5 - 0.7 = -2.2 \text{ V}$$

$$I_E = \frac{V_E - (-9)}{10} = \frac{-2.2 + 9}{10} = \frac{6.8}{10} = 0.68 \text{ mA}$$

$$I_C = I_E - I_B = 0.68 - 0.15 = 0.53 \text{ mA}$$

$$V_C = 9 - 0.53 \times 10 = 3.7 \text{ V}$$

$$V_{BC} = -1.5 - 3.7 = -5.2 \text{ V} \leq 0.4 \text{ V}$$

which means the transistor is in the active mode.




$$\beta = \frac{I_C}{I_B} = \frac{0.53}{0.15} = 3.5333$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{3.5333}{4.5333} = 0.7794 = \frac{I_C}{I_E}$$


Q7. A transistor with $\beta = 120$ is biased to operate at a DC collector current of 1.2mA. Find the values of g_m , r_{π} , and r_e .

Solution:

$$g_m = \frac{I_C}{V_T} = \frac{1.2}{25} = 0.048 \Omega^{-1}$$

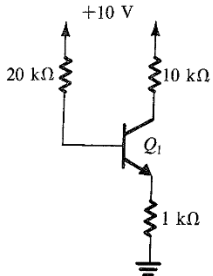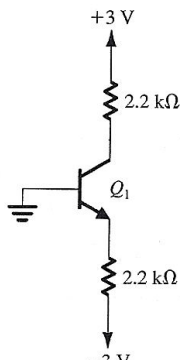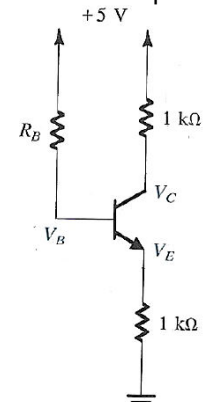	$r_{\pi} = \frac{\beta}{g_m} = \frac{120}{0.048} = 2500 \Omega$ $r_e = \frac{\alpha}{g_m} = \frac{\beta}{\beta + 1} \frac{1}{g_m} = \frac{120}{121} \frac{1}{0.048} = 20.7 \Omega$
<p>Q8. Find the collector voltage in the circuit shown below. Also, calculate forced β for the transistor. Assume the transistor is operating in saturation.</p> 	<p>Solution:</p> $\beta_{\text{forced}} = \frac{I_C}{I_B}$ $= \frac{\frac{V_{CC} - V_C}{R_C}}{\frac{V_{CC} - V_C - V_{BE}}{R_B}}$ $= \frac{\frac{10 - 1.46}{10}}{\frac{10 - 1.46 - 0.5}{20}} = 2.12$
<p>Q9. Consider the circuit shown below. Find the emitter, base and collector voltages and currents. Use $\beta=50$, but assume $V_{BE} = 0.8 \text{ V}$ independent of current level.</p> 	<p>Solution:</p> <p>Assuming the transistor is in active mode:</p> $V_E = -0.8 \rightarrow I_E = \frac{-0.8 - (-3)}{2.2} = \frac{2.2}{2.2} = 1 \text{ mA}$ $I_B = \frac{I_E}{\beta + 1} = \frac{1}{51} = 19.61 \times 10^{-3} \text{ mA}$ $I_C = \beta I_B = 50 \times 19.61 \times 10^{-3} = 0.980 \text{ mA}$ $V_B = 0$ $V_C = 3 - 2.2 \times 0.980 = 0.844 \text{ V}$ $V_{BC} = 0 - (0.844) = -0.844 \leq 0.4 \rightarrow \text{the CBJ is reverse-biased} \rightarrow \text{the transistor is in active mode as assumed!}$
<p>Q10. For the circuit shown below, find V_B, V_E and V_C for $R_B = 100 \Omega \text{ k}$. Let $\beta=100$.</p> 	<p>Solution:</p> $R_B = 100 \text{ k}\Omega$ <p>Assuming the transistor is in active mode:</p> $(\beta + 1)I_B = I_E$ $101 \times \frac{5 - (0.7 + V_E)}{100} = \frac{V_E}{1} \rightarrow 4.3 - V_E = \frac{100}{101} V_E$ $\rightarrow V_E = 2.16 \text{ V} \rightarrow I_E = \frac{2.16}{1} = 2.16 \text{ mA}$ $V_B = V_E + 0.7 = 2.16 + 0.7 = 2.86 \text{ V}$ $V_C = 5 - 1 \times I_C = 5 - \left(\frac{100}{101}\right) \times I_E = 2.86 \text{ V}$ $V_{BC} = V_B - V_C = 0 \leq 0.4 \text{ V}$ <p>the BJT is in active mode as assumed.</p>

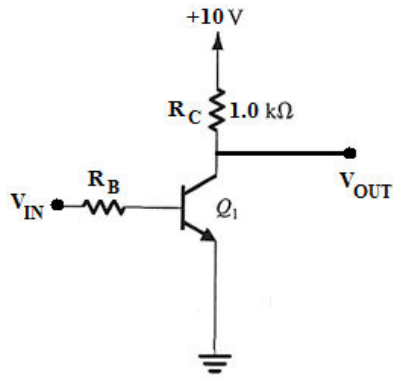- Q11. (a) For the transistor circuit shown, what is V_{CE} when $V_{IN} = 0V$?
 (b) What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Neglect $V_{CE(sat)}$.
 (c) Calculate the maximum value of R_B when $V_{IN} = 5V$.



Solution:

- (a) When $V_{IN} = 0V$,
 the transistor is in cutoff

$$V_{CE} = V_{CC} = 10V = V_{CE(cutoff)}$$

- (b) Since $V_{CE(sat)}$ is neglected

$$I_{C(sat)} = \frac{V_{CC}}{R_C} = \frac{10V}{1.0K\Omega} = 10mA$$

$$I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}} = \frac{10mA}{200} = 50\mu A$$


- (c) When the transistor is on.

$$V_{BE} \cong 0.7V$$

$$V_{R_B} = V_{IN} - V_{BE} = 5 - 0.7V = 4.3V$$


$$R_{B(max)} = \frac{V_{R_B}}{I_{B(min)}} = \frac{4.3}{50\mu A} = 86K\Omega$$

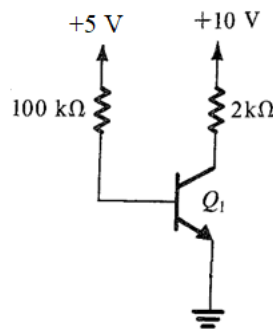- Q12. Determine the voltage at all nodes and current through the branches. Assume $\beta=100$.



Refer lecture notes

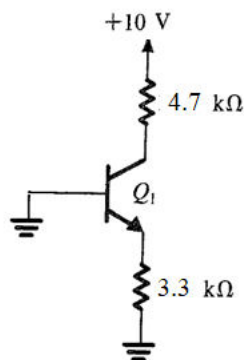- Q13. Determine the voltage at all nodes and current through the branches. Assume $\beta=100$.



Refer lecture notes