
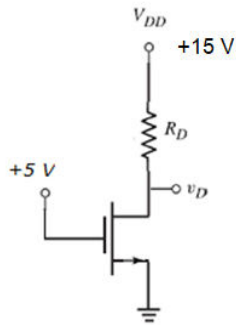


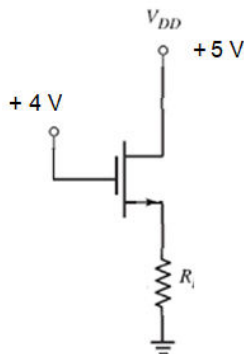
Q1. For the circuit shown, find i_D and v_{DS} . For the NMOS, $V_t = 1\text{ V}$ and $K_n = 0.5\text{ mA/V}^2$. Consider $R_D = 1\text{ k}\Omega$




Q2. Design the circuit so that $i_D = 1\text{ mA}$ and $v_{DS} = 2.5\text{ V}$. The NMOS has $V_t = 1\text{ V}$. Find k_n .



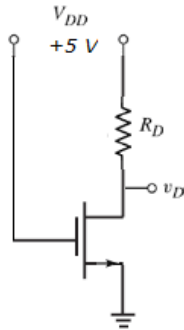
Q3. Design the circuit to establish a drain voltage of 0.2 V . What is the effective operating resistance between drain and source at this Q-point? Take $V_t = 1\text{ V}$ and $k(W/L) = 2\text{ mA/V}^2$.



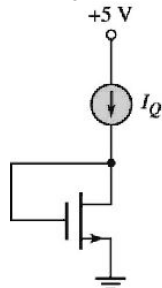
Q4. The parameters for the transistor below are $k_n = 0.5\text{ mA/V}^2$, $W/L=1$, $V_{tn} = 1.2\text{ V}$, and $\lambda = 0$. Determine V_{DS} and V_{GS} for $I_D = 1\text{ mA}$.



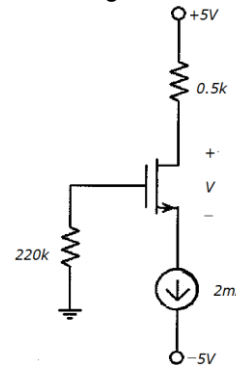Q5. The N-channel enhancement mode MOSFET in this circuit has the following parameters: $K_n'(W/L) = 2\text{ mA/V}^2$, $V_{tn}=1\text{V}$, and $\lambda = 0$. Determine the voltage V as shown.



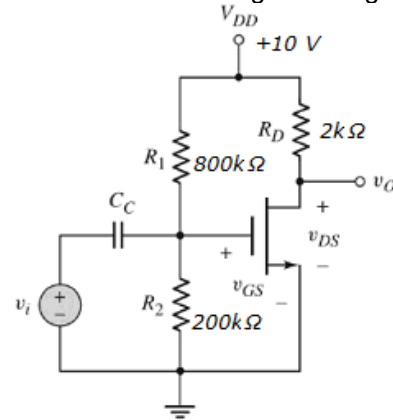Q6. The n-channel MOSFET in this circuit has $K_n'(W/L) = 2\text{ mA/V}^2$ and $V_{tn}=1\text{V}$. Neglect λ .
 a) Determine the dc operating point.
 b) Draw the small signal model for the circuit.
 c) Determine the small-signal voltage gain.



Q7. The parameters of the circuit shown below are $V_{DD} = 5\text{ V}$, $R_1 = 520\text{ k}\Omega$, $R_2 = 320\text{ k}\Omega$, $R_D = 10\text{ k}\Omega$, and $R_{Sig} = 0$. Assume transistor parameters $V_{tn} = 0.8\text{V}$, $K_n = 0.20\text{ mA/V}^2$, and $\lambda = 0$.
 (a) Determine the small-signal parameters g_m and r_o .
 (b) Find the small-signal voltage gain v_o/v_i .

