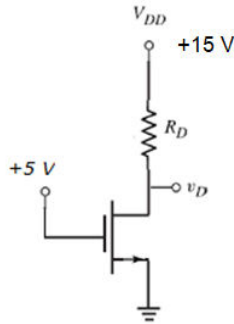


Q1. For the circuit shown, find i_D and v_{DS} . For the NMOS, $V_t = 1\text{ V}$ and $K_n = 0.5\text{ mA/V}^2$. Consider $R_D = 1\text{ k}\Omega$



Solution:


$V_{GS} = 5\text{ V} > V_t$
Assume the transistor is in saturation.

$$i_D = \frac{1}{2}K_n(V_{GS} - V_t)^2$$

$$= 0.25 \times (5 - 1)^2 = 4\text{ mA}$$

$$V_{DS} = V_{DD} - i_D R_D = 11\text{ V}$$

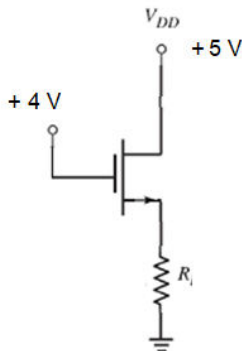Q2. Design the circuit so that $i_D = 1\text{ mA}$ and $v_{DS} = 2.5\text{ V}$. The NMOS has $V_t = 1\text{ V}$. Find k_n .



Solution:

$$v_{RS} = V_{DD} - v_{DS} = 2.5\text{ V}$$

$$R_S = (2.5\text{ V}) / (1\text{ mA}) = 2.5\text{ k}\Omega.$$


$$V_{GS} = V_G - v_{RS} = 4\text{ V} - 2.5\text{ V} = 1.5\text{ V}.$$

$V_{DS} > V_{GS}$ NMOS will be operating in saturation

$$i_D = \frac{1}{2}K_n(V_{GS} - V_t)^2$$

$$K_n = 8\text{ mA/V}^2$$

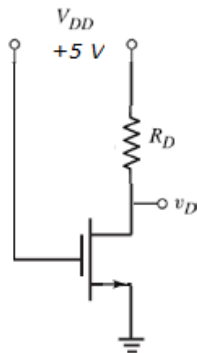Q3. Design the circuit to establish a drain voltage of 0.2 V . What is the effective operating resistance between drain and source at this Q-point? Take $V_t = 1\text{ V}$ and $k(W/L) = 2\text{ mA/V}^2$.



Solution:

$V_D < V_G$ by 4.8V so MOS operates in triode region.

$$I_D = \frac{1}{2}k'_n(W/L)[(V_{GS} - V_T)V_{DS} - V_{DS}^2/2]$$

$$= \frac{1}{2} \times 2 \times 10^{-3} [(5 - 1)0.2 - 0.2^2/2]$$

$$= 0.7\text{ mA}$$


$$R_D = V_{DD} - V_D / I_D$$

$$= 5 - 0.2 / 0.7\text{m} = 4.71\text{ k}\Omega$$

$$r_{DS} = V_{DS} / I_D$$

$$= 0.2 / 0.7\text{m} = 285.71\Omega$$

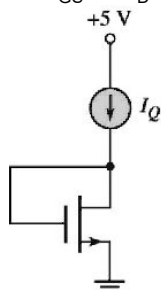Q4. The parameters for the transistor below are $k_n = 0.5\text{ mA/V}^2$, $W/L=1$, $V_{tn} = 1.2\text{ V}$, and $\lambda = 0$. Determine V_{DS} and V_{GS} for $I_D = 1\text{ mA}$.



Solution:


$$I_D = \frac{1}{2}k_n(V_{GS} - V_T)^2$$

$$1 \times 10^{-3} = 0.5 \times 10^{-3} (V_{GS} - 1.2)^2$$

$$V_{GS} = 3.2\text{ V} \text{ or } V_{GS} = -0.8\text{ V}$$

$$V_{DS} = V_{GS} = 3.2\text{ V}$$

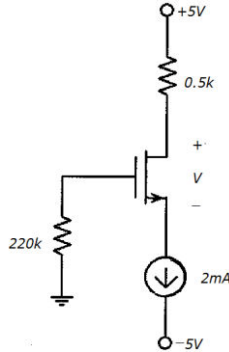Q5. The N-channel enhancement mode MOSFET in this circuit has the following parameters: $K_n'(W/L) = 2\text{mA/V}^2$, $V_{tn} = 1\text{V}$, and $\lambda = 0$. Determine the voltage V as shown.



Solution:

$$I_D = \frac{1}{2}K_n(V_{GS} - V_T)^2$$

$$2 \times 10^{-3} = \frac{1}{2} \times 2 \times 10^{-3} (V_{GS} - 1)^2$$

$$V_{GS} = 2.414 \text{ V}$$


$$V_S = -2.414 \text{ V}$$

$$V_D = 5 - 2\text{mA} \times 0.5\text{k} = 4 \text{ V}$$

$$V_{DS} = V_D - V_S = 4 - (-2.414) = 6.414 \text{ V}$$

V = 6.414 V

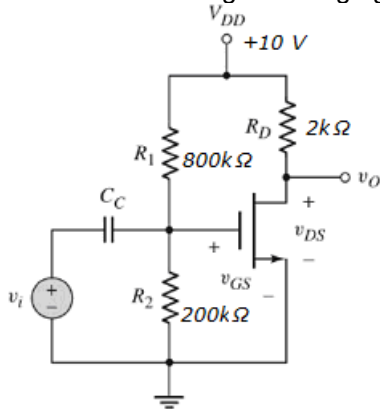
Q6. The n-channel MOSFET in this circuit has $K_n'(W/L) = 2\text{mA/V}^2$ and $V_{tn} = 1\text{V}$. Neglect λ .
 a) Determine the dc operating point.
 b) Draw the small signal model for the circuit.
 c) Determine the small-signal voltage gain.



Solution:


(a) $V_{GS} = 2\text{V}$
 $I_D = 1 \text{ mA}$, $V_{DS} = 8 \text{ V}$
 MOS is in saturation region

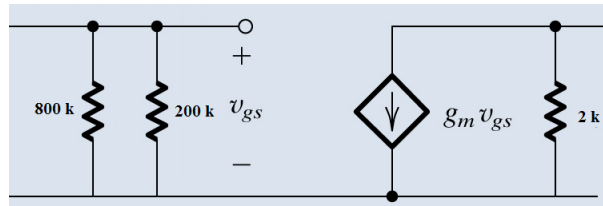(b) $g_m = 2I_D/V_{ov} = 2/1 = 2 \text{ mA/V}$



(c) Voltage gain = $-g_m R_D = -2 \text{ mA} \times 2 \text{ k} = -4 \text{ V/V}$

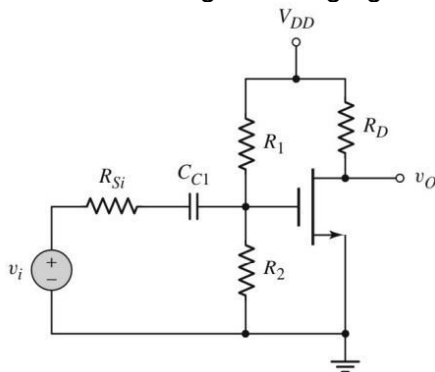Q7. The parameters of the circuit shown below are $V_{DD} = 5 \text{ V}$, $R_1 = 520 \text{ k}\Omega$, $R_2 = 320 \text{ k}\Omega$, $R_D = 10 \text{ k}\Omega$, and $R_{Sig} = 0$. Assume transistor parameters $V_{tn} = 0.8\text{V}$, $K_n = 0.20 \text{ mA/V}^2$, and $\lambda = 0$.
 (a) Determine the small-signal parameters g_m and r_o .
 (b) Find the small-signal voltage gain v_o/v_i .



Solution:

(a) $V_{GS} = \left(\frac{R_2}{R_1 + R_2}\right)V_{DD} = \left(\frac{320}{520 + 320}\right)(5) = 1.905 \text{ V}$
 $I_{DQ} = 0.20(1.905 - 0.8)^2 = 0.244 \text{ mA}$
 $g_m = 2\sqrt{K_n I_{DQ}} = 2\sqrt{(0.2)(0.244)} = 0.442 \text{ mA/V}$
 $r_o = \infty$

(b) $A_v = -g_m R_D = -(0.442)(10) = -4.42$