

Exp. No.

Date:

## APPLICATIONS OF DIODES

### OBJECTIVE

The purpose of the experiment is to

- (i) experiment the use of diodes in limiting, clamping and rectifying circuits.
- (ii) analyze the use of diodes in clipping circuits and to measure the voltage limits of both biased and unbiased clipping circuits.
- (iii) study the characteristics of bridge rectifier and to examine the operation of Zener diode as shunt voltage regulator.

### EQUIPMENT AND COMPONENTS USED

30 MHz Dual Channel Digital Storage Oscilloscope (DSO)  
 3 MHz Function Generator  
 0-30 V dc dual regulated power supply  
 1N4007 Diode  
 1Z5V6 Zener Diode  
 Resistor 220  $\Omega$ , 1 k $\Omega$ , 1/4W  
 Electrolytic Capacitor 10 $\mu$ F/25V, 100 $\mu$ F/63V  
 Breadboard, Connecting wires, BNC Cables and Probes

### PRE-LAB

1. Read the specifications of the following diodes from its datasheet:

**Device Part Number: 1N4001**

**Device Manufacturer:** \_\_\_\_\_

**Description:** \_\_\_\_\_

Peak Repetitive Reverse Voltage,  $V_{RRM}$  =

Average Rectified Forward Current,  $I_{F(av)}$  =

Maximum RMS Voltage,  $V_{RMS}$  =

DC Reverse Voltage,  $V_R$  =

Maximum reverse current  $I_{RM}$  =

Maximum instantaneous forward voltage drop  $V_F$  =

**Device Part Number: 1N4007**

**Device Manufacturer:** \_\_\_\_\_

**Description:** \_\_\_\_\_

Peak Repetitive Reverse Voltage,  $V_{RRM}$  =

Average Rectified Forward Current,  $I_{F(av)}$  =

Maximum RMS Voltage,  $V_{RMS}$  =

DC Reverse Voltage,  $V_R$  =

Maximum reverse current  $I_{RM}$  =

Maximum instantaneous forward voltage drop  $V_F$  =

2. Read the specifications of 1Z5V6 Zener diode from its datasheet.

**Device Part Number: 1Z5V6**

**Device Manufacturer:** \_\_\_\_\_

Nominal Zener voltage,  $V_Z =$

Zener test current,  $I_{ZT} =$

Maximum Zener impedance,  $Z_{ZT} @ I_{ZT} =$

$Z_{ZK} @ I_{ZK} =$

Zener Knee current  $I_{ZK} =$

Power dissipation,  $P_D =$

**PRACTICE PROCEDURE**

**1. Unbiased Clippers**

1. Connect the circuit as shown in Figure 1.
2. Apply sine wave of 10Vp-p, 1 kHz from function generator.
3. Observe the input, output waveforms and its transfer characteristics on DSO screen.

Repeat the above steps for Figure 2, Figure 3 and Figure 4.

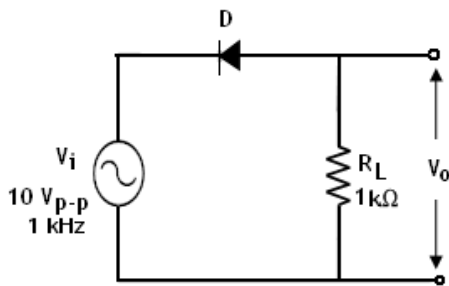


Figure 1: Unbiased Series Positive Clipper


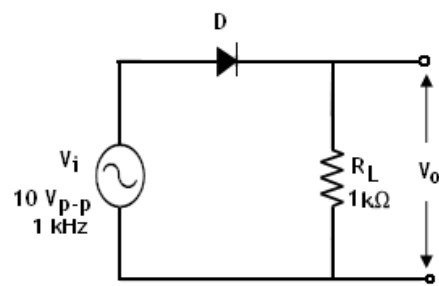


Figure 2: Unbiased Series Negative Clipper

**Observations**

Volt/div =


Time/div =

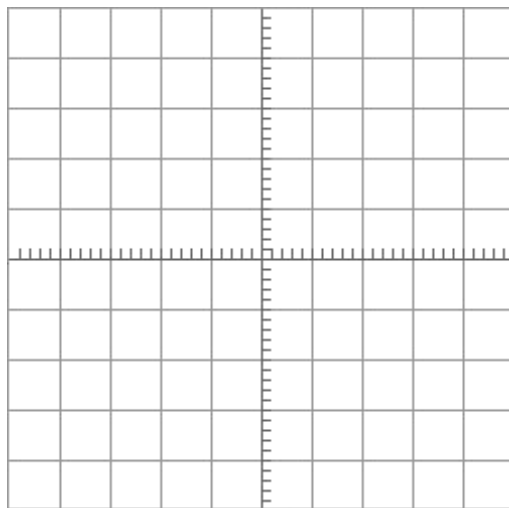

Output waveform

Volt/div =

Time/div =

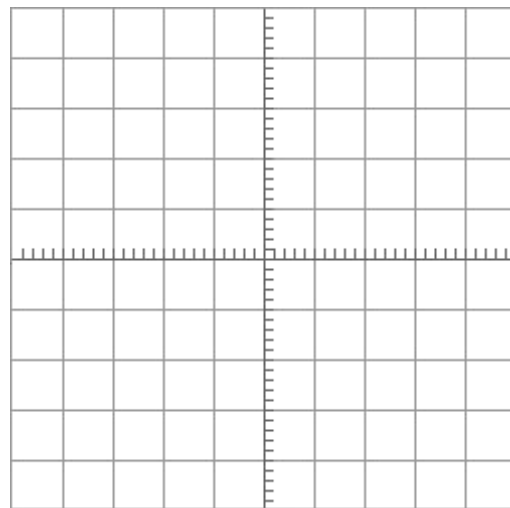

Output waveform

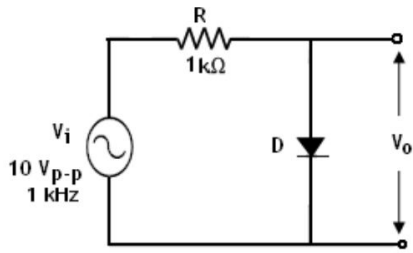


Figure 3: Unbiased Shunt Positive Clipper


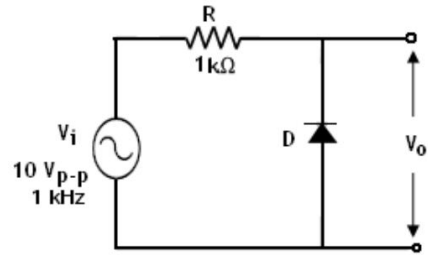


Figure 4: Unbiased Shunt Negative Clipper

**Observations**

Volt/div =


Time/div =

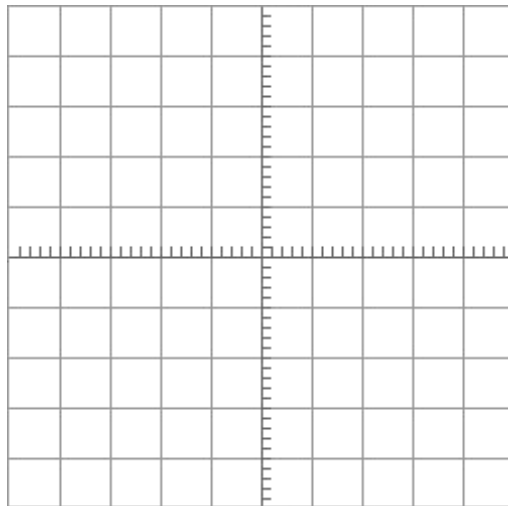

Output waveform

Volt/div =

Time/div =

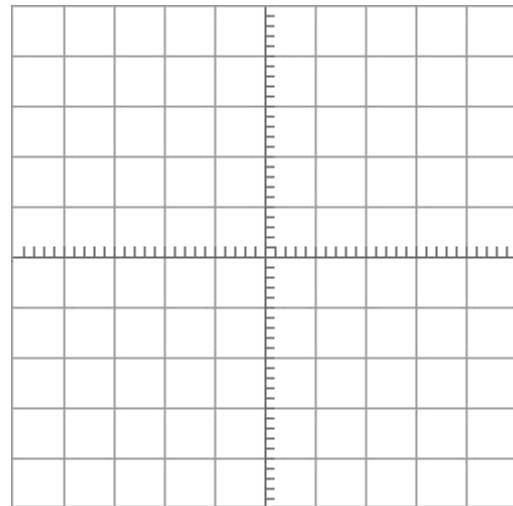

Output waveform

**INFERENCE**

---



---



---



---



---



---



---



---

**2. Biased Clippers**

1. Connect the circuit as shown in Figure 5.
  2. Apply sine wave of 10Vp-p, 1 kHz from function generator and 2 V dc from regulated power supply.
  3. Observe the input, output waveforms and its transfer characteristics on DSO screen.
- Repeat the above steps for Figure 6.

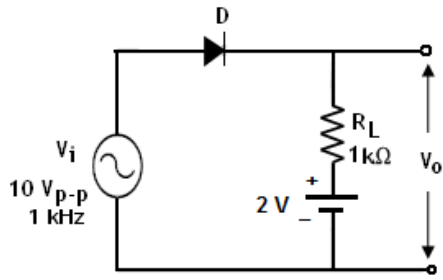


Figure 5: Biased Series Negative Clipper


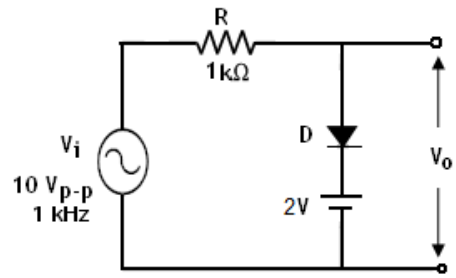
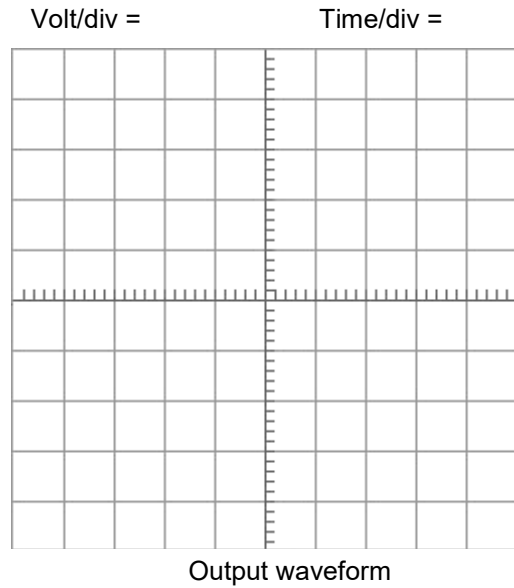


Figure 6: Biased Shunt Positive Clipper

**Observations**

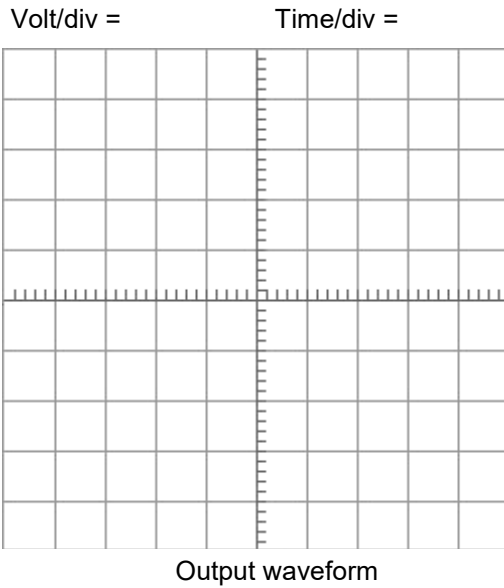

**INFERENCE**

---



---



---



---



---



---



---



---

**3. Clampers and Voltage multipliers**

1. Connect the circuit as shown in Figure 7 and Figure 8.
2. Apply sine wave of 10Vp-p, 1 kHz from function generator.
3. Observe the input and output waveforms on DSO screen.
4. Measure the peak value of the output signal.

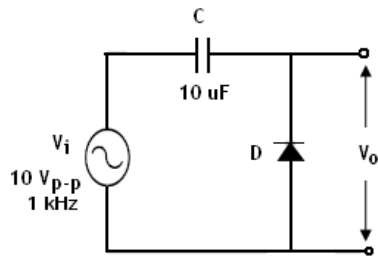


Figure 7: Unbiased Positive Clamper


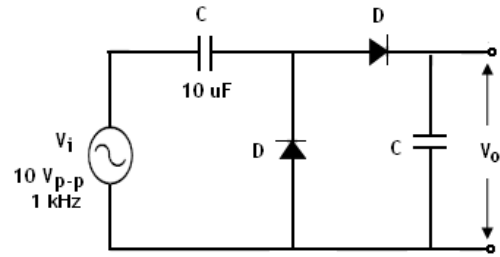
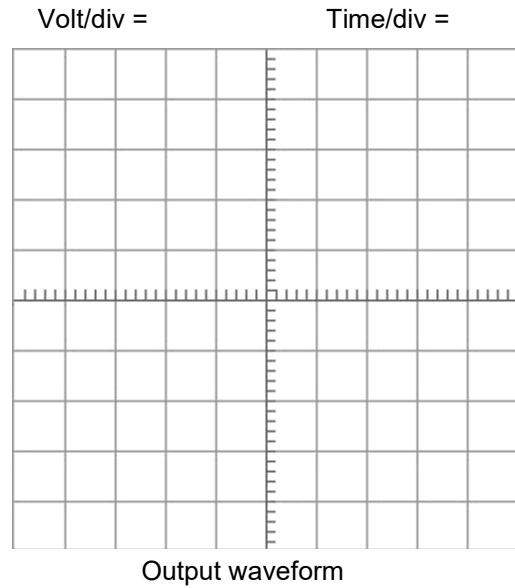


Figure 8: Voltage doubler

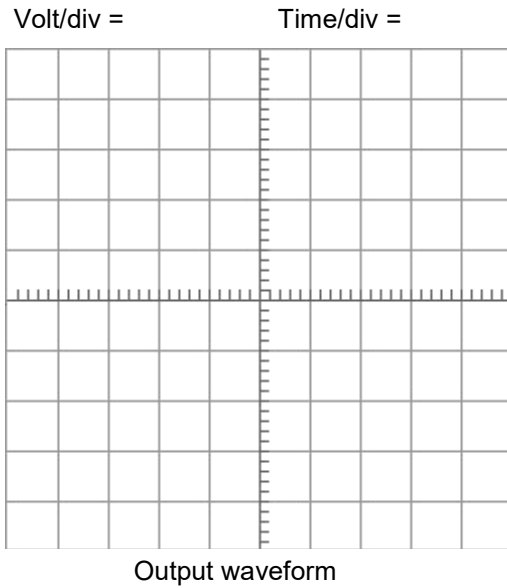

**Inference**

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

#### 4. Bridge rectifiers

1. Connect the circuit as shown in Figure 9 without capacitor.
2. Apply sine wave of 20Vp-p, 50 Hz from function generator.
3. Observe the input and output waveforms on DSO screen.
4. Measure the peak value of output  $V_m$  and calculate  $V_{rms}$  and  $V_{dc}$ . Note:  $V_{rms} = V_m/\sqrt{2}$ ,  $V_{dc} = 2V_m/\pi$ .
5. Connect the capacitor filter and observe the output. Measure the peak value of output  $V_m$  and peak to peak ripple voltage  $V_{rpp}$ .

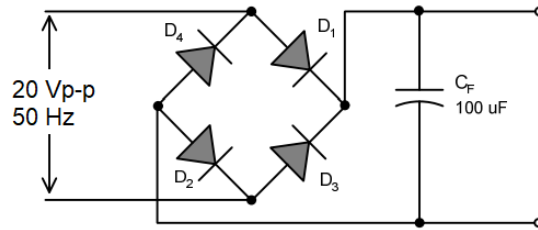


Figure 9: Bridge Rectifier

#### Observations

	Bridge Rectifier Without filter
$V_m$	
$V_{rms} = V_m/\sqrt{2}$	
$V_{dc} = 2V_m/\pi$	
Ripple factor, $r$ $r = \sqrt{(V_{rms}/V_{dc})^2 - 1}$	

	Bridge Rectifier With filter
$V_m$	
$V_{rpp}$	
$V_{r,rms} = V_{rpp}/2\sqrt{3}$	
$V_{dc} = V_m - V_{rpp}/2$	
Ripple factor, $r$ $r = V_{r,rms} / V_{dc}$	

#### Inference

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

---

### 5. Bridge rectifiers with Zener regulators

1. Connect the circuit as shown in Figure 10 without load resistor.
2. Observe the output waveforms on DSO screen. Compare with the waveforms obtained for rectifiers with filter.
3. Measure the no load voltage,  $V_{NL}$ .
4. Connect  $220\ \Omega$  resistor as  $R_L$  and measure the full load voltage,  $V_{FL}$ .
5. Calculate the percentage regulation. Note:  $\% \text{ regulation} = (V_{NL} - V_{FL})/V_{FL} \times 100$ .

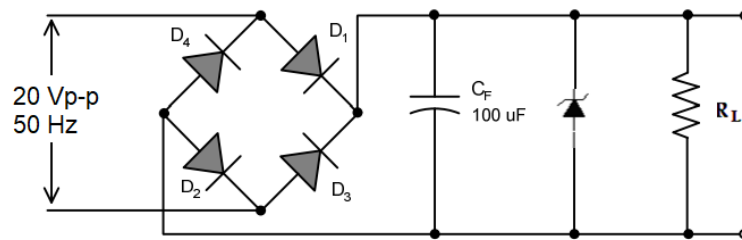


Figure 10: Bridge Rectifier with Zener regulator

#### Observations

$V_{NL} =$

$V_{FL} =$

#### Inference

---



---



---



---



---



---



---



---



---



---



---



---



---



---



---



---

**RESULTS AND CONCLUSION**

Prepared by:

Name: \_\_\_\_\_

Reg. No.: \_\_\_\_\_

Date of Experiment: .....

**ASSESSMENT**

Date of Report Submission: .....

Signature

Student Task	Max. Marks	Graded Marks
Pre-lab Preparation	10	
Results & Inference	10	
Post-lab / Viva-voce	10	
Total	30	