

Exp. No.

Date:

FREQUENCY RESPONSE OF COMMON SOURCE AMPLIFIER

OBJECTIVE

The purpose of the experiment is to

- # design a single stage MOSFET common source (CS) amplifier with voltage divider biasing
- # analyze and plot the frequency response of the amplifier with and without capacitor bypassed source resistance, also to compare the bandwidth of the amplifier with and without feedback.

EQUIPMENT AND COMPONENTS USED

30 MHz Dual Channel Cathode Ray Oscilloscope
 3 MHz Function Generator
 0-30 V dc regulated power supply
 4 ½ digit Digital Multimeter
 MOSFET 2N7000
 Resistors ¼W
 Electrolytic Capacitors
 Breadboard and Connecting wires
 BNC Cables and Probes

PRE-LAB

1. Read the specifications of 2N7000 transistor from its datasheet.

Device Part Number: 2N7000

Device Manufacturer: _____

Drain – source voltage, $V_{DS} =$

Gate-source voltage, $V_{GS} =$

Drain Current, $I_D =$

Gate Threshold Voltage, $V_{GS(th)} =$

Drain–Source Breakdown Voltage, $V_{(BR)DSS} =$

Static Drain–Source On Resistance, $r_{DS(ON)} =$

2. Design a common source amplifier as per the design requirements given. With standard value of resistors, determine the dc operating conditions.

3. Comment on the mid-band gain and bandwidth of the CS amplifier with and without capacitor bypassed source resistance.

CIRCUIT DIAGRAM

 


Figure1. Common Source Amplifier

DESIGN

Output requirements: Mid-band voltage gain of the amplifier, $A_V = 50$ V/V

Select the MOSFET as 2N7000.

DC biasing conditions

$$V_{DD} = 12 \text{ V}, I_D = 5 \text{ mA}$$

$$V_{RD} = 45\% \text{ of } V_{DD} =$$

$$V_{RS} = 10\% \text{ of } V_{DD} =$$

$$V_{DS} = 45\% \text{ of } V_{DD} =$$

Design of Drain resistor R_D

$$V_{RD} = I_D \times R_D$$

$$\Rightarrow R_D =$$

Design of Source resistor R_S

$$V_{RS} = I_D \times R_S, \text{ here } I_S = I_D$$

$$\Rightarrow R_S =$$

Design of voltage divider R_1 and R_2

Take $V_{GS} = 2.5$ V (above V_t , in saturation region)

$$V_{GS} = V_G - V_S \Rightarrow V_G = V_{GS} + V_S =$$

Use large value for R_1 to ensure zero gate current. Take $R_1 = 240$ k Ω

$$V_{R2} = V_G = V_{DD} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$\text{Then } R_2 =$$

Design of Load Resistor, R_L

$$A_V = g_m(R_D || R_L)$$

$$\text{Take } g_m = 50 \text{ mS}, R_L =$$

Design of blocking capacitors C_{C1} and C_{C2}

Impedance of the coupling capacitor $X_C \leq R_G/10$

$$\text{Using } f_L = 100 \text{ Hz}, C_{C1} \geq 1/(2\pi f \times X_{C1}) =$$

$$C_{C1} = C_{C2} =$$

Design of bypass capacitor

Take $X_{CS} \leq R_S/10$ at 100Hz to bypass this frequency

$$C_S \geq 1/2\pi \times 100 \times X_{CS}$$

$$C_S =$$

PRACTICE PROCEDURE**DC Operating Point**

1. Connect the voltage divider bias network from the circuit shown in Figure 1.
2. Apply DC bias voltage V_{DD} and measure the operating point quantities: V_{GS} , V_{DS} , I_D .

Table1: Operating Point measurements

| Quantities | Designed Value | Measured Value |
|--------------------------------|----------------|----------------|
| Gate-source Voltage, V_{GS} | | |
| Drain-Source Voltage, V_{DS} | | |
| Drain Current, I_D | | |

Inference

Amplifier Gain Measurements

1. Connect the circuit as shown in Figure 1.
2. Apply an input sine wave signal of 100mV, 1 kHz from the function generator.
3. Observe the output in CRO. Calculate the corresponding gain.

Table2: Amplifier gain measurements

| | Amplitude (V) | Frequency (kHz) | Voltage gain, A_V (V/V) |
|---|---------------|-----------------|---------------------------|
| Small signal Input voltage, V_s | | | |
| Amplified output voltage, V_o with bypass capacitor | | | |
| Amplified output voltage, V_o without bypass capacitor | | | |

Inference

Frequency Response

1. Keeping the magnitude of the input same, ie.,100mV, vary the frequency of the input signal and tabulate the output voltage for different frequencies.
2. Compute the gain and plot the Frequency versus Gain (dB) using semi-log sheet.
3. From the plot, determine the values of (a) Mid band voltage gain, $A_V(\text{mid})$, (b) Lower cut-off frequency, (c) Upper cut-off frequency and (d) Bandwidth.

Repeat the above by removing the bypass capacitor.

Table3: Frequency response with bypass capacitor

Input voltage, $V_s =$ mV

| Signal frequency (Hz) | Output voltage, V_o (Volts) | Gain = $\frac{V_o}{V_s}$ | $20 \log_{10}(\text{Gain})$ dB |
|-----------------------|-------------------------------|--------------------------|--------------------------------|
| 10 | | | |
| 20 | | | |
| 50 | | | |
| 100 | | | |
| 200 | | | |
| 500 | | | |
| 1k | | | |
| 2k | | | |
| 5k | | | |
| 10k | | | |
| 20k | | | |
| 50k | | | |
| 100k | | | |
| 200k | | | |
| 500k | | | |
| 1M | | | |
| | | | |

Inference

Table4: Frequency response without bypass capacitorinput voltage, $V_s =$ mV

| Signal frequency (Hz) | Output voltage, V_o (volts) | Gain = $\frac{V_o}{V_s}$ | $20 \log_{10}(\text{Gain})$ dB |
|-----------------------|-------------------------------|--------------------------|--------------------------------|
| 10 | | | |
| 20 | | | |
| 50 | | | |
| 100 | | | |
| 200 | | | |
| 500 | | | |
| 1k | | | |
| 2k | | | |
| 5k | | | |
| 10k | | | |
| 20k | | | |
| 50k | | | |
| 100k | | | |
| 200k | | | |
| 500k | | | |
| 1M | | | |
| | | | |

Inference

UNDERSTANDING & LEARNING

RESULTS AND CONCLUSION

Prepared by:
Name: _____

Reg. No.: _____

Date of Experiment:

ASSESSMENT

Date of Report Submission:

| Student Task | Max. Marks | Graded Marks |
|-------------------------------------|------------|--------------|
| Pre-lab Preparation / Conduction | 10 | |
| Results & Inference | 10 | |
| Post-lab / Viva-voce | 10 | |
| Total | 30 | |

Signature