

19EEE114 Electronic Circuits

2nd Semester B.Tech. EEE



PN junction diodes

Biasing

Ideal Characteristics


Diode Current

Characteristics

Temperature Dependence


PN Junction Diode

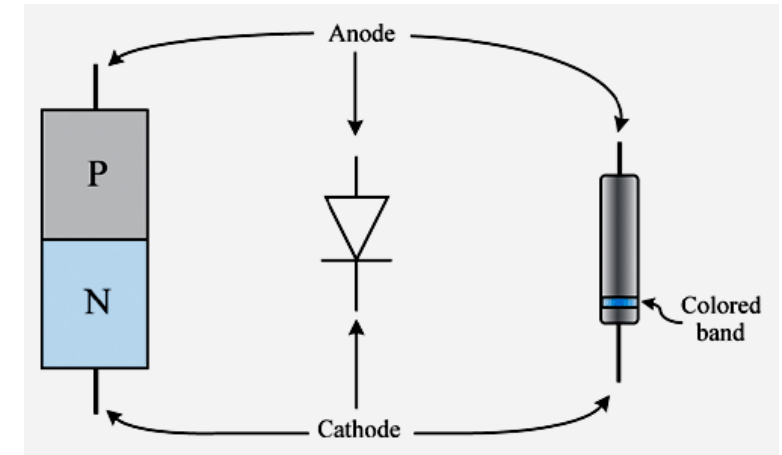- Allows current to flow in one direction but not the other
- The *anode* connects to the p-type material, the *cathode* to the n-type material of the diode.




Forward Biased Diodes

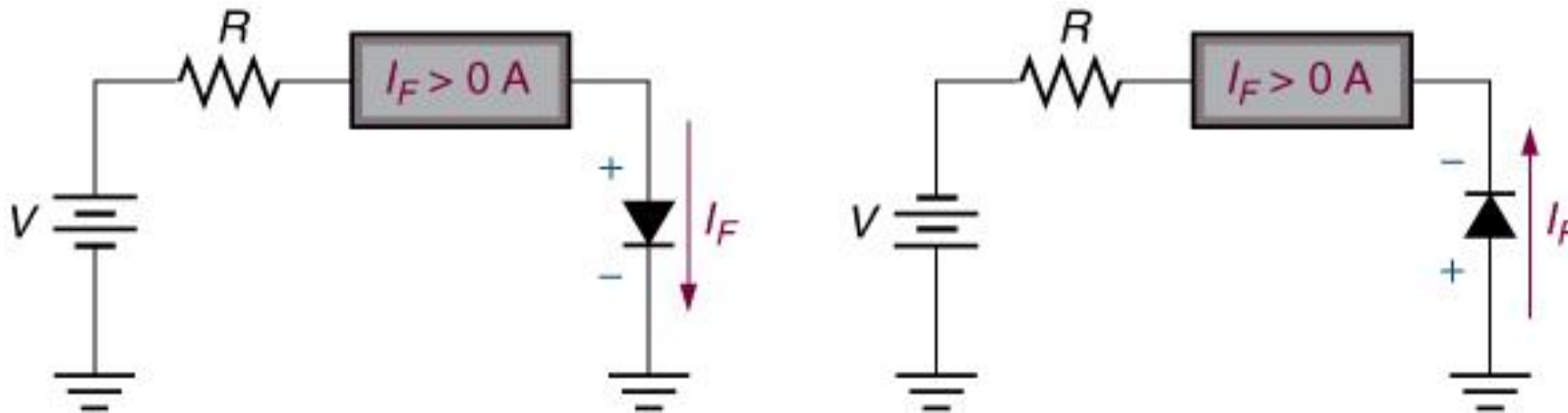- The component is biased so that the anode is more positive than the cathode.
- The diode conducts fully when V_F is approximately 0.7 V (for silicon) or 0.3 V (for germanium).
- The value of I_F depends on the circuit voltage and resistance values.




Reverse Biased Diodes

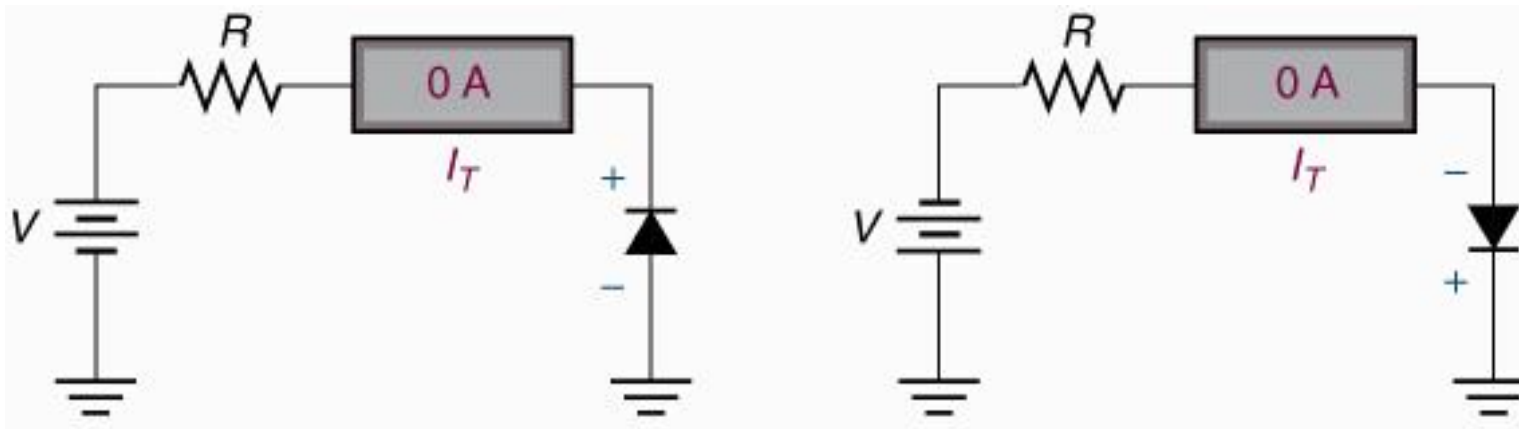- The component is biased so that the cathode is more positive than the anode.
- The voltage across the diode is approximately equal to the applied voltage.
- The diode current is approximately 0 A (as indicated by the ammeter).





Ideal diode characteristics

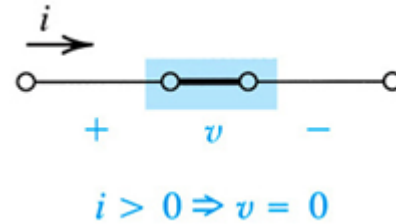
- When **forward biased** (closed switch), the diode:
 - Has no resistance.
 - Does not limit current.
 - Has no voltage drop across its terminals.



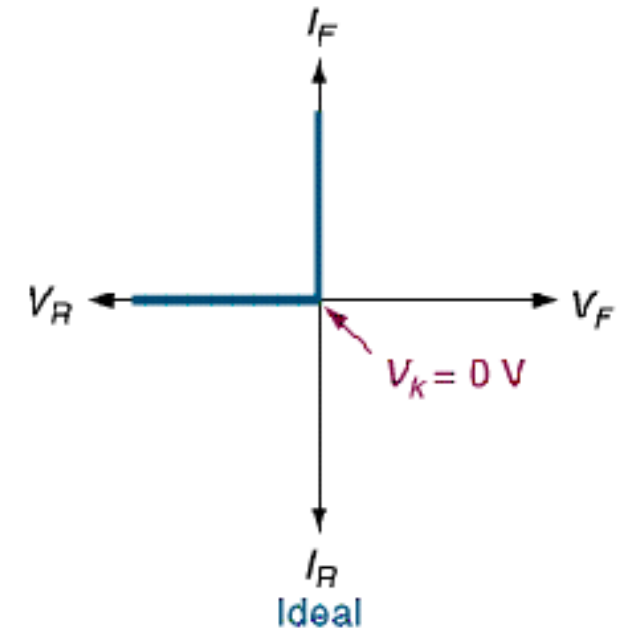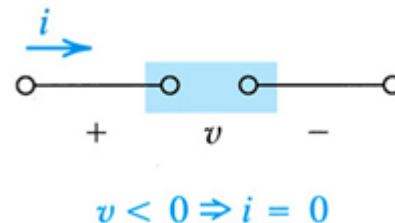
- When **reverse biased** (open switch), the diode:
 - Has infinite resistance.
 - Blocks current.
 - Drops the applied voltage across its terminals.



Current through Ideal diode


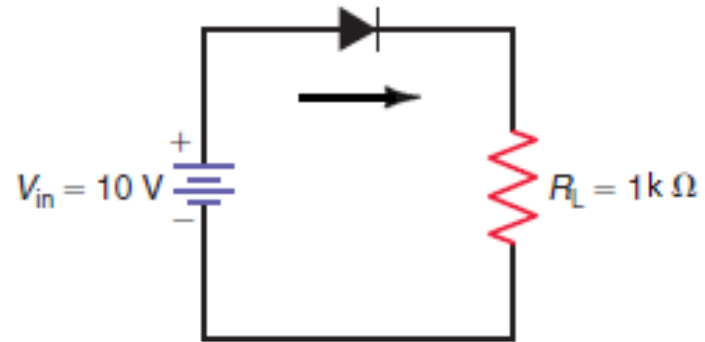


$$I = 10\text{ mA}$$

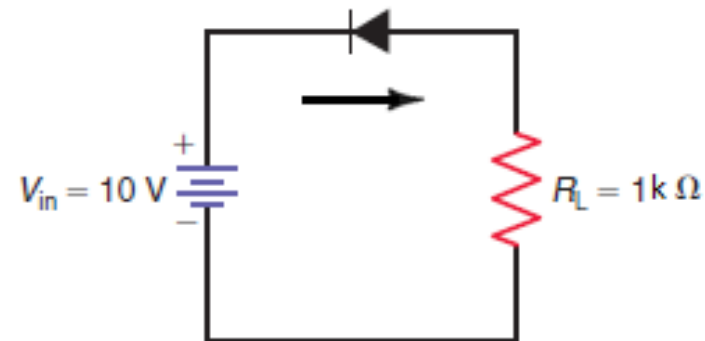


$$I = 0\text{ mA}$$

Circuit Connections

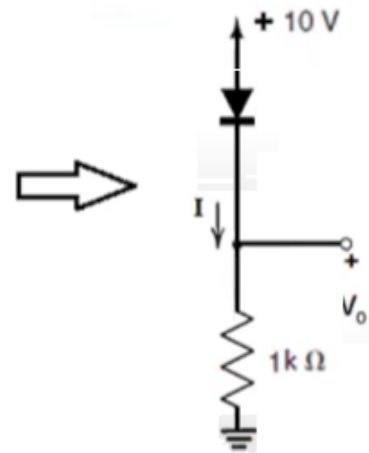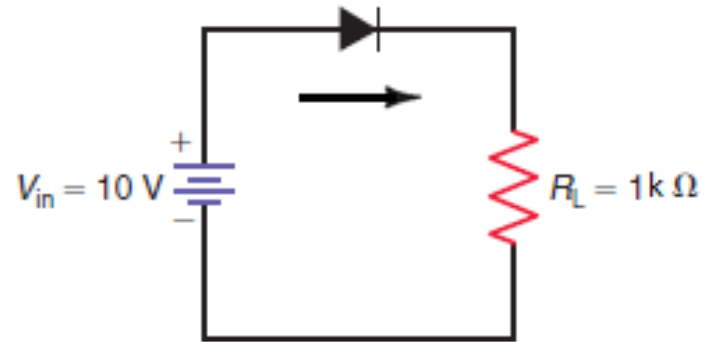


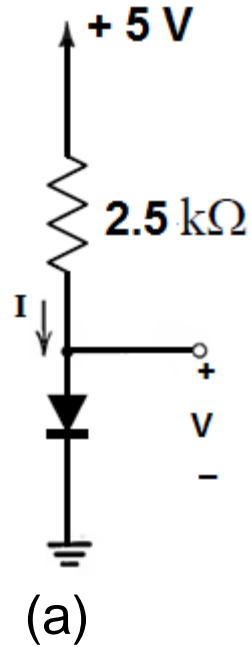Problem #1

Find the values of I and V in the circuits shown below. Assume diodes to be ideal.




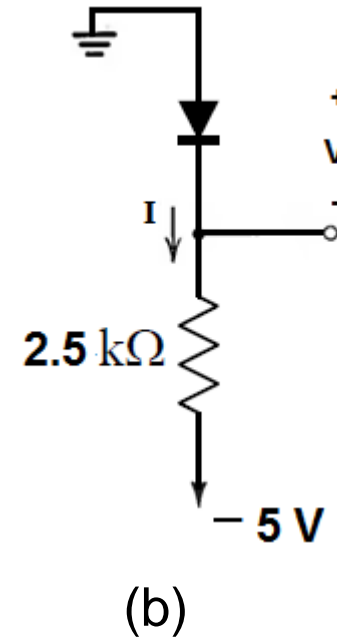Solution: $I = 2\text{ mA}$, $V = 0\text{ V}$



Solution: $I = 2\text{ mA}$, $V = 0\text{ V}$

Characteristics of Junction diode

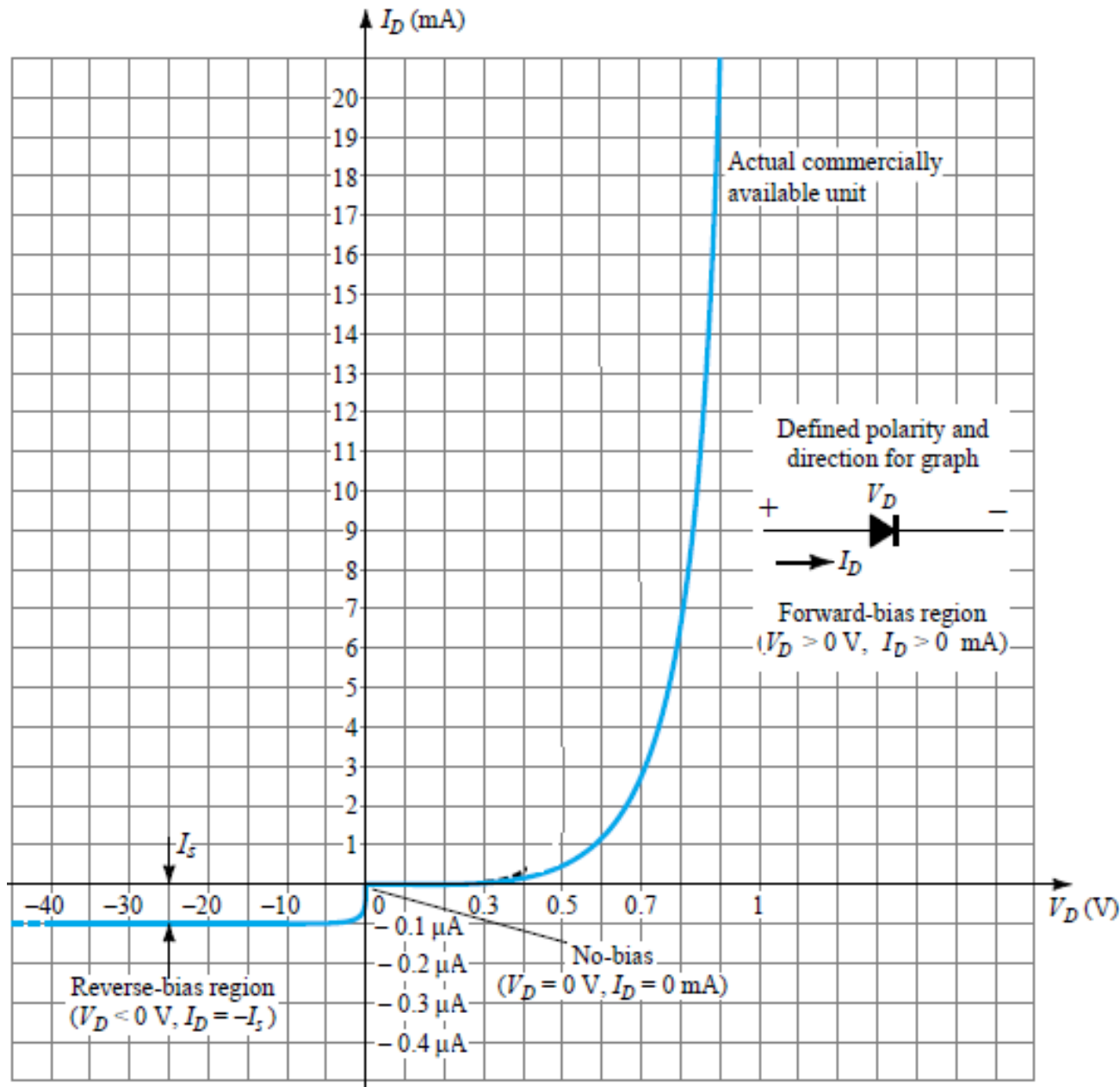

Forward-bias region

Cut-in voltage - below which, minimal current flows

- approximately 0.5V


Fully conducting region – region where R_{diode} is approximately equal zero

– between 0.6 and 0.8 V

Diode current,

$$i = I_S (e^{v/\eta V_T} - 1)$$

Characteristics of Junction diode

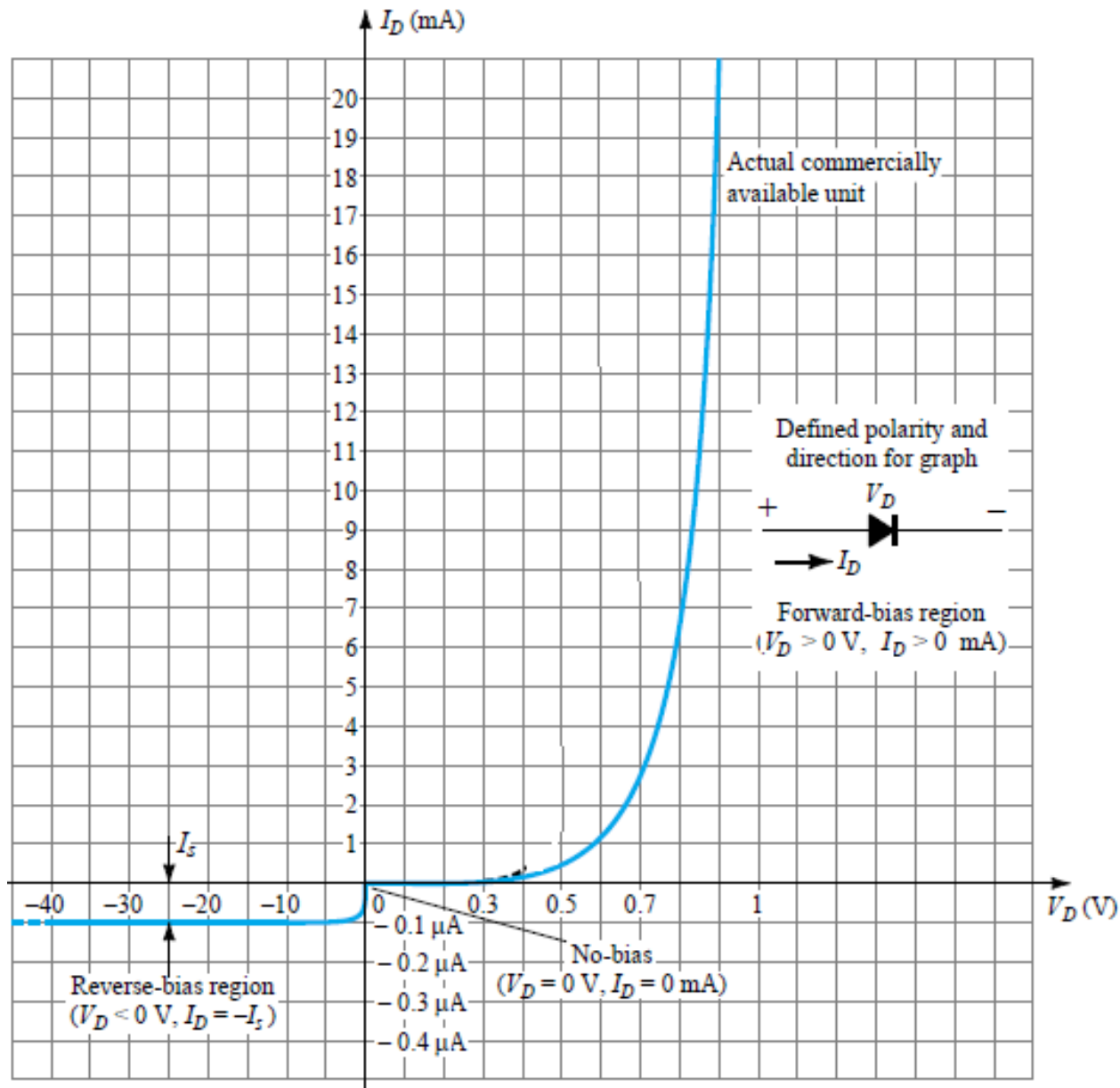

Reverse-bias region

Saturation current- constant current in reverse direction

$$i = -I_S$$


Breakdown – when $V_D \ll 0$

Exponential Model

- most **difficult** to employ in circuit analysis
 - due to nonlinear nature


$$I_D = I_S e^{V_D / V_T}$$

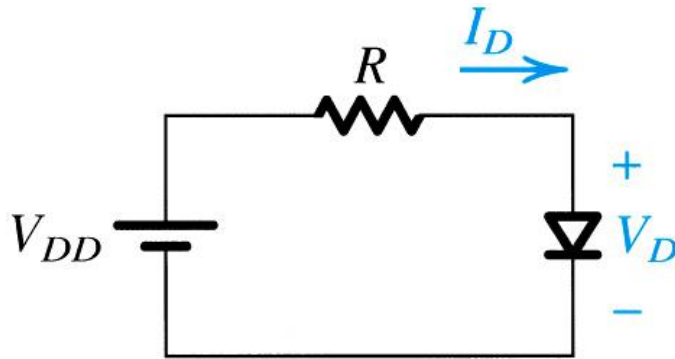V_D = voltage across diode
 I_D = current through diode



- **solve** for I_D in the circuit
 - $V_{DD} = 5\text{ V}$
 - $R = 1\text{ k}\Omega$
 - $I_D = 1\text{ mA}$ @ 0.7 V
- Solution...
 - **graphical method**

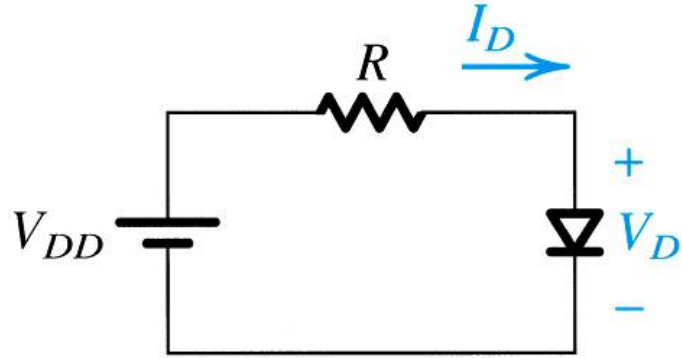Graphical Analysis Using Exponential Model




$$V_{DD} = I_D R + V_D$$


$$I_D = \frac{V_{DD} - V_D}{R}$$

$$V_D = V_{DD} - I_D R$$

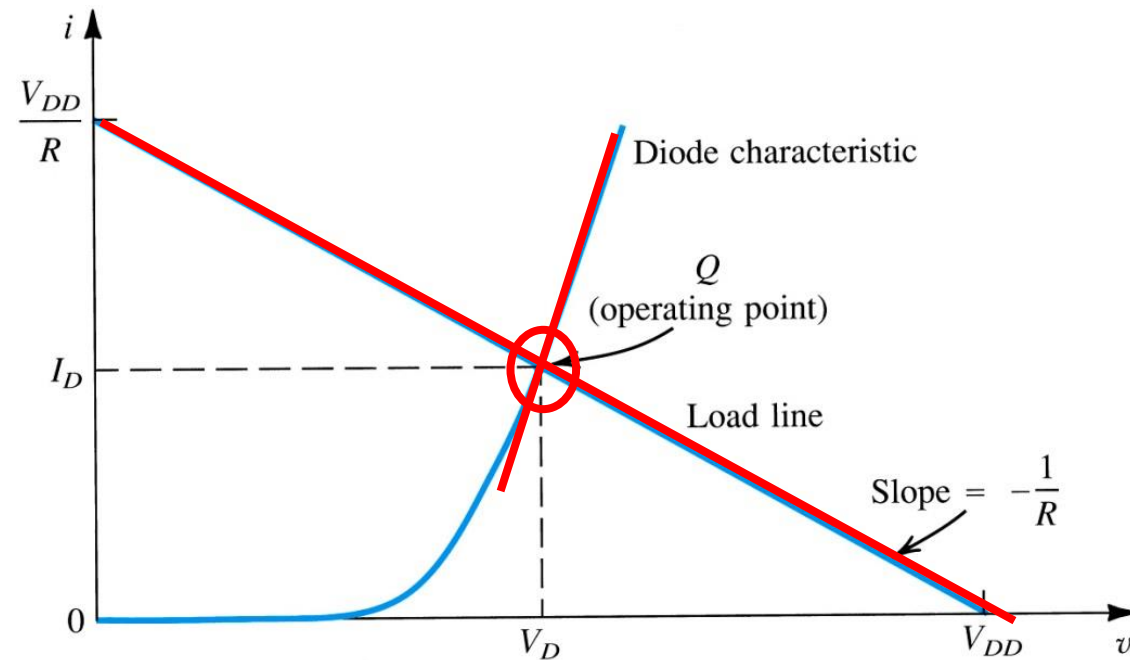- **load line** and diode characteristic intersect at **operating point**



Diode Temperature dependence

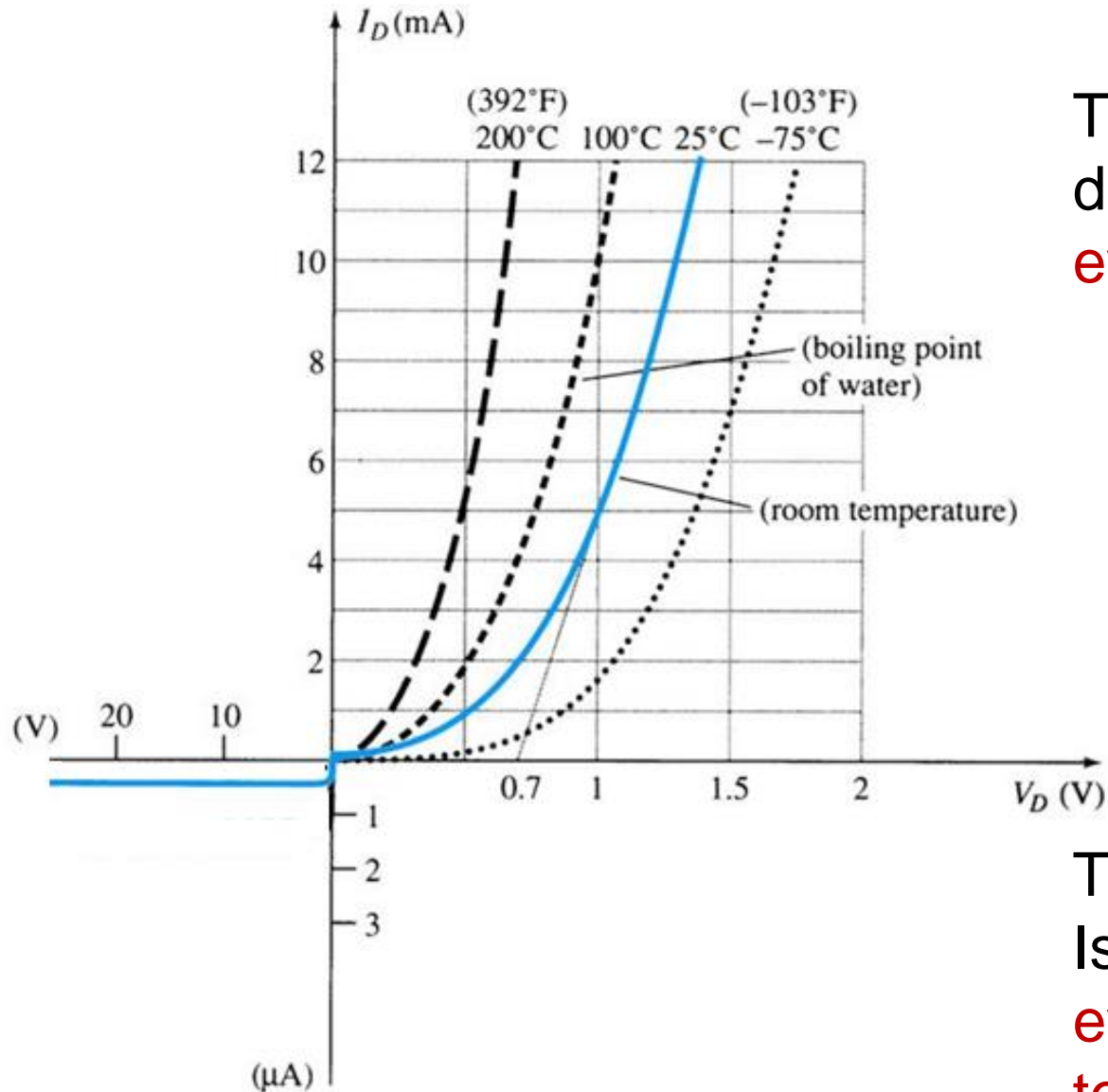


The forward voltage drop decrease by approx. **2 mV** for every **1°C** increase in temperature

The reverse saturation current I_S will **double in magnitude** for every **10°C** increase in temperature

Diode Resistance



- DC or Static Resistance

$$R_D = V_D / I_D$$

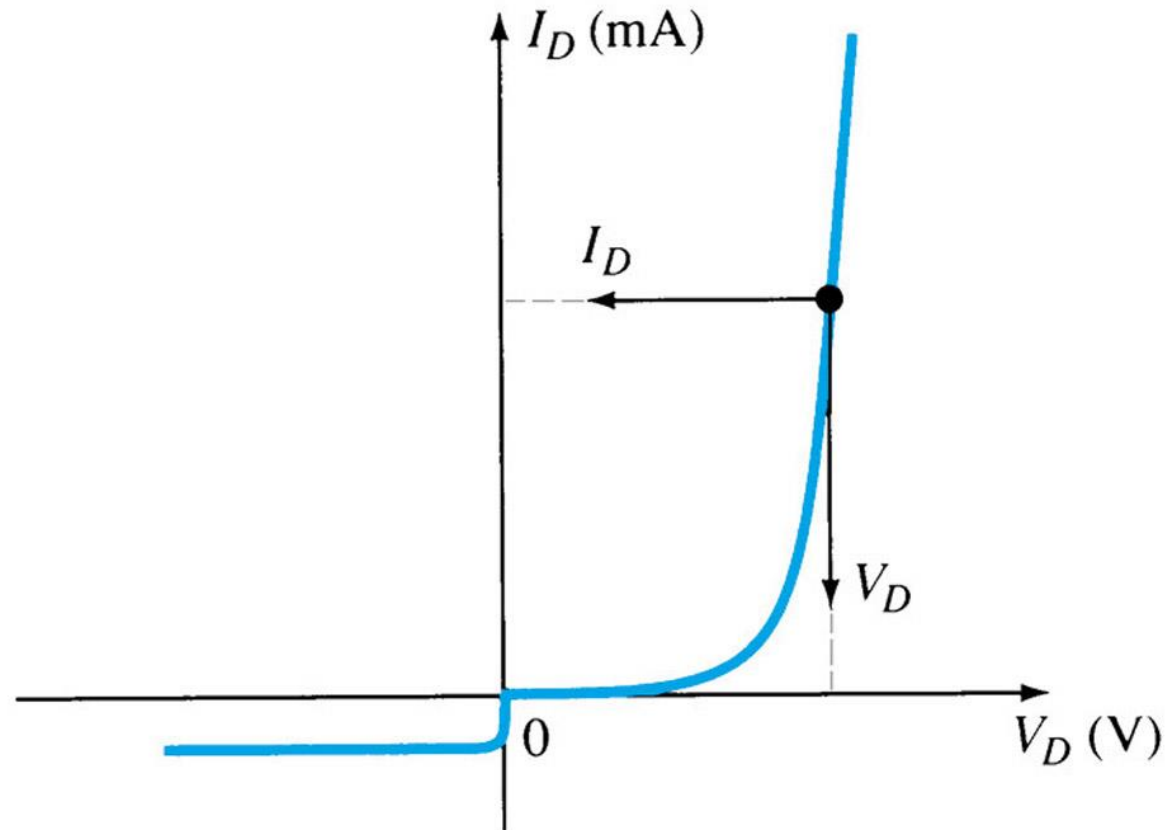

Diode Resistance

- AC or Dynamic Resistance

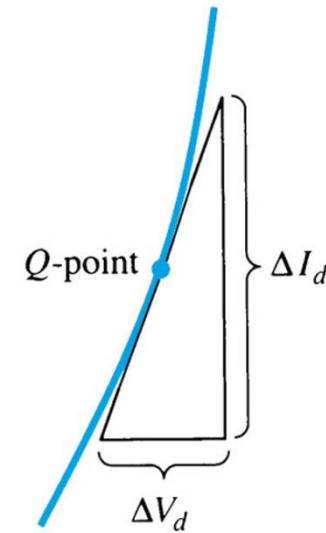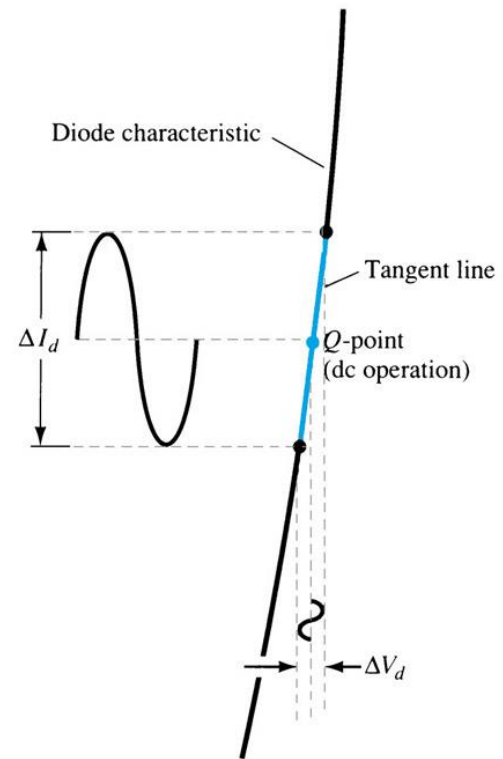

Diode Resistance


- Determining AC or Dynamic Resistance

$$r_d = \frac{\eta V_T}{I_D}$$

At room temperature

$$V_T = 26 \text{ mV}$$

$$r_d = 26\text{mV} / I_D$$

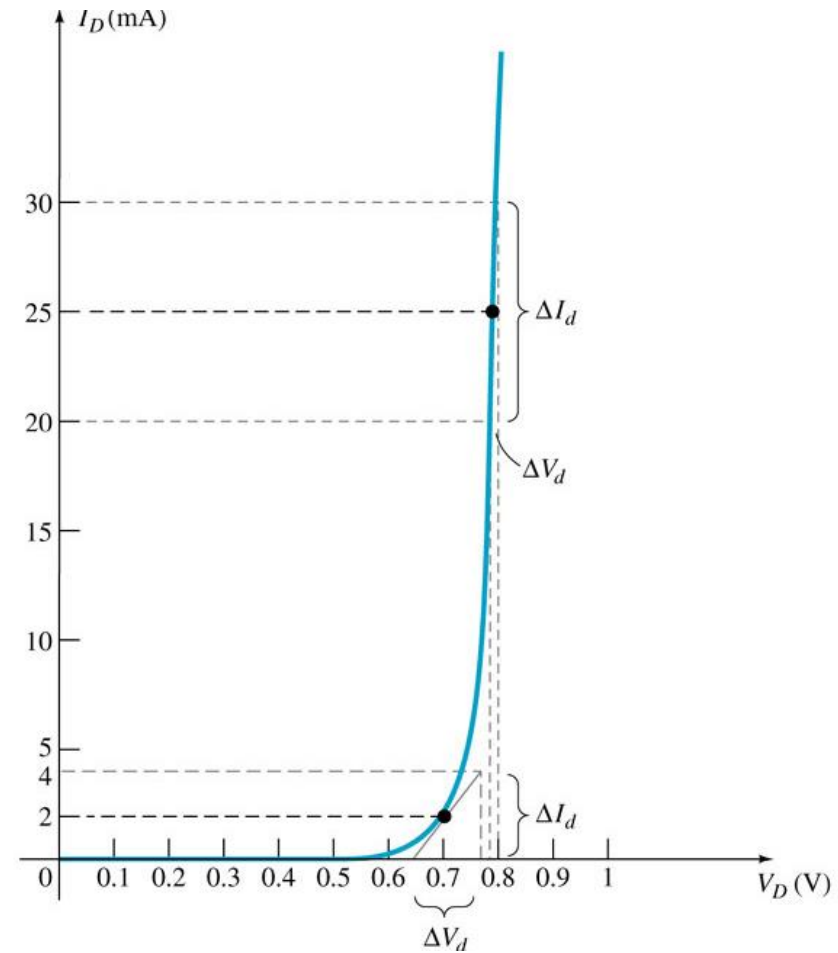

i-v relationship

- $I_D = I_s (e^{V_D/\eta V_T} - 1)$

Current I_1 corresponding to diode voltage V_1

$$I_1 = I_s (e^{V_1/\eta V_T})$$

Current I_2 corresponding to diode voltage V_2

$$I_2 = I_s (e^{V_2/\eta V_T})$$


$$I_2/I_1 = e^{V_2 - V_1/\eta V_T}$$

$$V_2 - V_1 = \eta V_T \ln(I_2/I_1)$$

$$V_2 - V_1 = 2.3\eta V_T \log(I_2/I_1)$$

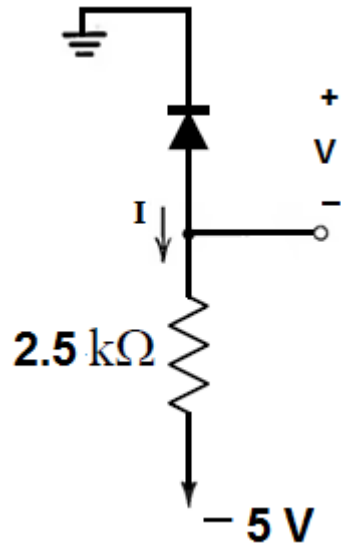
Problem #2

Find the values of I and V in the circuits shown below. Assume diodes to be ideal.



(a)

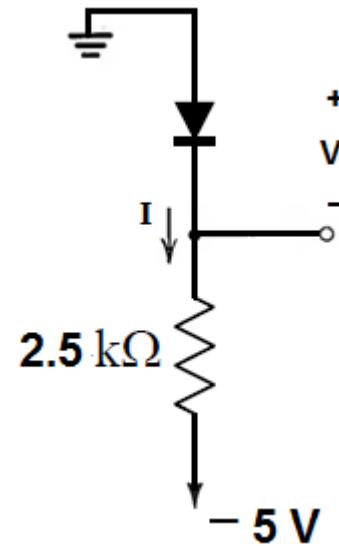Solution: $I = 0\text{ mA}$, $V = 5\text{ V}$




(b)

Solution: $I = 2\text{ mA}$, $V = 0\text{ V}$

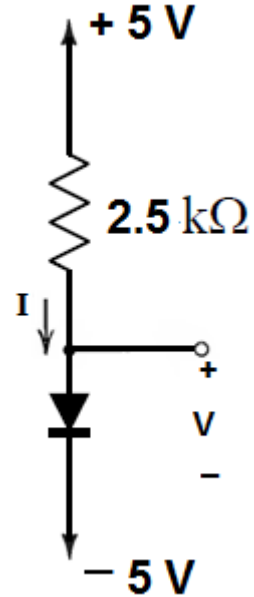Problem #3

Find the values of I and V in the circuits shown below. Assume diodes to be ideal.



Solution: $I=4 \text{ mA}$, $V= -5 \text{ V}$