



FPGA Fabrics



Reference


- Wayne Wolf, 'FPGA-Based System Design' Pearson Education, 2004




CPLD / FPGA

CPLD

 - Interconnection of several PLD blocks with Programmable interconnect on a single chip
- Logic blocks executes sum-of-product expressions and stores the results in micro-cell registers
- Programmable interconnects route signals to and from logic blocks



CPLD

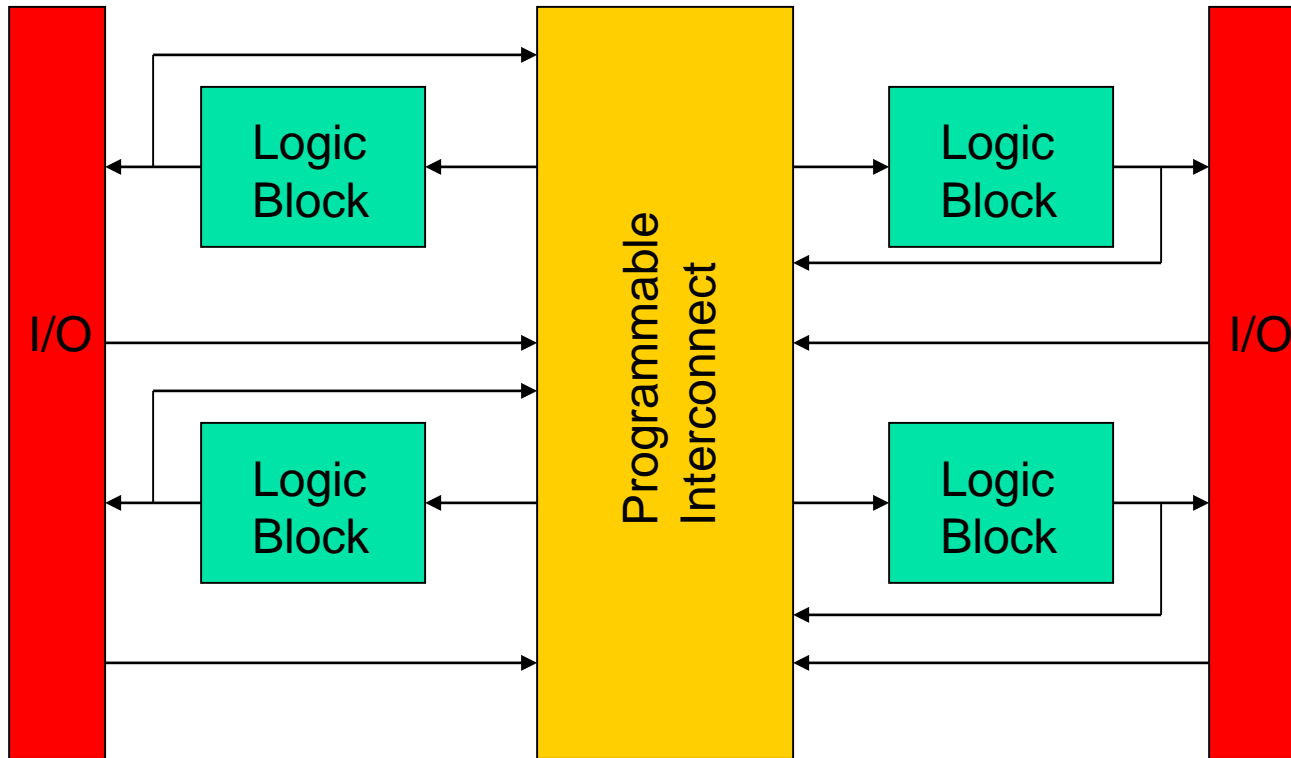




Major CPLD Resources


- Number of macro-cells per logic block
- Number of inputs from programmable interconnect to logic block
- Number of product terms in logic block

FPGA

 
- Programmable Logic Blocks
 - Implement combinational & sequential logic
- Programmable Interconnect
 - Wires to connect inputs and outputs to logic blocks
- Programmable I/O blocks
 - Logic blocks at the periphery for external connections



Structure of FPGA

 

FPGA Fabric

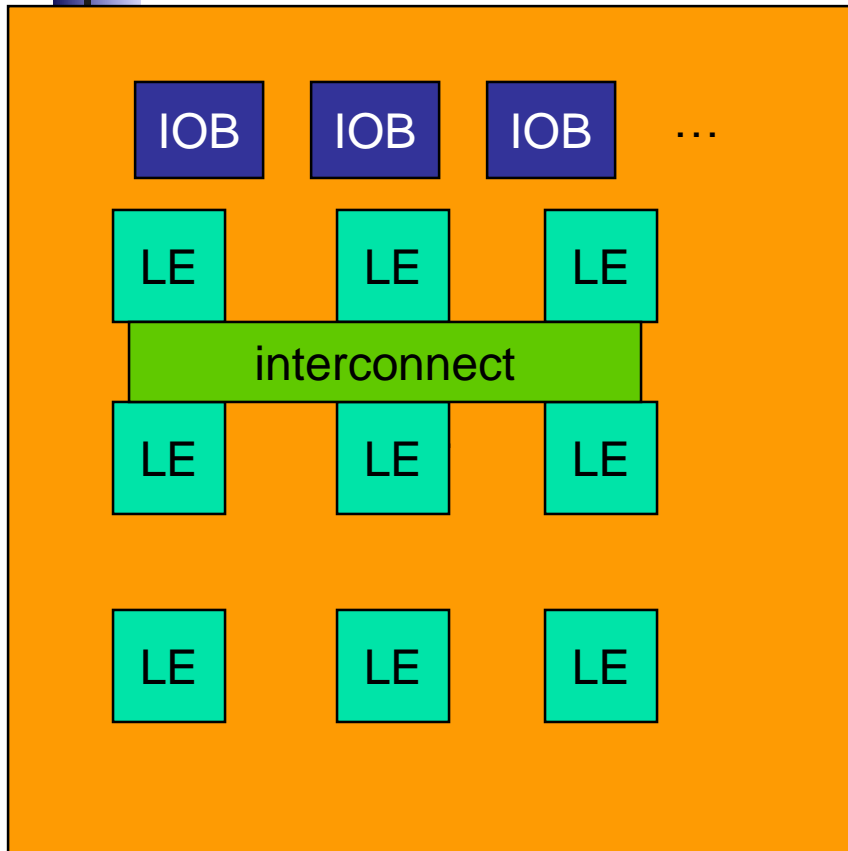


- CLB: combinational logic block = logic element (LE).
- LUT: Lookup table = SRAM used for truth table.
- I/O block (IOB): I/O pin + associated logic and electronics.

FPGA Fabric


- Look-up table with N-inputs can be used to implement any combinational function of N-inputs
- LUT is programmed with truth table

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0

Truth-table

 


LUT implementation

 


Gate implementation

FPGA Fabric


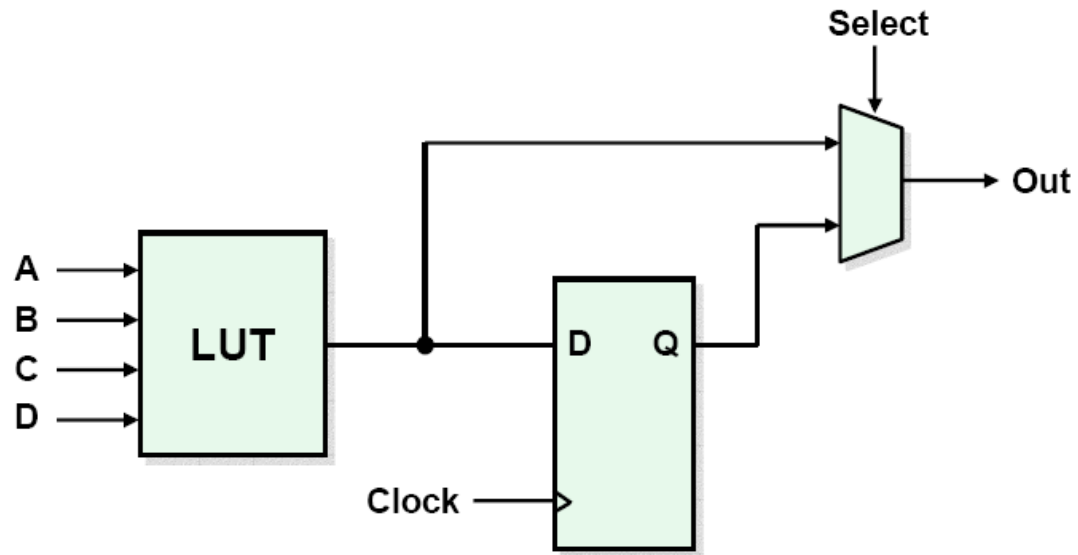


LUT

 - 3-input LUT
- Based on Multiplexers
- LUT entries stored in configuration memory cells




FPGA Fabric (contd)

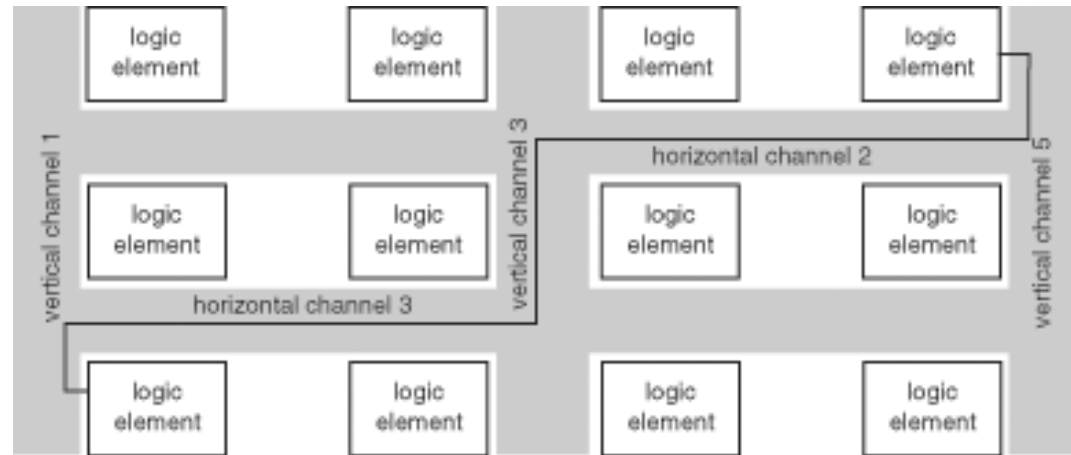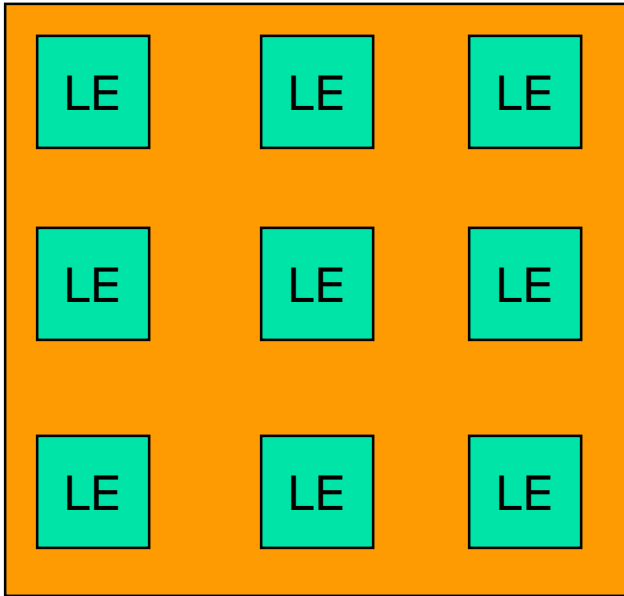




 - Organized into channels.
 - Many wires per channel.
- Connections between wires made at programmable interconnection points.
- Must choose:
 - Channels from source to destination.
 - Wires within the channels.



Choosing a Path

 




Routing Problems

- Global routing:
 - Which combination of channels?
- Local routing:
 - Which wire in each channel?
- Routing metrics:
 - Net length.
 - Delay.


Segmented wiring Vs Offset wiring

■ Segments


Length 1

 

Length 2

 

■ Offset

 



SRAM-based FPGA fabrics

- Xilinx
- Altera



SRAM-based FPGAs


- Program logic functions, interconnect using SRAM.
- Advantages:
 - Re-programmable;
 - dynamically reconfigurable;
 - Fabricated with standard VLSI processes.
- Disadvantages:
 - SRAM burns power.
 - Possible to steal, disrupt configuration bits.



Logic elements


- Logic element includes combinational function + register(s).
- Use SRAM as lookup table **LUT** for combinational function.

LUT-based logic element

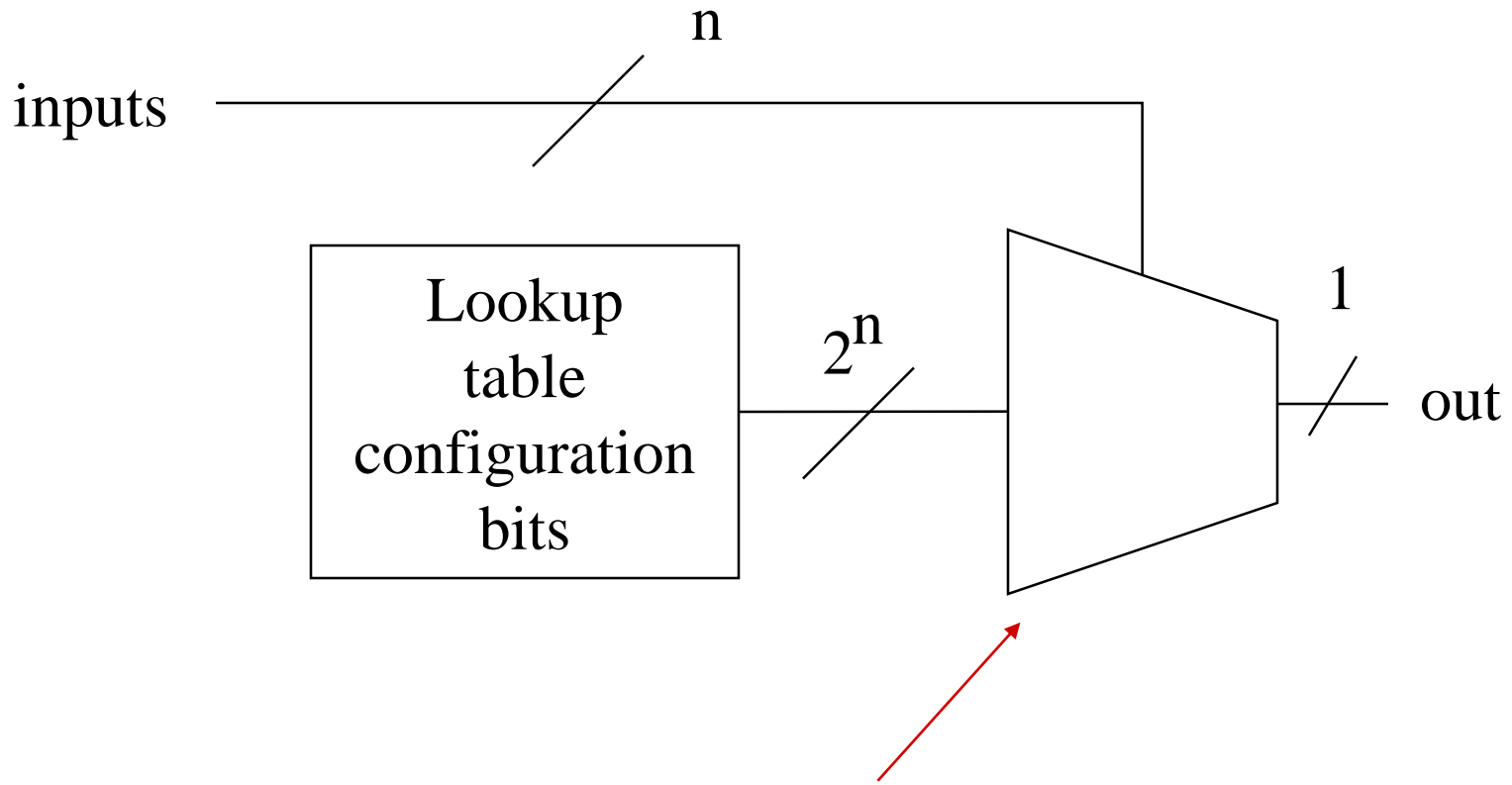

Can multiplex at output or address at input

Example

 




Evaluation of SRAM-based LUT

- N-input LUT can handle function of 2^n inputs.
- All logic functions take the same amount of space.
- All functions have the same delay.
- SRAM is larger than static gate equivalent of function.
- Burns power at idle.
- Want to selectively add register to LE:

Registers in logic elements

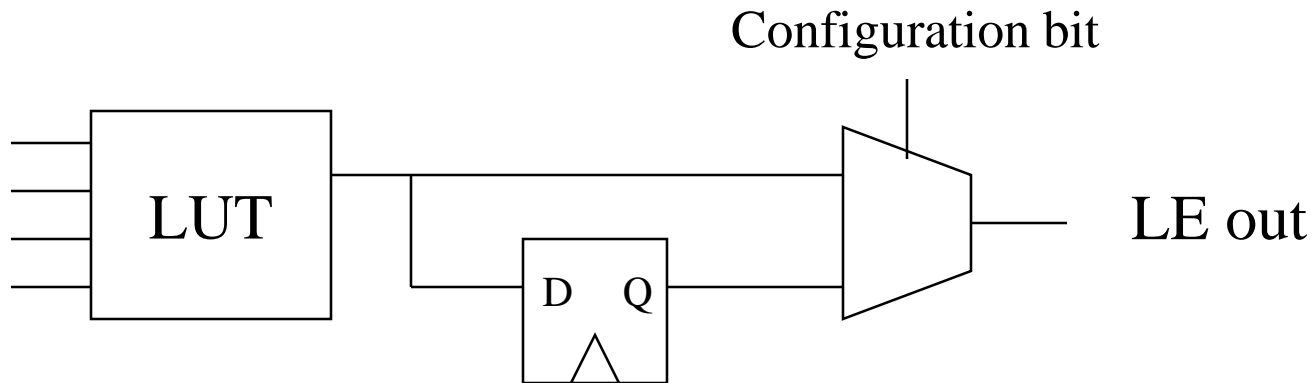- Register may be selected into the circuit:






Other LE features

- Multiple logic functions in an LE are possible.
- Specialized Addition logic:
 - carry chain.
- Partitioned lookup tables.



Xilinx Spartan-II CLB

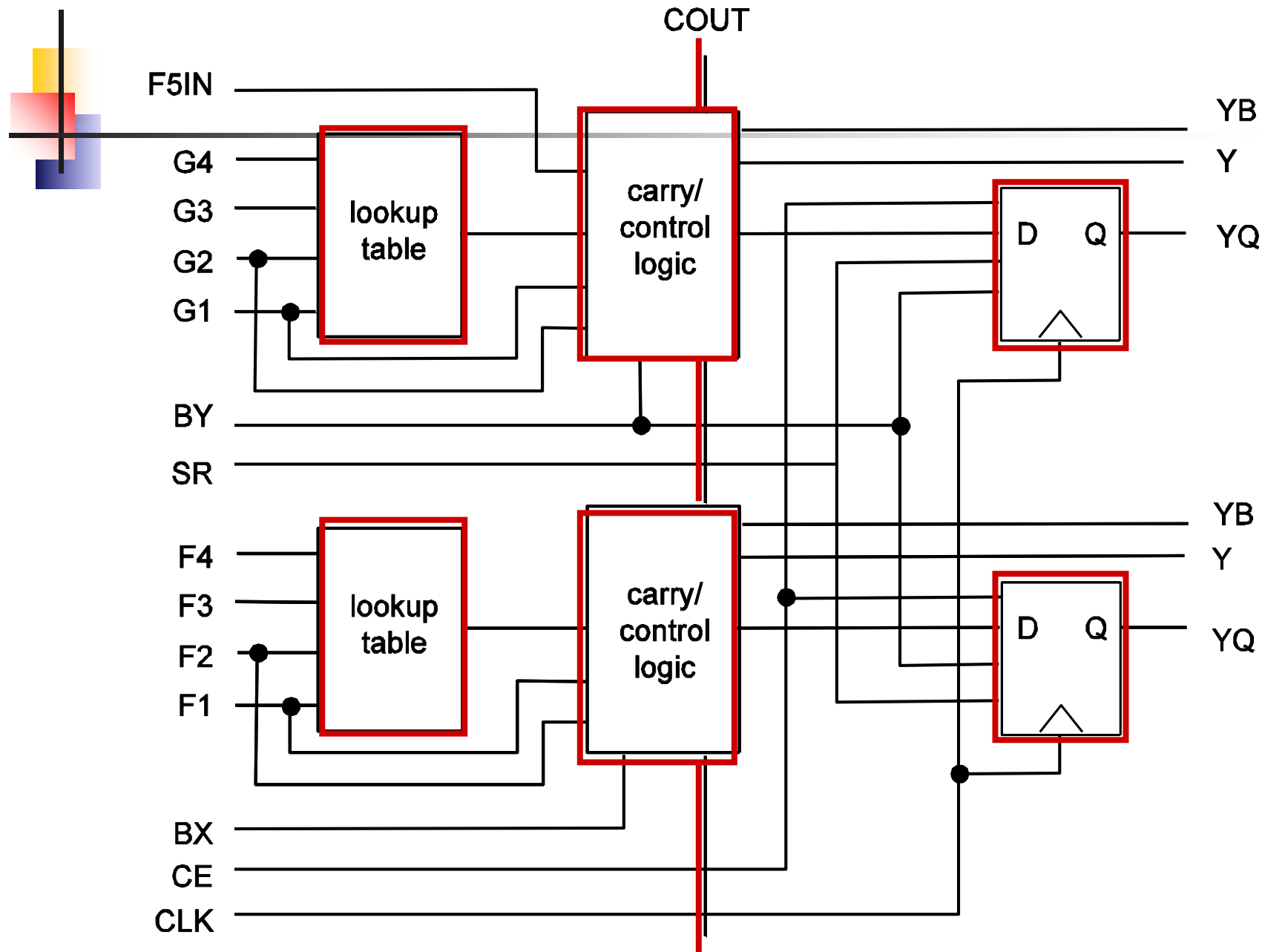- Each CLB has two identical slices.
- Slice has two logic cells:
 - LUT.
 - Carry/control logic.
 - Registers.





Spartan-II CLB details

- Each lookup table can be used as a 16-bit synchronous RAM or 16-bit shift register.
- Arithmetic logic includes an XOR gate.
- Each slice includes a mux to combine the results of the two function generators in the slice.
- Register can be configured as DFF or latch.




Spartan-II CLB operation

- Arithmetic:
 - Carry block includes XOR gate.
 - Use LUT for carry, XOR for sum.
- Each slice uses F5 mux to combine results of multiplexers.
- F6 mux combines outputs of F5 muxes.
- Registers can be FF/latch; clock and clock enable.
- Includes three-state output for on-chip bus.



Altera APEX II logic element

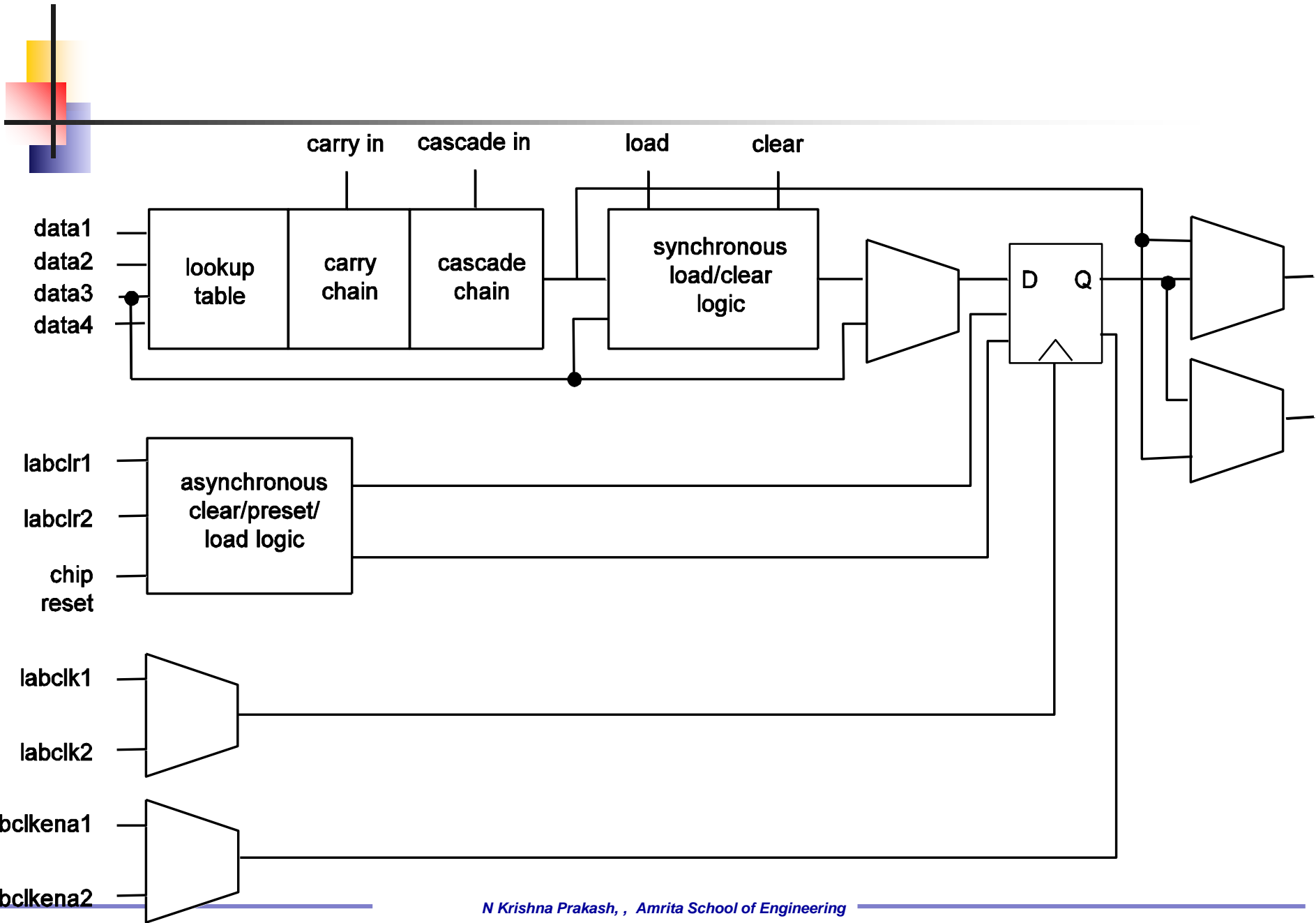- Each logic array block (LAB) has 10 logic elements.
- Each LE contains LUT, FF.
- Logic elements share some logic – carry and control signal generation







Apex II LE modes

- Modes of operation:
 - Normal.
 - Arithmetic.
 - Counter.


APEX-II LE normal mode

 


APEX-II LE arithmetic mode

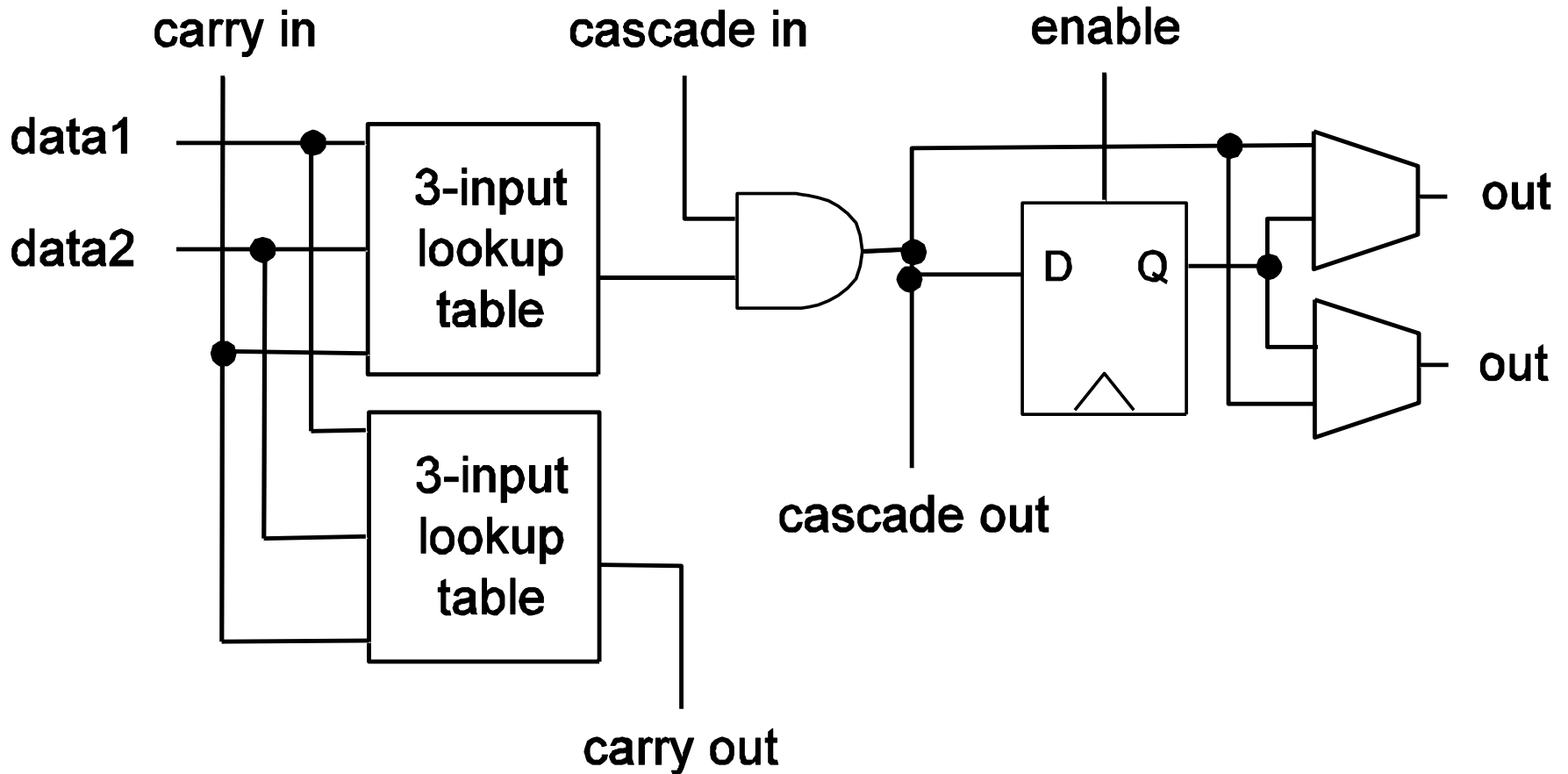

APEX-II LE counter mode

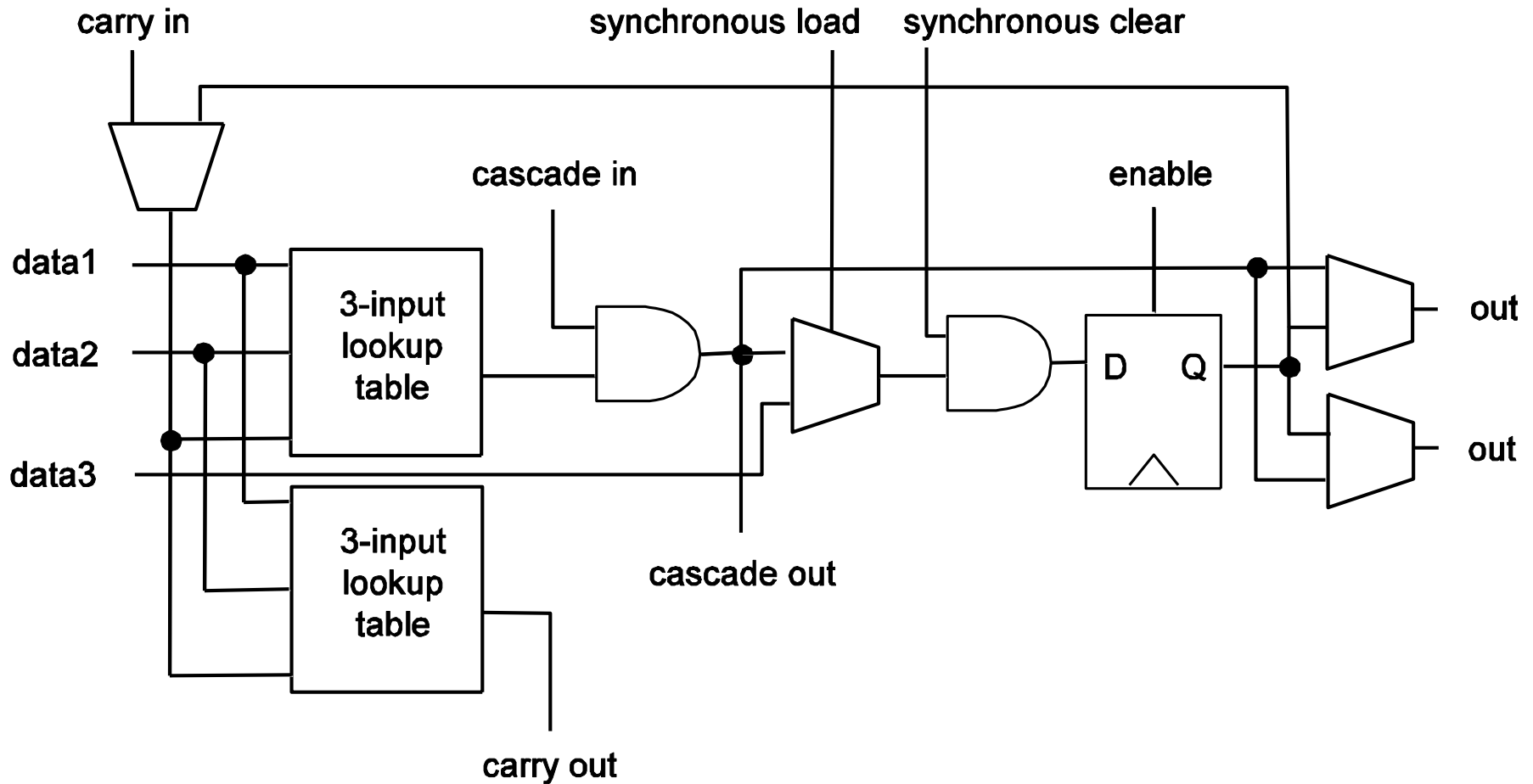


APEX-II LE control logic

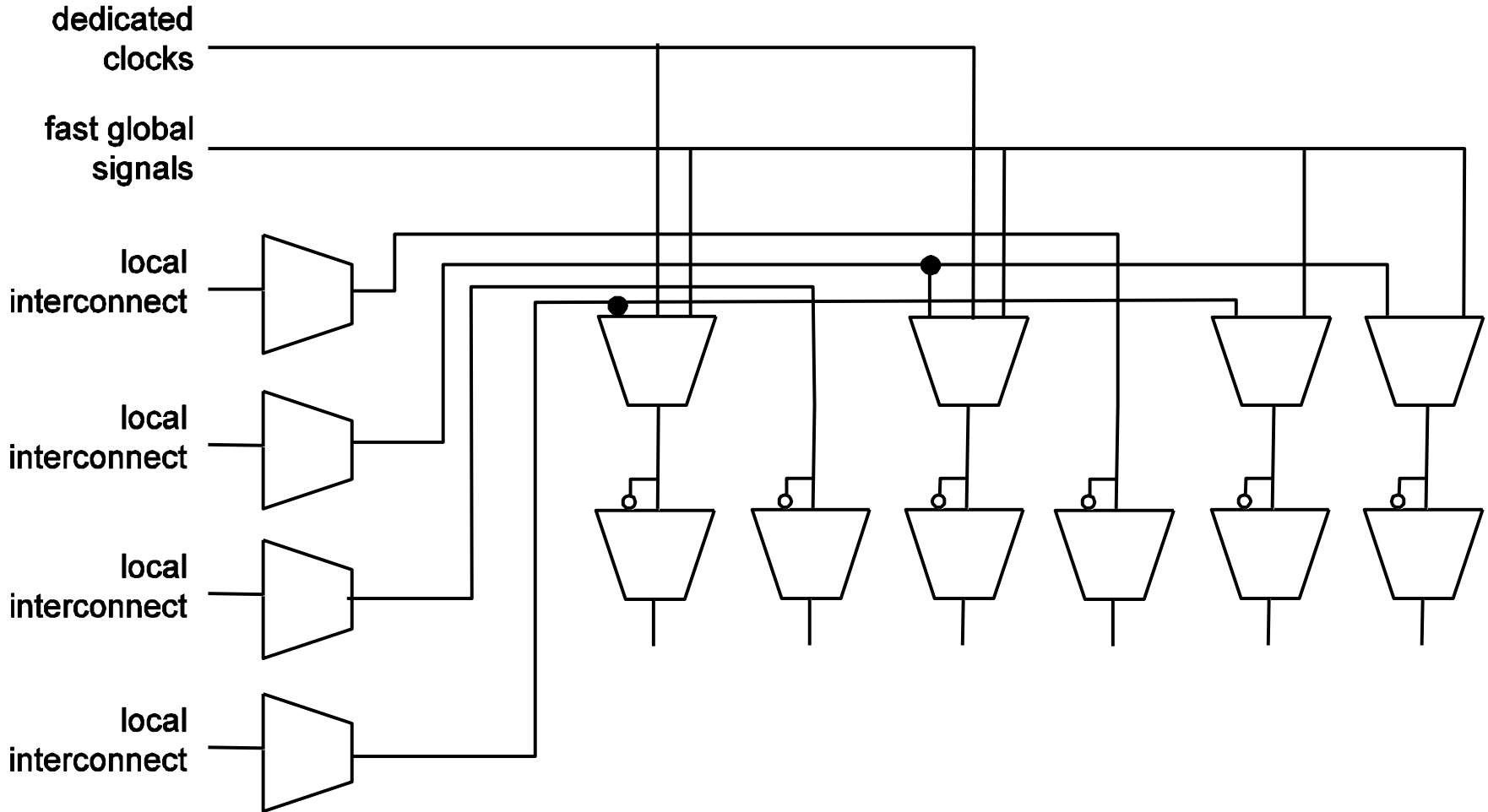

Programmable interconnect

 - Uses SRAM to hold information used to program interconnect
- MOS switch controlled by configuration bit:
- CMOS transistor – pass transistor
- CMOS has good off state





Programmable vs. fixed interconnect

- Switch adds delay.
- Transistor off-state is worse in advanced technologies.
- FPGA interconnect has extra length = added capacitance.




Interconnect strategies

- Some wires will not be utilized.
- Congestion will not be same throughout chip.
- Types of wires:
 - Short wires: local LE connections.
- Global wires: long-distance, buffered communication.
 - Special wires: clocks, etc.


Paths in interconnect

- Connection may be long, complex:

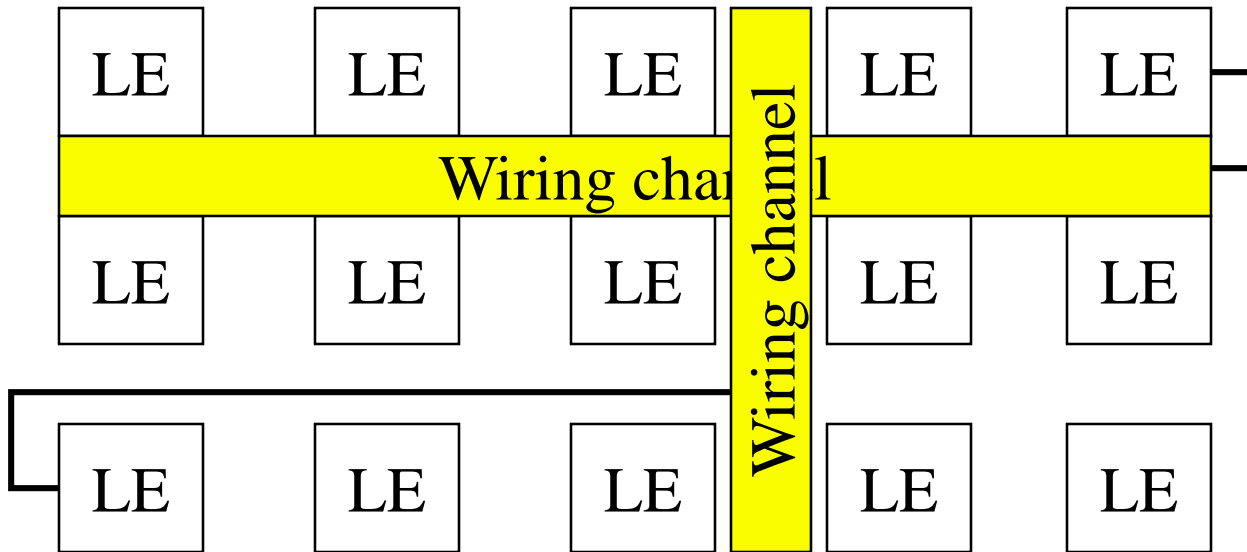

Interconnect architecture

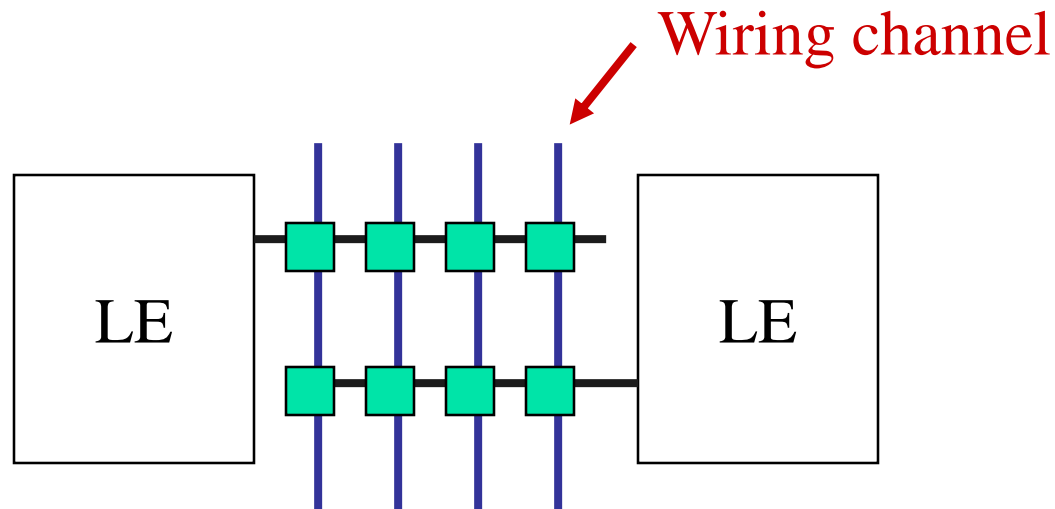- Connections from wiring channels to LEs.
- Connections between wires in the wiring channels.






Interconnect richness

- Within a channel:
 - How many wires.
 - Length of segments.
 - Connections from LE to channel.
- Between channels:
 - Number of connections between channels.
 - Channel structure.




Segmented wiring

 




Offset segments

 



Switchbox

 



Spartan-II interconnect

- Types of interconnect:
 - local;
 - general-purpose;
 - dedicated;
 - I/O pin
 - Global
 - Clock




Spartan-II general-purpose network

- Provides majority of routing resources:
 - General routing matrix (GRM) connects horizontal/vertical channels and CLBs.
 - Interconnect between adjacent GRMs.
 - Hex lines connect GRM to GRMs six blocks away.
 - Hex lines provide longer interconnect.
 - 12 longlines span the chip.


Spartan-II routing

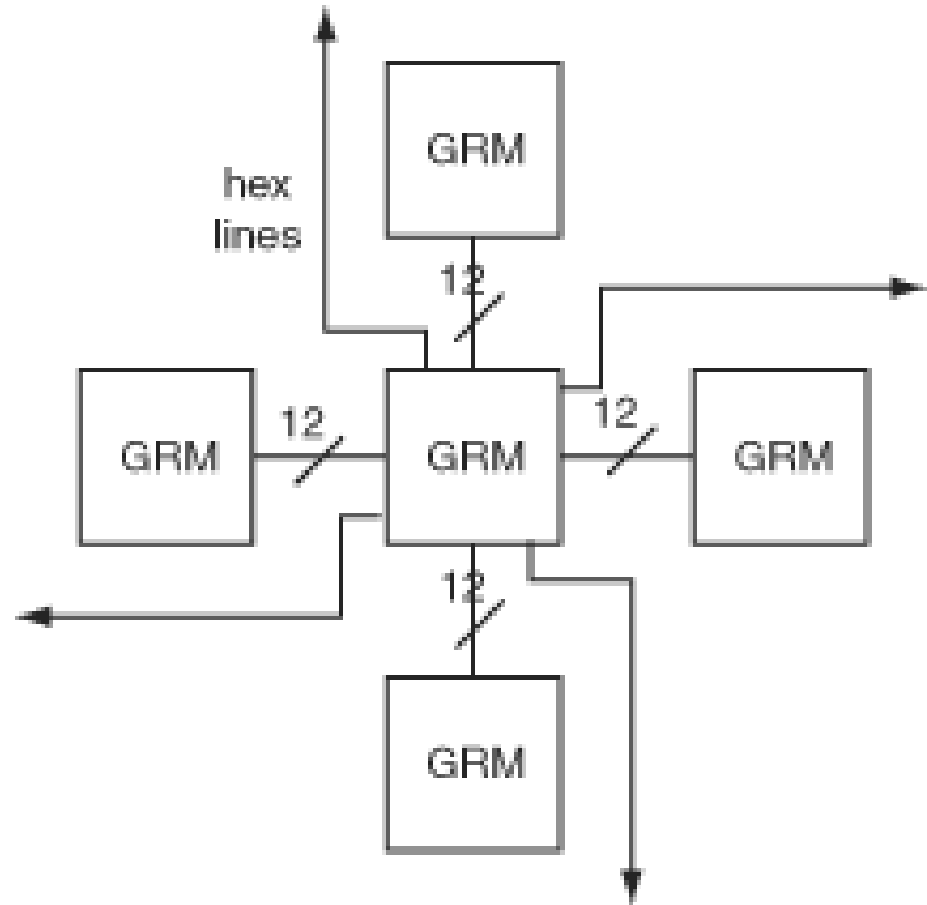- Relationship between GRM, hex lines, and local interconnect:




Spartan-II three-state bus

- Horizontal on-chip busses:

 


Spartan-II clock distribution

 



Altera APEX II interconnect

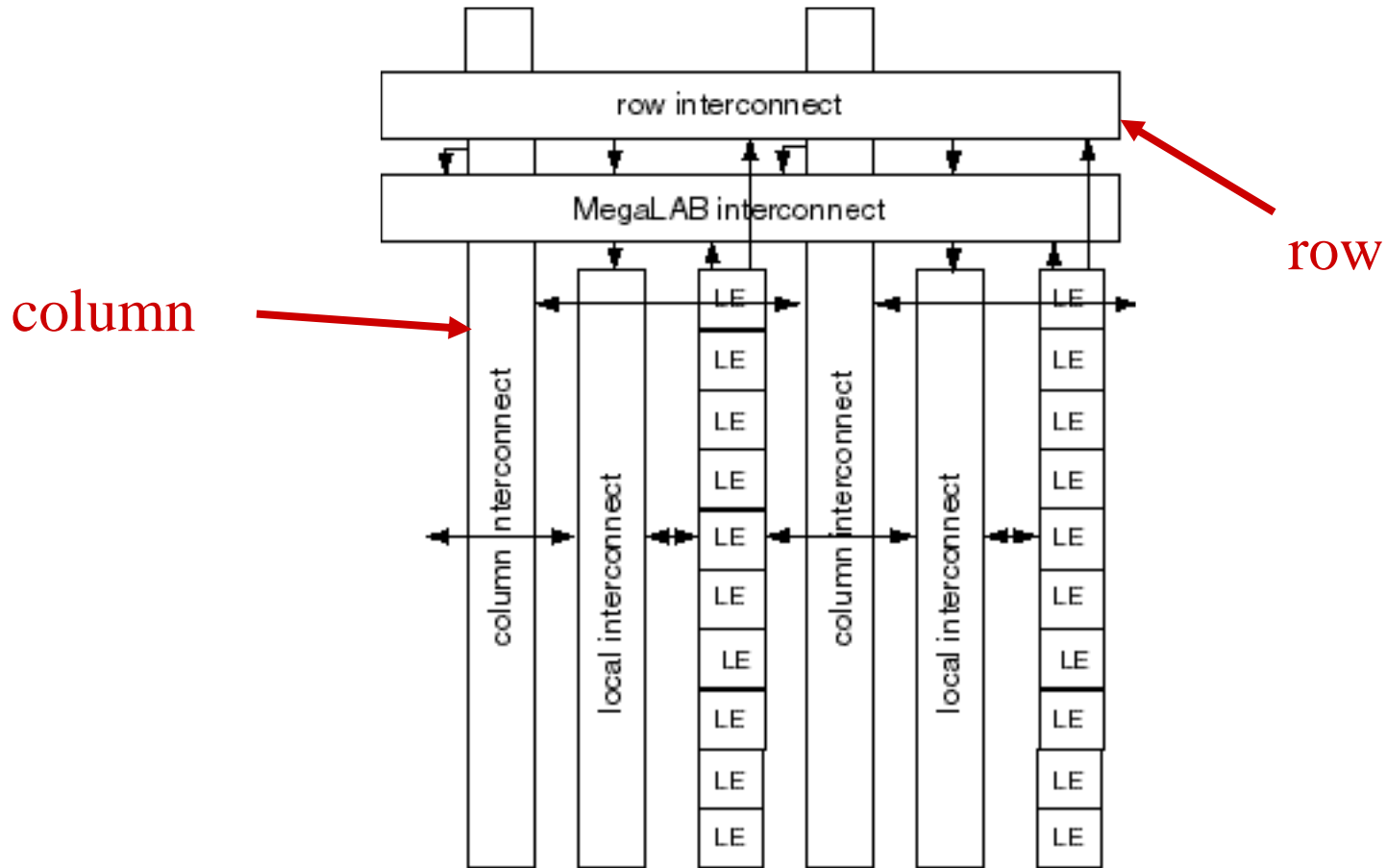



Permanently programmed FPGAs

- Antifuse




Antifuses

- Permanently programmed.
- Make a connection with electrical signal.
- Resistance of about 100Ω which is more than standard via



Antifuse structure

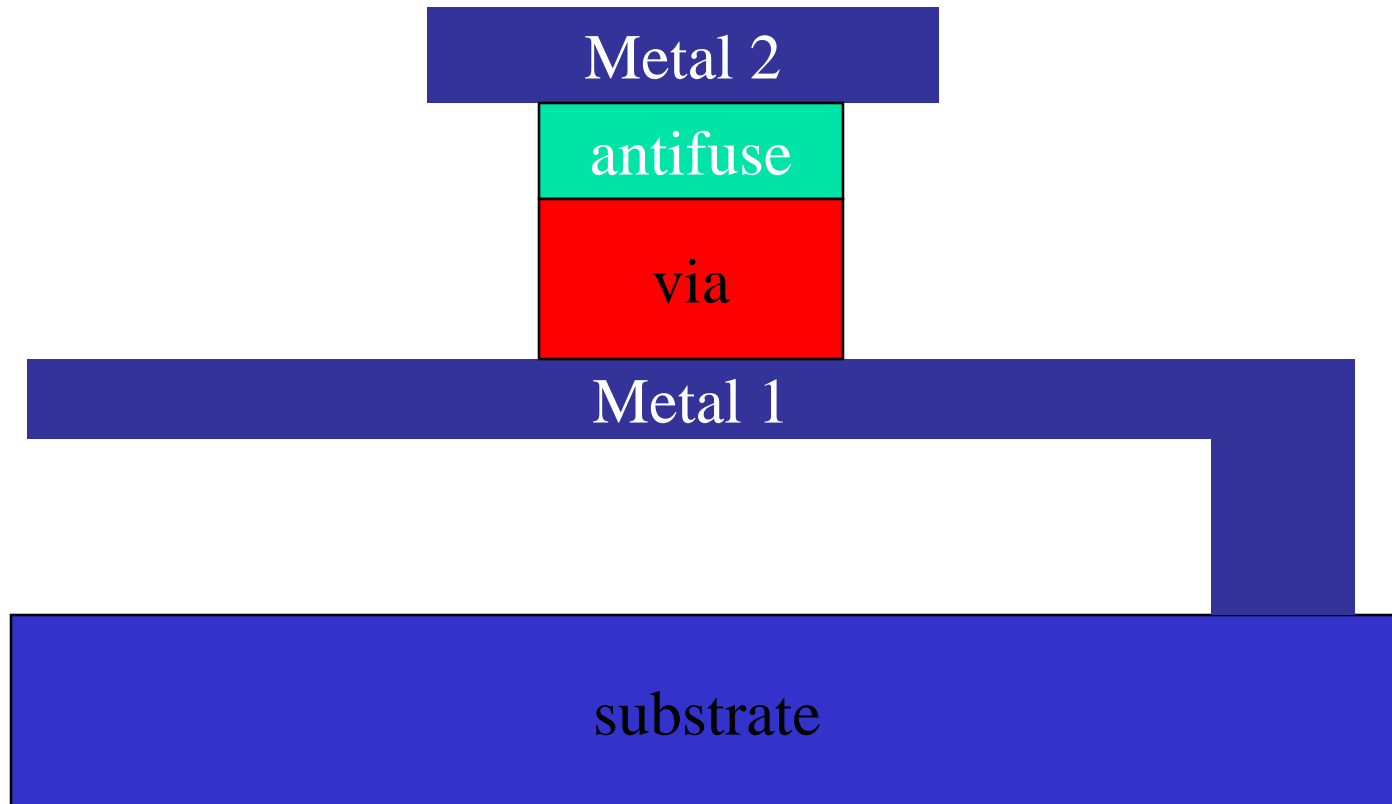




Flash-programmed FPGA

- Flash is high quality programmable read only memory
- Uses a floating gate structure where low leakage capacitor holds a voltage that controls a transistor gate




Flash-programmed switch

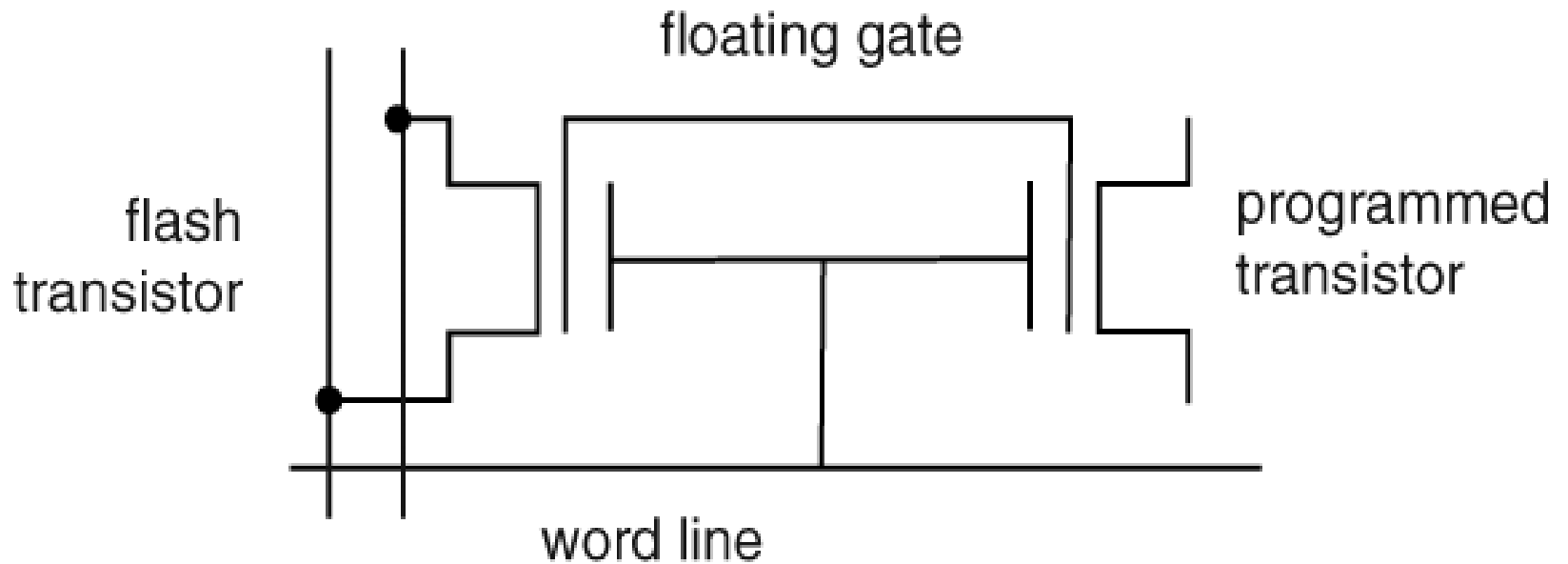

Logic blocks

 
- Program by making connections.
- Based on multiplexing.



a	out
0	d0
1	d1


Truth table

Larger logic block

 


Actel 54SX adder logic

 - Uses two C-cells in SuperCluster.
- Adds bits A0 and A1.
- Carry in FCI, carry out FCO.
- Active when CFN is high.



Actel 54SX R cell

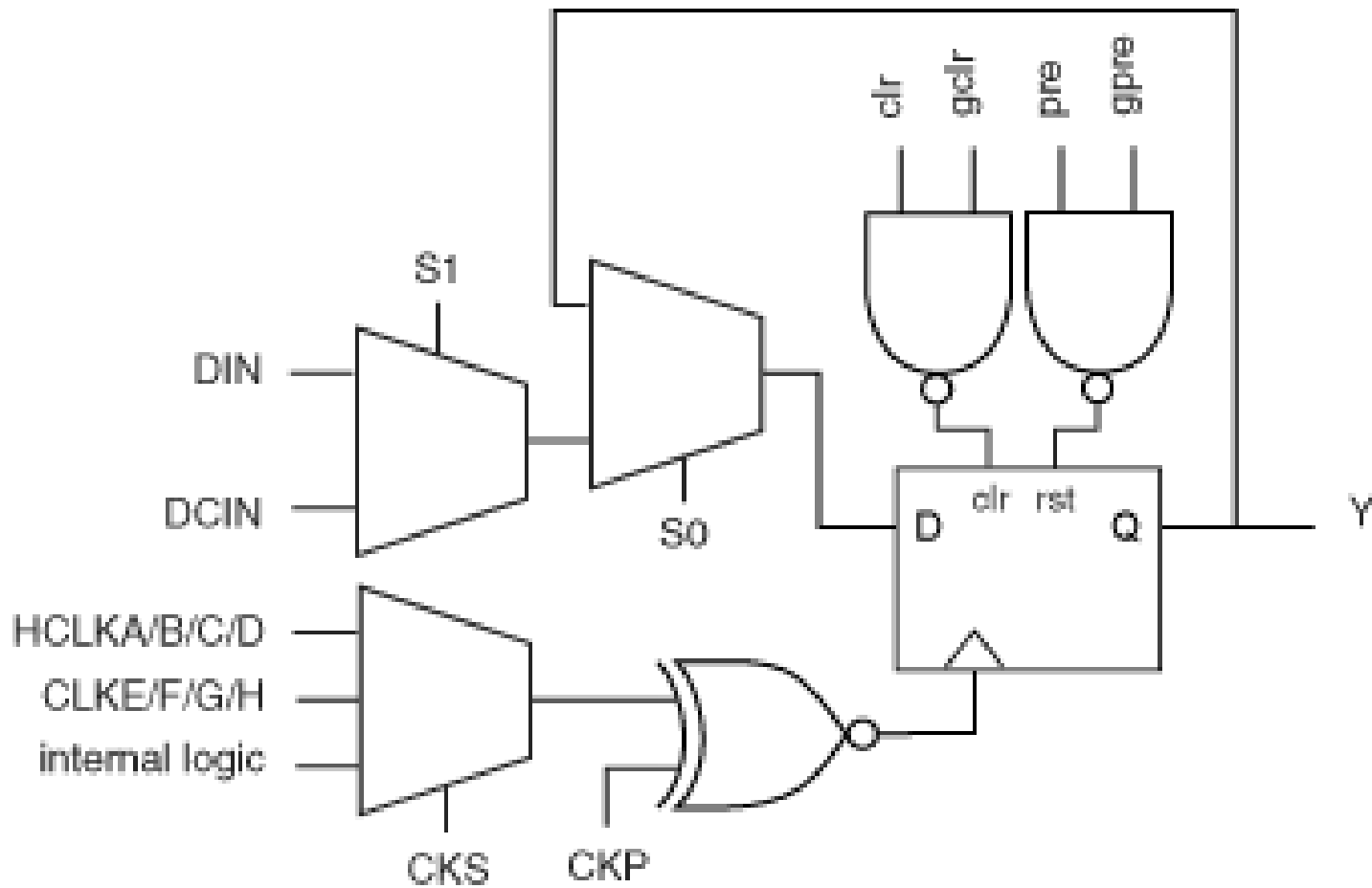




Actel 54SX LE

- C/R cells organized into clusters.
 - Type 1 cluster: CRC.
 - Type 2 cluster: CRR.
- Clusters grouped into superclusters.
 - Type 1: two type 1 clusters.
 - Type 2: one type 1, one type 2.

Actel ProASIC 500K logic gate

 - Uses switches to connect inputs, feedback, etc.





Actel 54SX interconnect


- FastConnect provides horizontal connections between logic modules.
 - Within a supercluster.
 - To supercluster below.
- DirectConnect is within a supercluster:
 - connects C-cell to R-cell neighbor.
- Generic global wiring in segmented channels.



Antifuse programming

- Need to be able to apply programming voltage to every antifuse.
 - Path from VDD to GND.
- Programming can be performed slowly.
 - Don't need a lot of parallelism.
- Use the wiring network to gain access to the antifuses.
 - Access transistors control path to antifuse.

Antifuse programming access transistors

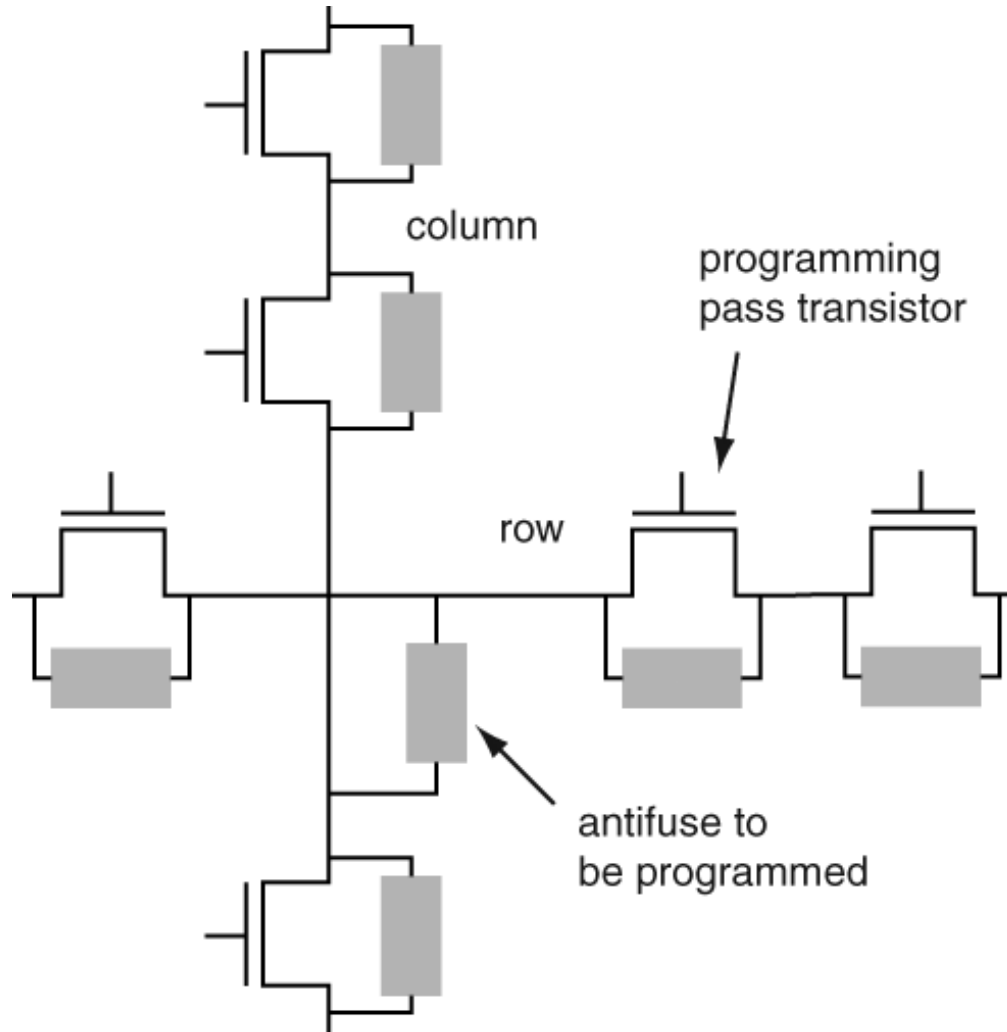



I/O pins


- Need programmable pins:
 - Input or output.
 - Three-state.
- Other features:
 - Registers.
 - Slew rate.
 - Voltage levels.
 - Double-data rate (DDR) support.



Actel APEX II I/O

- Supports SDRAM and double-data rate (DDR) memory.
- Six registers and latch.
- Bidirectional buffers.
- Two inputs and two outputs.


APEX II I/O

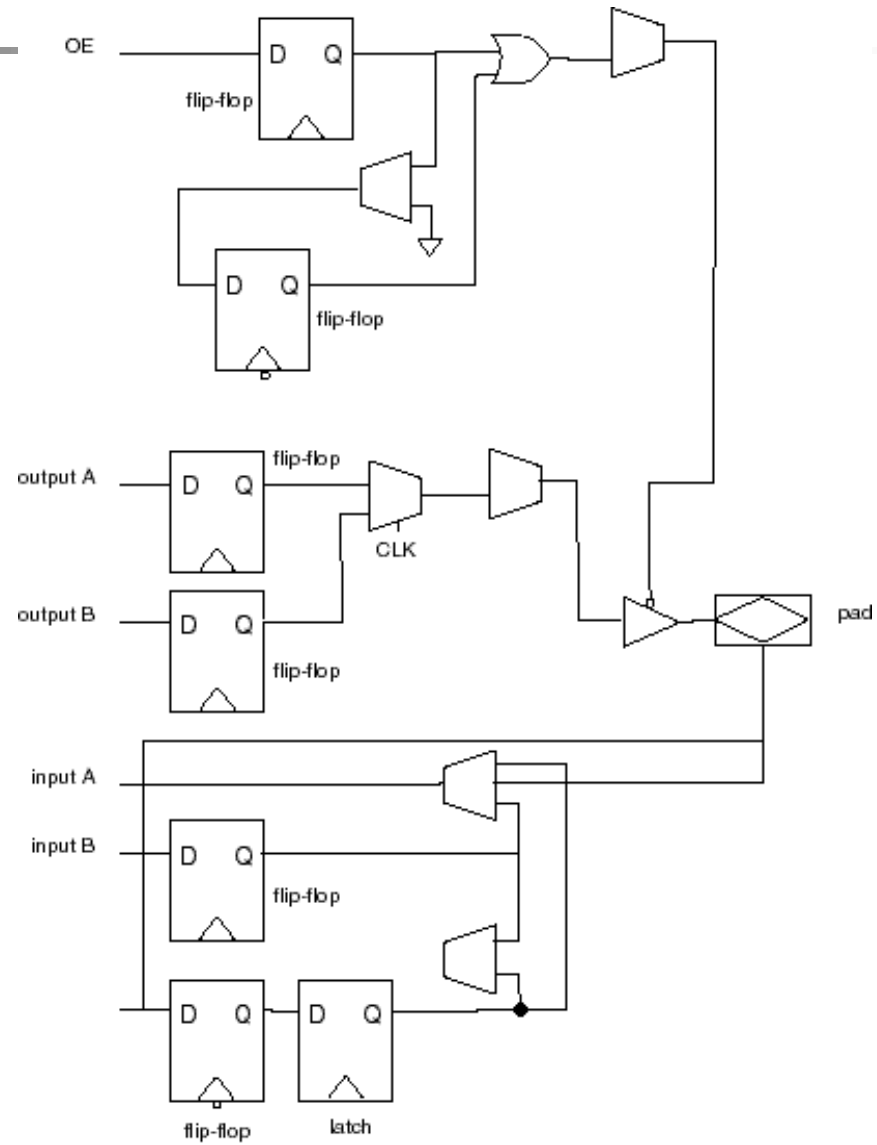


- 
-
- Circuit design for FPGAs:
 - Logic elements.
 - Interconnect.



Multiplexers as logic elements

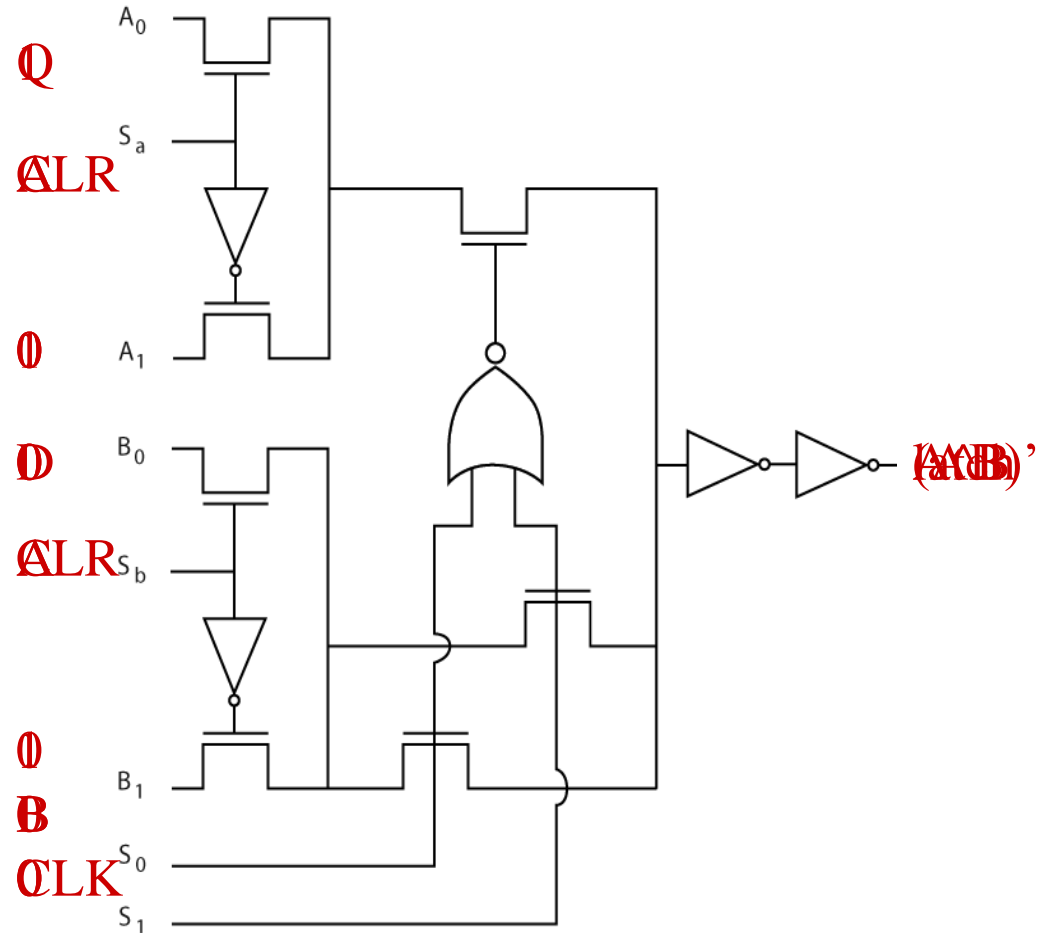

Using antifuses

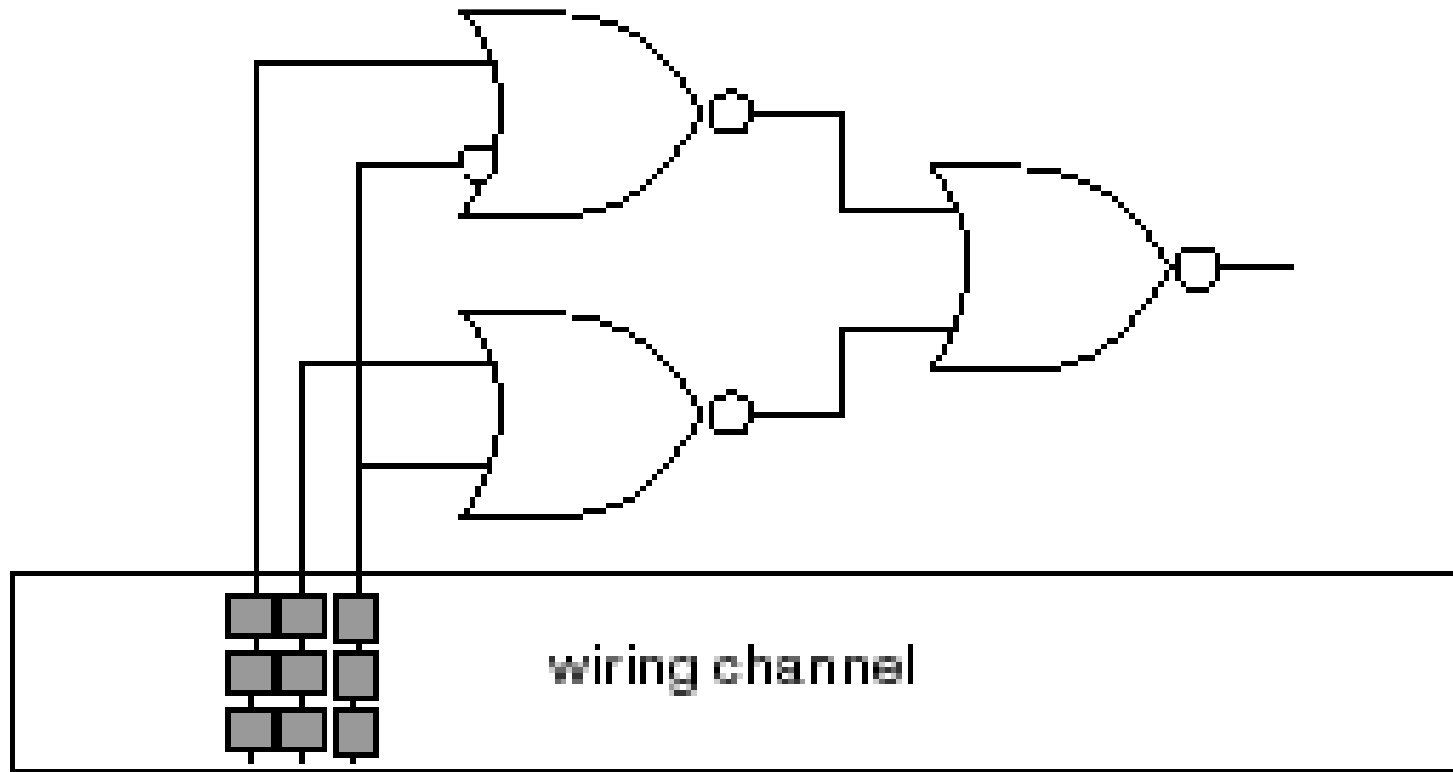




Static CMOS gate vs. LUT

- Number of transistors:
 - NAND/NOR gate has $2n$ transistors.
 - 4-input LUT has 128 transistors in SRAM, 96 in multiplexer.
- Delay:
 - 4-input NAND gate has 9τ delay.
 - SRAM decoding has 21τ delay.
- Power:
 - Static gate's power depends on activity.
 - SRAM always burns power.


Lookup table circuitry

- Demultiplexer or multiplexer?

 

Traditional RAM/ROM

- Cell drives long bit line:

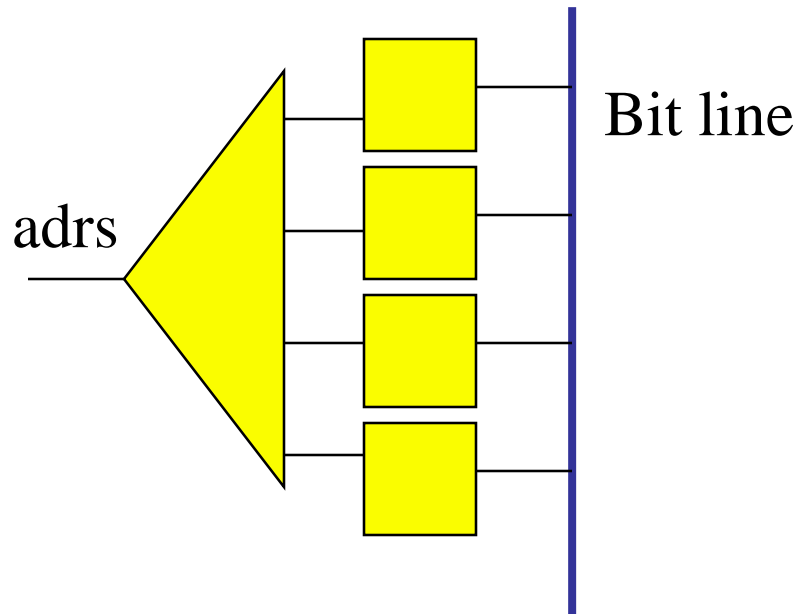





Lookup memory

- Multiplexer presents smaller load to memory cells.
 - Allows smaller memory cells.

Multiplexer styles

 

static gates

 

pass transistors





Multiplexer design

- Pass transistor multiplexer uses fewer transistors than fully complementary gates.
- Pass transistor is somewhat faster than complementary switch:
 - Equal-strength p-type is 2.5X n-type width.
 - Total resistance is 0.5X, total capacitance is 3.5X.
 - RC delay is $0.5 \times 3.5 = 1.75$ times n-type switch.



Static gate four-input mux

  - Delay through n-input NAND is $(n+2)/3$.
- $\lg b + 1$ inputs at first level, so delay is $(\lg b + 3)/3$.
- Delay at second level is $(b+2)/3$.
- Delay grows as $b \lg b$.




Pass-transistor-based four-input mux

  - Must include decode logic in total delay.



Tree-based four-input mux

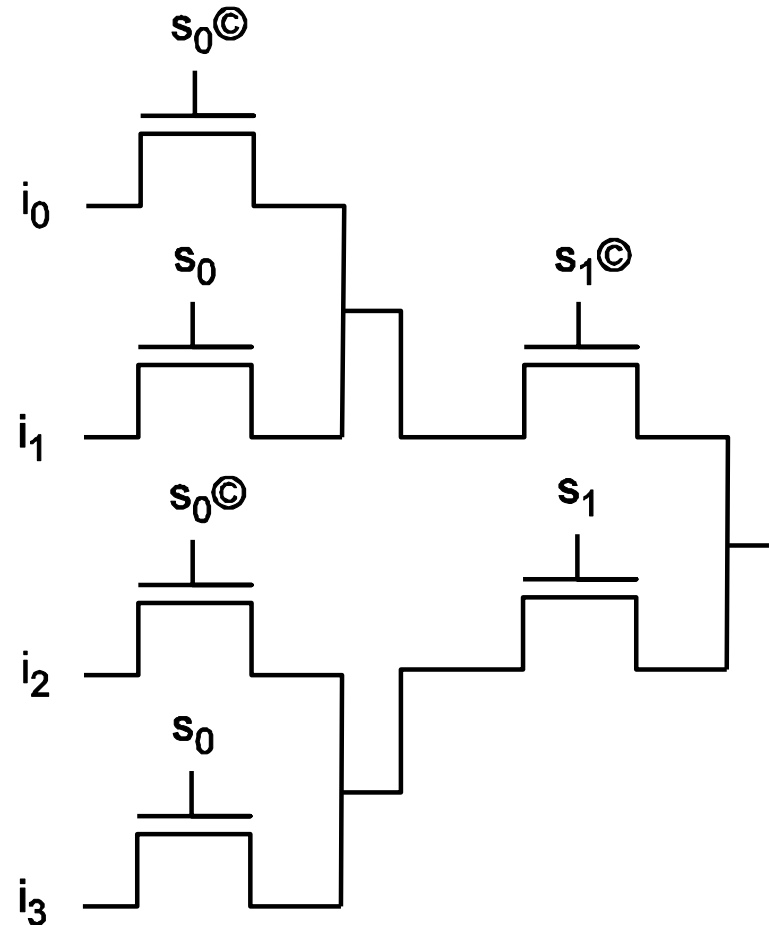- Delay proportional to square of path length.
- Delay grows as $\lg b^2$.






LE output drivers

- Must drive load:
 - Wire;
 - Destination LE.
- Different types of wiring present different loads.


Avoiding programming hazards

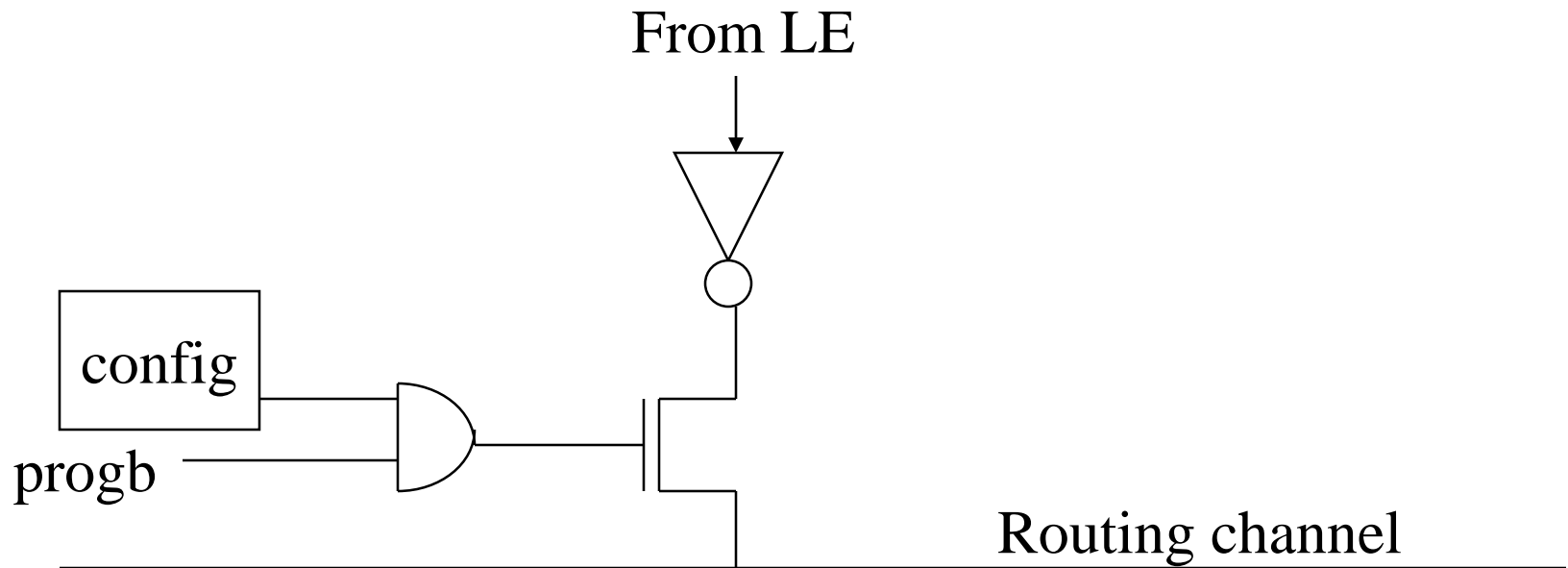- Want to disable connections to routing channel before programming.



Interconnect circuits

 - Why so many types of interconnect?
 - Provide a choice of delay alternatives.
- Sources of delay:
 - Wires.
 - Programming points.



Styles of programmable interconnection point




pass transistor



Three-state


Pass transistor programmable interconnect point

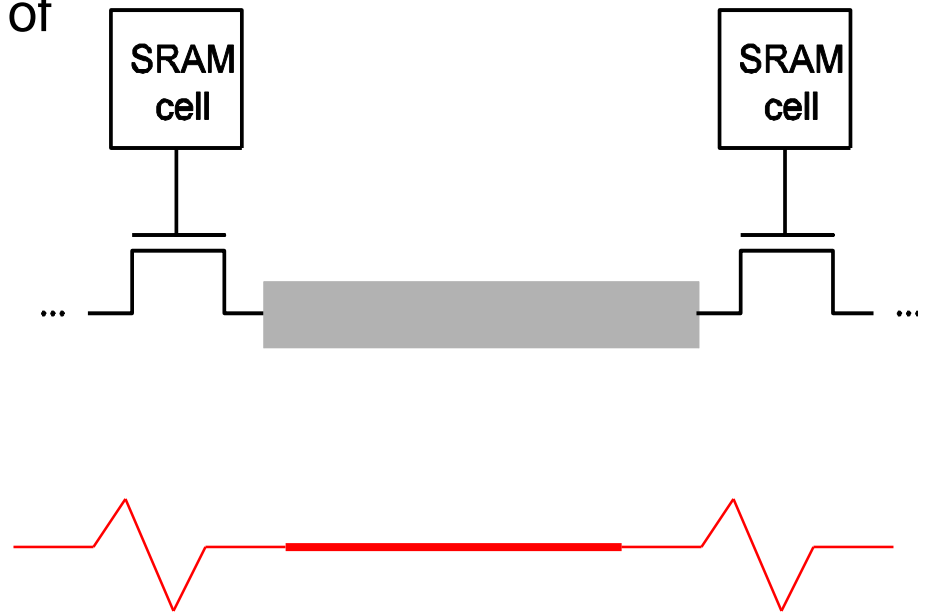- Small area.
- Resistive switch.
- Delay grows as the square of the number of switches.



Clock drivers

- Clock driver tree:

 



Clock nets

- Must drive all LEs.
- Design parameters:
 - number of fanouts;
 - load per fanout;
 - wiring tree capacitance.
- Determine optimal buffer sizes.