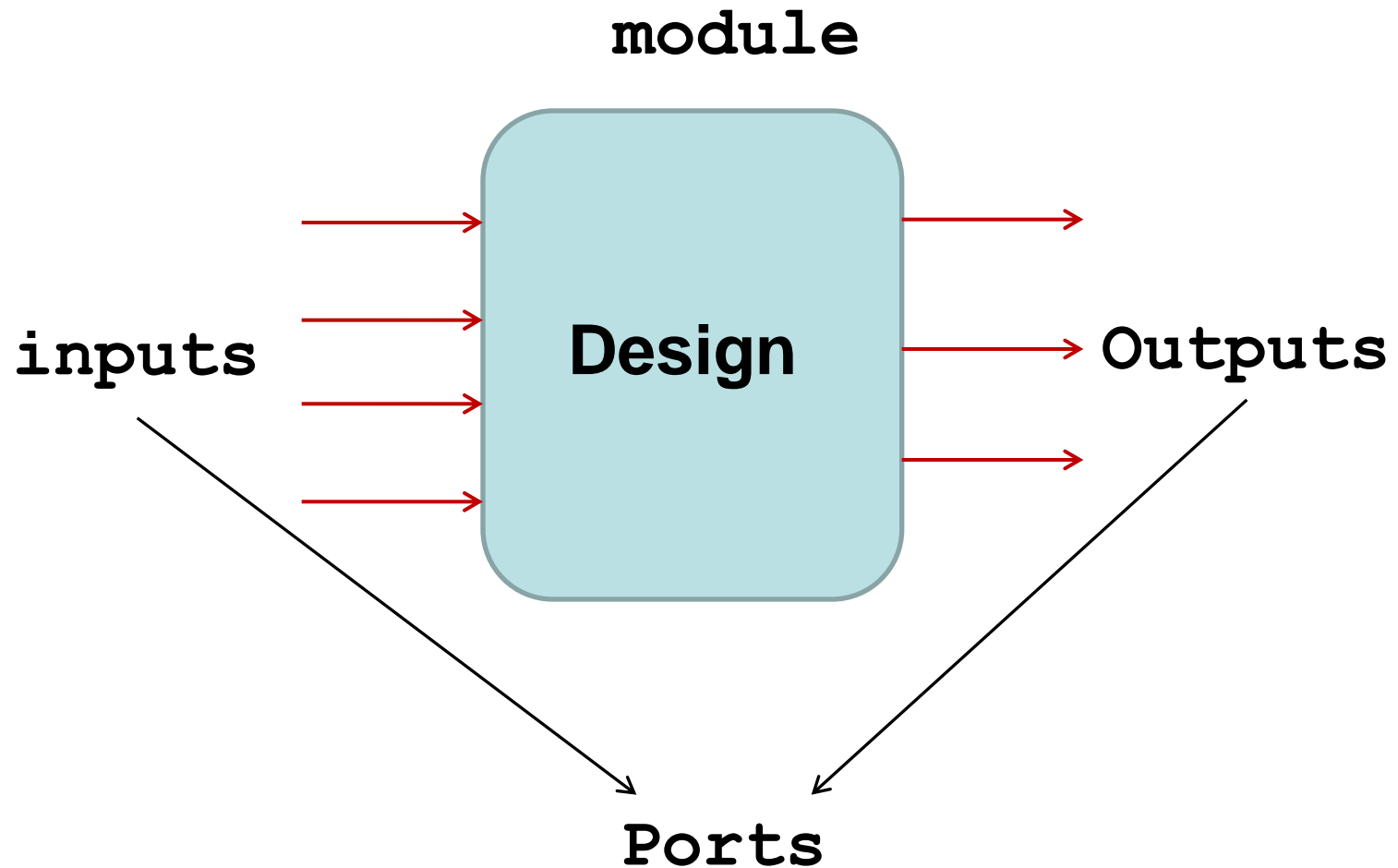


VerilogHDL



Module Structure



Basic Modeling structure

```
module module_name(port_list);
```

```
port declarations
```

```
data type declarations
```

```
circuit functionality
```

```
endmodule
```

- Begins with keyword **module** and ends with keyword **endmodule**
- Case –sensitive
- All keywords are lowercase
- Whitespace for readability
- Semicolon is the statement terminator
- // single line comment
- /* ... */ Multiline comment



Modules and Ports

```
module SR_latch(Q, Qbar, Sbar, Rbar);
```

```
output Q, Qbar;
```

```
input Sbar, Rbar;
```

```
...
```

```
...
```

```
...
```

```
endmodule
```

- Module name includes port list
- Port types
 - Input
 - Output
 - inout
- Port declarations
<port type> <port name>



First Exercise – Gate level

- Develop the Boolean function of output
- Draw the circuit with logic gates/primitives
- Connect gates/primitives with net (usually wire)
- write HDL description





Primitives

- Primitives are modules ready to be instanced
- Verilog build-in primitive gate
 - *and, or, xor, nand, nor, xnor*
 - `<prim_name>< inst_name>(out0, in0, in1,.....);`
 - *not, buf*
 - `<prim_name>< inst_name>(out0, out1, ..., in0);`



Gate-level Modeling

- Examples

  

```
module halfadder (S,C,x,y);  
    input x,y;  
    output S,C;  
    //Instantiate primitive gates  
    xor (S,x,y);  
    and (C,x,y);  
endmodule
```


Data Types

- Value set
- Nets
- Registers
- Vectors
- Integer & Real
- Strings
- Arrays
- Memory



Value Set

- 0 – Logic zero, false condition
- 1 – Logic one, true condition
- x – Unknown logic value
- z – High Impedance, floating state

Strength Level	Type	Degree
supply	Driving	strongest
strong	Driving	
pull	riving	
large	Storage	
weak	Driving	
medium	Storage	
small	Storage	
highz	High Impedance	weakest



Vectors

- Multiple bit widths
- **Nets** or **reg** data types can be declared as vectors

```
input a; // scalar net variable, default  
wire a;
```

```
input [3:0] a; // 4-bit signal  
wire [7:0] bus; // 8-bit bus
```


- Vectors can be declared as

```
[high# : low#]
```


```
[low# : high#]
```



Gate Types

 


		i1			
		0	1	x	z
i2	and	0	0	0	0
	0	0	0	0	0
	1	0	1	x	x
	x	0	x	x	x
z	0	x	x	x	

 


		i1			
		0	1	x	z
i2	or	0	1	x	x
	0	0	1	x	x
	1	1	1	1	1
	x	x	1	x	x
z	x	1	x	x	

Gate Types

 


		i1			
		0	1	x	z
i2	nand	1	1	1	1
	0	1	0	x	x
	x	1	x	x	x
	z	1	x	x	x

 


		i1			
		0	1	x	z
i2	nor	1	0	x	x
	0	0	0	0	0
	x	x	0	x	x
	z	x	0	x	x

Gate Types

 

buf	in	out
	0	0
	1	1
	x	x
	z	x

 

not	in	out
	0	1
	1	0
	x	x
	z	x

- Keywords: **buf** **not**



Gate Types

- **bufif** / **notif**
- additional control signals on **buf** and **not** gates

bufif1

notif1


bufif0

notif0


- gates propagate only if their control signal is asserted
- propagate z if their control signal is deasserted




Gate Types

 


		ctrl			
		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

 

		ctrl			
		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	x	z	x	x

 



		ctrl			
		0	1	x	z
in	0	z	1	H	H
	1	z	0	L	L
	x	z	x	x	x
	z	z	x	x	x

 


		ctrl			
		0	1	x	z
in	0	1	z	H	H
	1	0	z	L	L
	x	x	z	x	x
	z	x	z	x	x



Examples

  

Examples

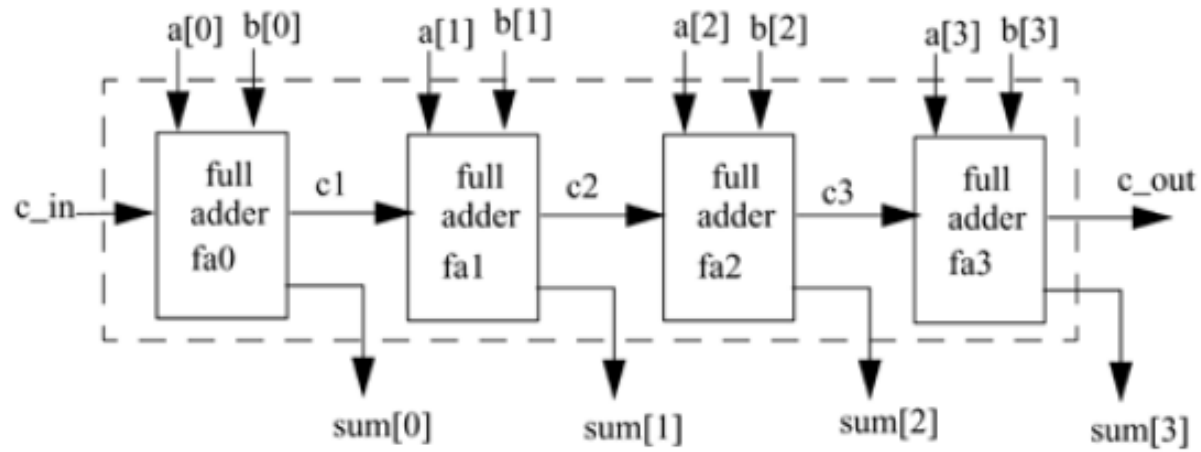

Stimulus block

```
module stimulus;
// Declare variables to be connected to inputs
reg IN0, IN1, IN2, IN3;
reg S1, S0;
// Declare output wire
wire OUTPUT;
// Instantiate the multiplexer
mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
// Stimulate the inputs. Define the stimulus module(no ports)
initial
begin
// set input lines
IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
#100 S1 = 0; S0 = 0;
#100 S1 = 0; S0 = 1;
#100 S1 = 1; S0 = 0;
#100 S1 = 1; S0 = 1;
end
endmodule
```



Dataflow Modeling

